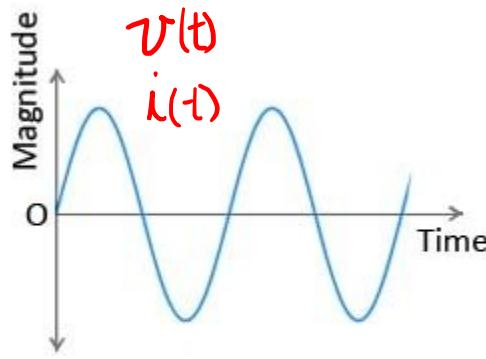


# 電子電工學

## Lecture 11




# Recap: AC circuits



Alternating Current

AC

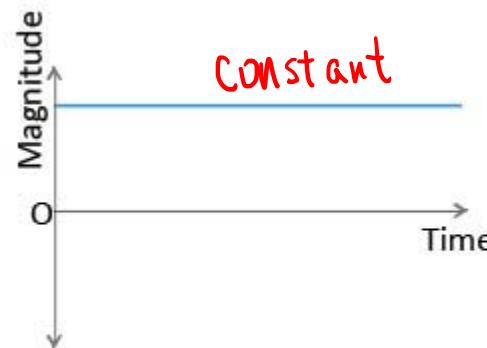

Direct Current

DC

Sinusoidal Wave

$$\cos(\omega t) \longrightarrow -\sin(\omega t) = \cos(\omega t + 90^\circ)$$

# Recap: basic AC sinusoidal wave

$$\text{KVL: } v_s(t) = v_R(t) + v_L(t)$$

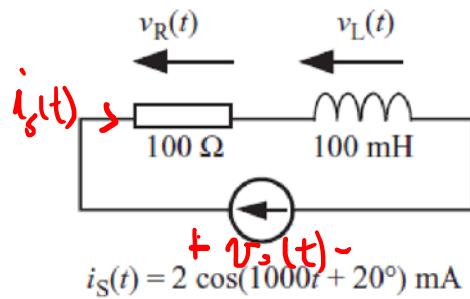


Figure 9.10 The circuit discussed in Example 9.2

= - - -

$$= 200 [ \cos(\omega t + 20^\circ) + \cos(\omega t + 110^\circ) ]$$

Given  $v_s(t) \rightarrow$  Find  $i_s(t) = ?$   
Differential Equation ?

- Laplace Transform
- Fourier Transform

\* Phasor diagram transform

Product to Sum Formula

Algebraic

Sum to Product Formula

$$\cos x + \cos y = 2 \cos \frac{x+y}{2} \cos \frac{x-y}{2}$$

$$\cos x - \cos y = -2 \sin \frac{x+y}{2} \sin \frac{x-y}{2}$$

$$\sin x + \sin y = 2 \sin \frac{x+y}{2} \cos \frac{x-y}{2}$$

$$\sin x - \sin y = 2 \cos \frac{x+y}{2} \sin \frac{x-y}{2}$$

$$2 \cos x \cos y = \cos(x+y) + \cos(x-y)$$

$$-2 \sin x \sin y = \cos(x+y) - \cos(x-y)$$

$$2 \sin x \cos y = \sin(x+y) + \sin(x-y)$$

$$2 \cos x \sin y = \sin(x+y) - \sin(x-y).$$

# Euler's formula

Let  $j = \sqrt{-1}$

$$e^{jx} = \cos x + j \sin x$$

2<sup>nd</sup> ODE :

e.g.  $y''(x) + \omega^2 y(x) = 0$

Sol 1.  $\begin{cases} y(x) = A \cos \omega x + B \sin \omega x \\ y'(x) = -A\omega \sin \omega x + B\omega \cos \omega x \\ y''(x) = -A\omega^2 \cos \omega x - B\omega^2 \sin \omega x \end{cases}$

Real  
Domain  
Solutions

Sol 2. Try  $y = e^{\lambda x} \rightarrow y' = \lambda e^{\lambda x} \rightarrow y'' = \lambda^2 e^{\lambda x}$

$$\Rightarrow \lambda^2 e^{\lambda x} + \omega^2 e^{\lambda x} = 0$$

$$\Rightarrow \lambda^2 + \omega^2 = 0 \Rightarrow \lambda = +j\omega, -j\omega$$

Complex  
Domain  
Solutions

$$\Rightarrow y_1 = e^{j\omega x} \quad y_2 = e^{-j\omega x}$$

# Euler's formula for ODE

Taylor's expansion

$$\begin{aligned} e^{jx} &= 1 + jx + \frac{(jx)^2}{2!} + \frac{(jx)^3}{3!} + \dots \\ &= \left(1 - \frac{x^2}{2!} + \frac{x^4}{4!} - \dots\right) + j \left(x - \frac{x^3}{3!} + \frac{x^5}{5!} + \dots\right) \\ &= \cos x + j \sin x \end{aligned}$$

# Euler's formula

$$e^{jx} = \cos x + j \sin x$$
$$e^{-jx} = \cos x - j \sin x$$

Conjugate


$$\Rightarrow \cos x = \frac{1}{2} [e^{jx} + e^{-jx}] = \operatorname{Re}[e^{jx}]$$
$$\sin x = \frac{1}{2j} [e^{jx} - e^{-jx}] = \operatorname{Im}[e^{jx}]$$

# Euler's formula

$$e^{jx} = \cos x + j \sin x$$

[Unit Circle in Complex Plane]
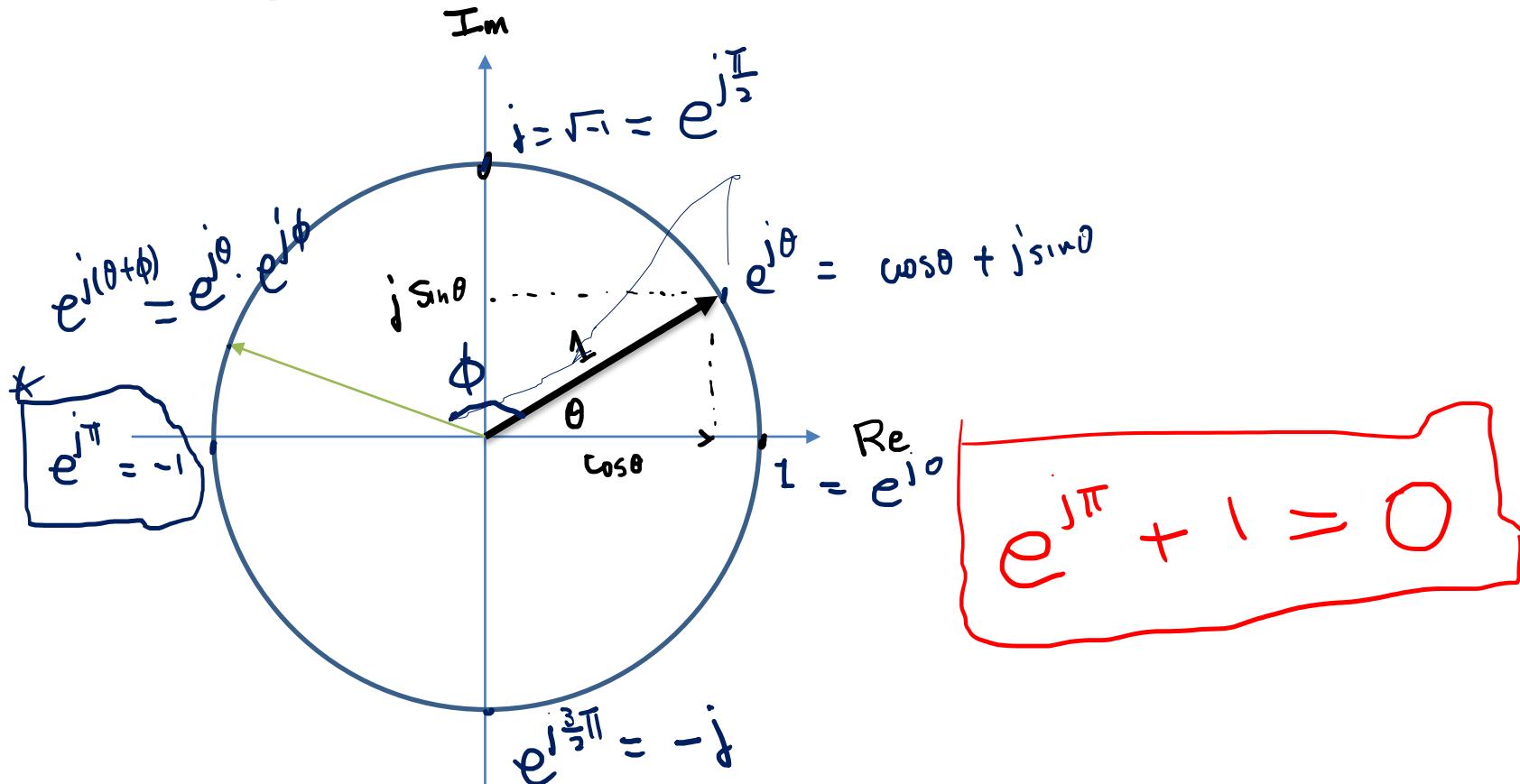
$$e^{j\theta} = \cos \theta + j \sin \theta$$



"...the most remarkable formula in mathematics."

--Richard Feynman

# Euler's formula for R-L circuits

Real  $i_s(t) = 2 \cos(1000t + 20^\circ)$


$$+ 2j \sin(1000t + 20^\circ) \rightarrow \hat{i}_s(t) = 2 e^{j(1000t + 20^\circ)}$$

$\text{KVL: } \hat{v}_s(t) = R \hat{i}_s(t) + L \frac{d}{dt} \hat{i}_s(t)$

$$= 200 e^{j(1000t + 20^\circ)} + 0.1 \cdot 2 j 1000 e^{j(1000t + 20^\circ)}$$

$$= 200 (1+j) e^{j(1000t + 20^\circ)}$$

Complex

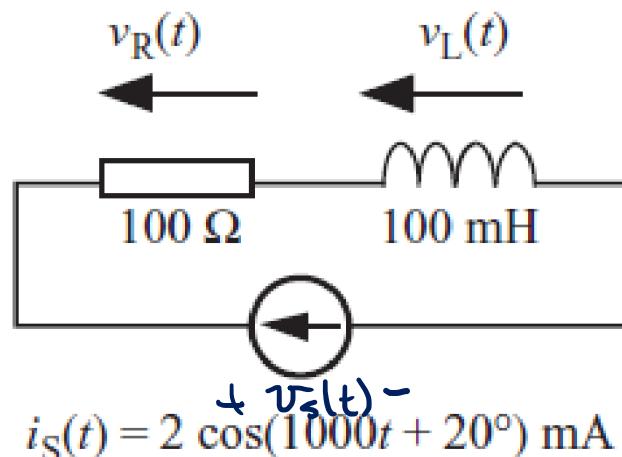



**Figure 9.10** The circuit discussed in Example 9.2

# Euler's formula for R-L circuits

$$\begin{aligned}\hat{V}_s(t) &= 200(1+j) e^{j(1000t + 20^\circ)} \\ &= 200 \sqrt{2} e^{j45^\circ} e^{j(1000t + 65^\circ)} \\ &= 200 \sqrt{2} e^{j(1000t + 65^\circ)}\end{aligned}$$

$\text{Re} \quad \hookrightarrow v_s(t) = 200 \sqrt{2} \cos(1000t + 65^\circ)$

No sum-product rule !!

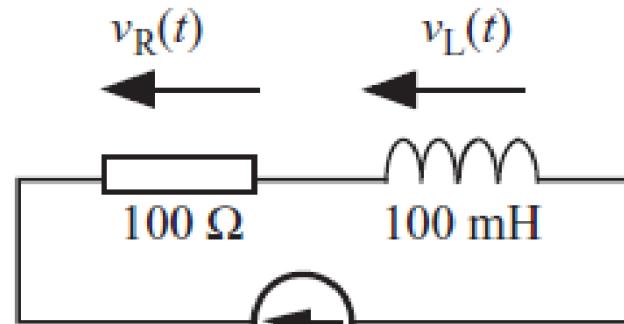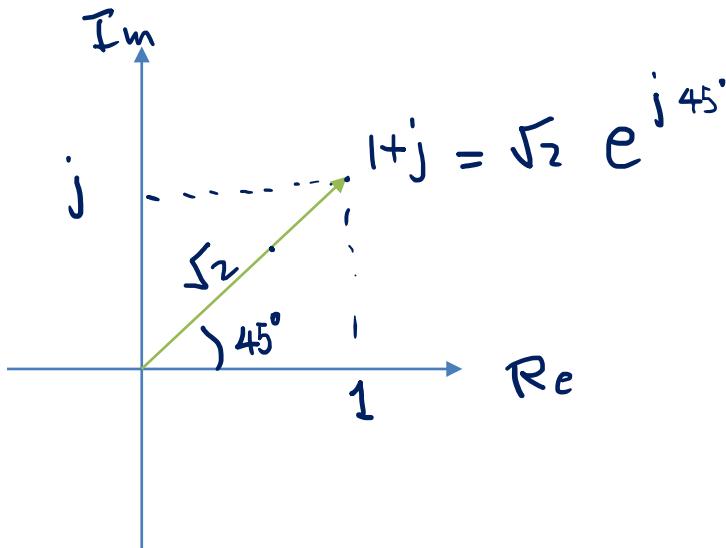

$$i_S(t) = 2 \cos(1000t + 20^\circ) \text{ mA}$$

Figure 9.10 The circuit discussed in Example 9.2

# Phasor

相量

→ Phase    Vector



Real Voltage  
Current

Transform

Complex Voltage  
current

$$v(t) = V \cos(\omega t) \rightarrow V(t) = V e^{j\omega t}$$
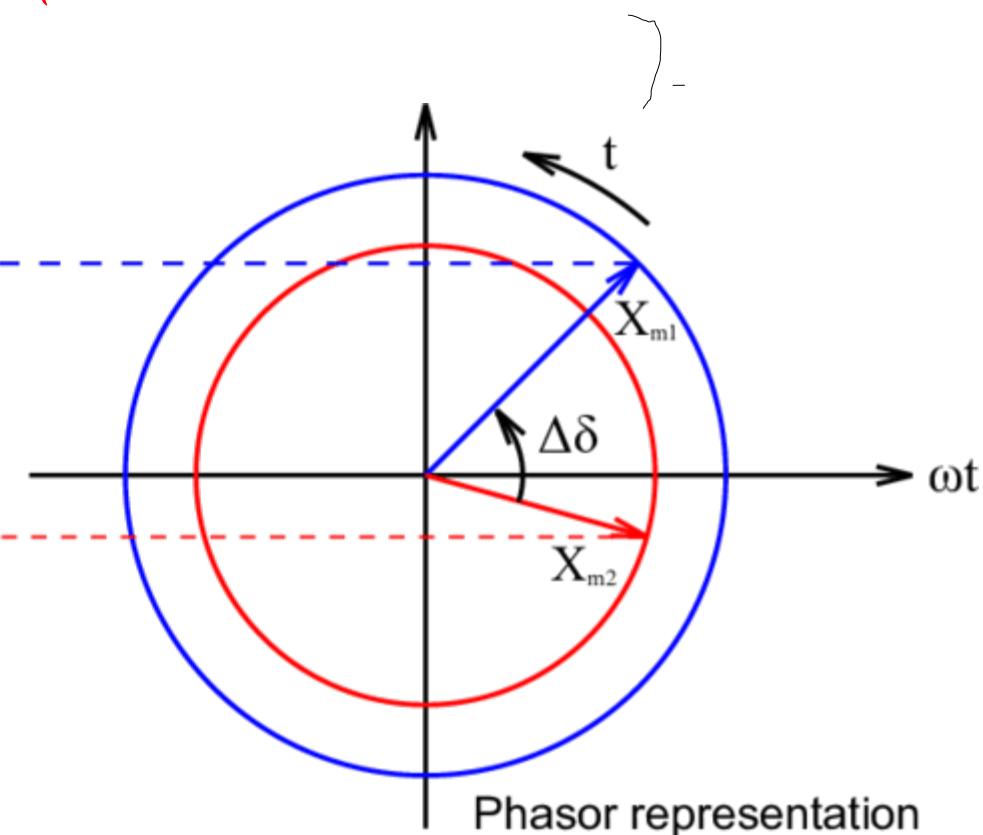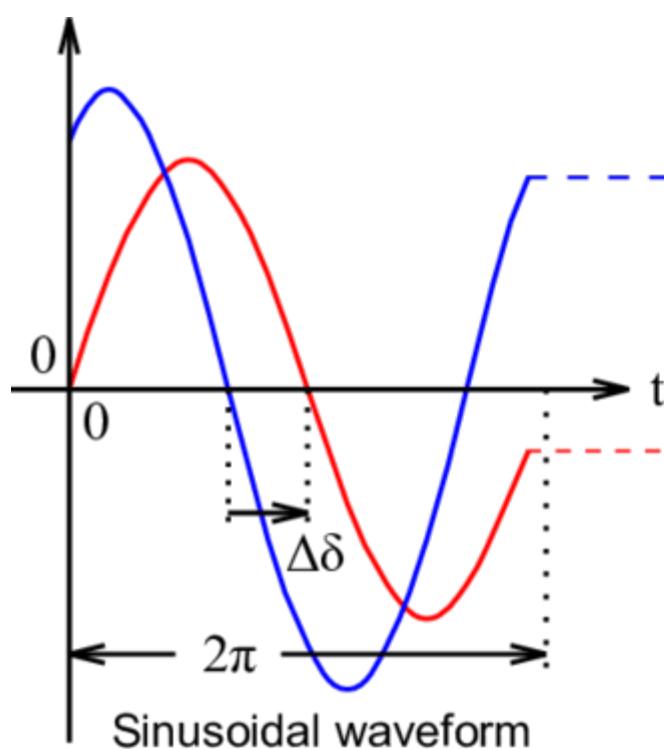
$$i(t) = I \cos(\omega t) \rightarrow I(t) = I e^{j\omega t}$$



# Phasor transform

Time-domain Phasor

$$f(t) = \operatorname{Re} \left[ F(\omega) e^{j\omega t} \right] \xrightarrow{\text{transform}} F(\omega)$$

$$A \cos \omega t = \operatorname{Re} [ A e^{j\omega t} ] \longrightarrow A$$

# Complex impedance - capacitor

$$v(t) = V \cos(\omega t) \xrightarrow{\text{complex transform}}$$

$$i(t) = C \frac{dv(t)}{dt}$$

$$i(t) = \operatorname{Re} \{ j\omega CV e^{j\omega t} \}$$

$$\begin{aligned} j &= e^{j\frac{\pi}{2}} \\ &= e^{j90^\circ} \end{aligned}$$

$$\begin{aligned} i(t) &= \omega CV \operatorname{Re} \{ e^{j\frac{\pi}{2}} e^{j\omega t} \} \\ &= \omega CV \cos(\omega t + \frac{\pi}{2}) \end{aligned}$$


↓  
phasor

$$V(t) = V e^{j\omega t}$$

$$I(t) = C \frac{d}{dt} (V e^{j\omega t})$$

$$I(t) = j\omega C V e^{j\omega t}$$

$$I(t) = j\omega C V(t)$$

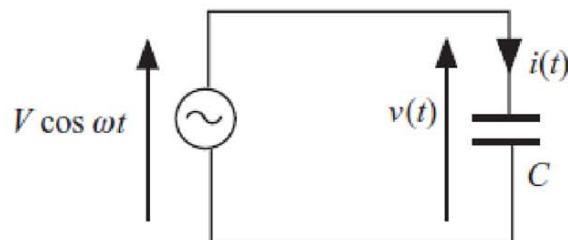

**Figure 9.2** A capacitor with its voltage defined by a sinusoidal voltage source of radian frequency  $\omega$


## Generalized Ohm's law - capacitor

$$I(t) = j\omega C V(t) *$$

$$V(t) = \frac{1}{j\omega C} I(t)$$

$$V(t) = Z_C I(t)$$


↓  
Impedance of capacitor

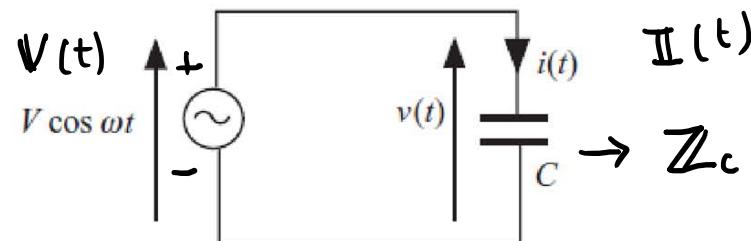

**Figure 9.2** A capacitor with its voltage defined by a sinusoidal voltage source of radian frequency  $\omega$

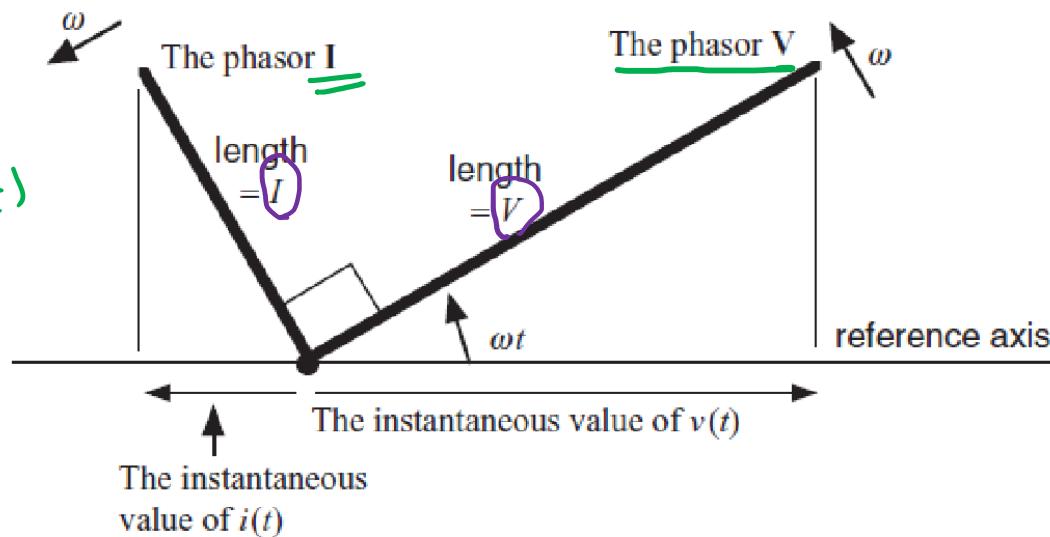
# Phasor diagram - capacitor

$$\begin{aligned} \mathbb{I}(t) &= j\omega C \underline{\underline{V(t)}} \\ &= e^{j\frac{\pi}{2}} \omega C \underline{\underline{V}} e^{j\omega t} \\ &= \omega C V e^{j(\omega t + \frac{\pi}{2})} \end{aligned}$$



$$V(t) = V e^{j\omega t}$$

$V \cos \omega t$

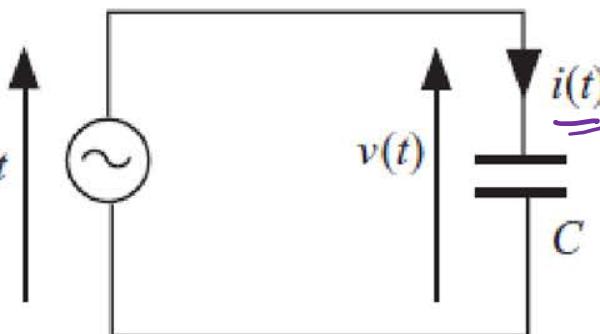


**Figure 9.11** A capacitor with its voltage defined by a sinusoidal voltage source of radian frequency  $\omega$

# Complex impedance - inductor

$$\text{Source } I(t) = I e^{j\omega t}$$

$$\begin{aligned} V(t) &= L \frac{d I(t)}{dt} \\ &= j\omega L \underline{I} e^{j\omega t} \\ V(t) &= j\omega L \underline{I(t)} \end{aligned}$$

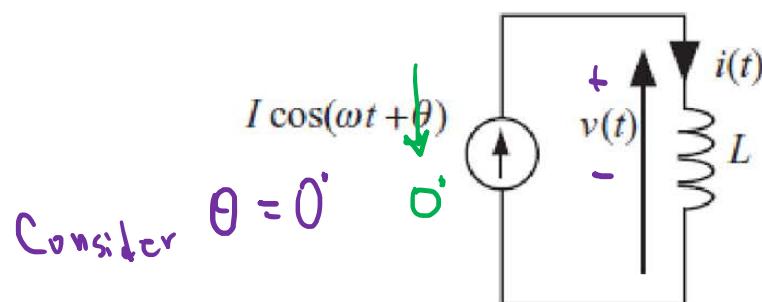


**Figure 9.7** An inductor with its current defined by a sinusoidal current source of radian frequency  $\omega$

# Generalized Ohm's law - inductor

$$V(t) = j\omega L I(t)$$

$\downarrow$

$\cancel{Z}_L$  : Impedance  
of inductor  $L$

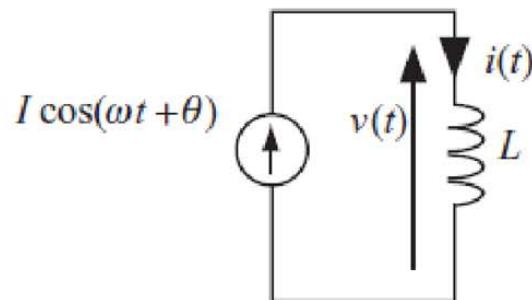

**Figure 9.7** An inductor with its current defined by a sinusoidal current source of radian frequency  $\omega$

# Phasor diagram - inductor

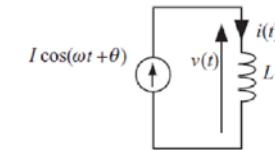



Figure 9.7 An inductor with its current defined by a sinusoidal current source of radian frequency  $\omega$

$$v(t) = \omega L I \cos\left(\omega t + \theta + \frac{\pi}{2}\right)$$

$\text{Re}[\cdot]$

$$V(t) = j\omega L \cdot I(t)$$
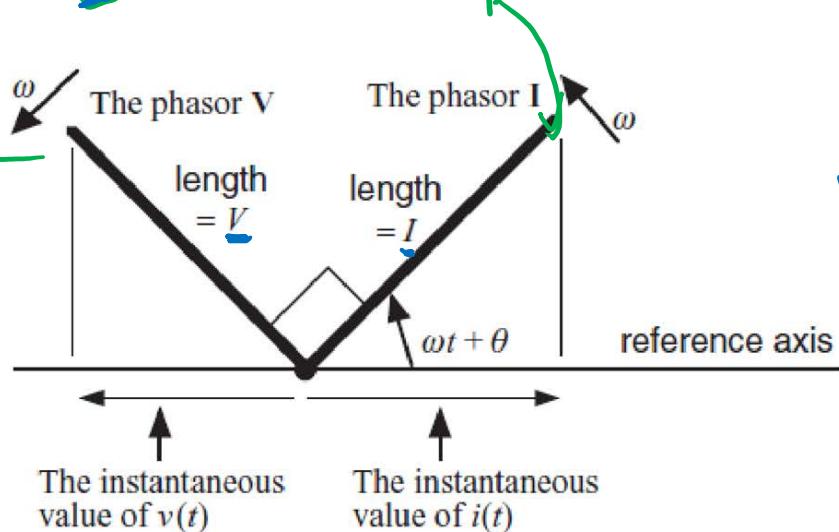
$$V(t) = j\omega L \underbrace{I e^{j(\omega t + \theta)}}_R$$



$$V = \omega L I$$


Figure 9.13 A Phasor diagram showing phasors representing inductor voltage and current

# Phasor diagram - resistor

Complex

$$\begin{aligned} V(t) &= R i(t) \\ V(t) &= R \mathbb{I}(t) \end{aligned}$$

$$V = R \cdot \mathbb{I}$$

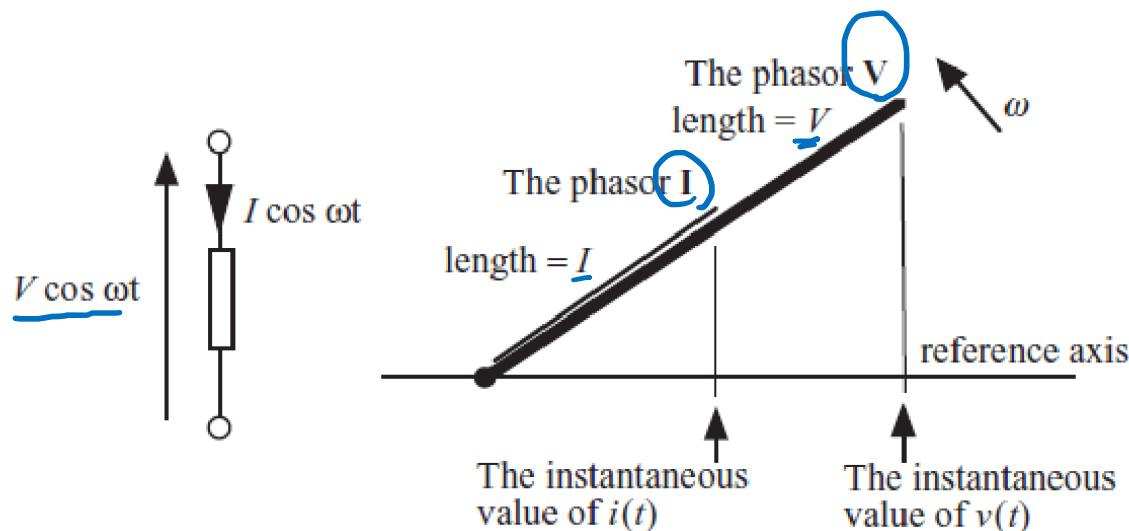




**Figure 9.14** The phasors representing the sinusoidal voltage and current of a resistor are in phase. The current phasor has been offset slightly for clarity

# Phasor diagram

$$V(t) = \boxed{\frac{1}{j\omega C}} \cdot I(t)$$

$$V(t) = \boxed{j\omega L} \cdot I(t)$$










$$V(t) = \boxed{R} \cdot I(t)$$

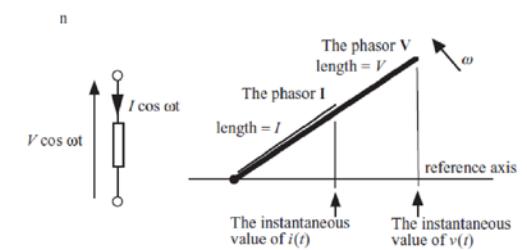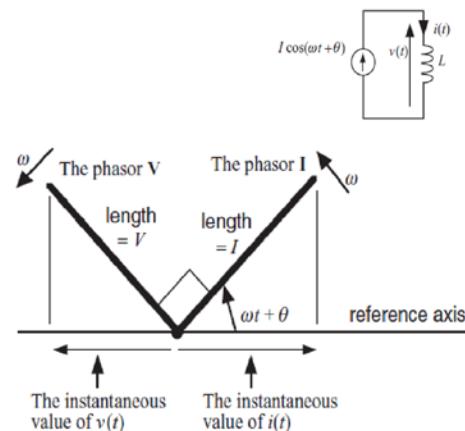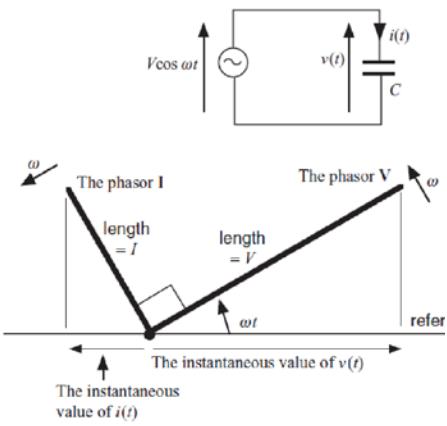

**Figure 9.12** A phasor diagram showing phasors representing capacitive voltage and current. Note that the phasors rotate at an angular frequency  $\omega$  and it is the reference axis that determines the actual scalar instantaneous values  $v(t)$  and  $i(t)$ .

**Figure 9.13** A phasor diagram showing phasors representing inductive voltage and current.

**Figure 9.14** The phasors representing the sinusoidal voltage and current of a resistor are in phase. The current phasor has been offset slightly for clarity.

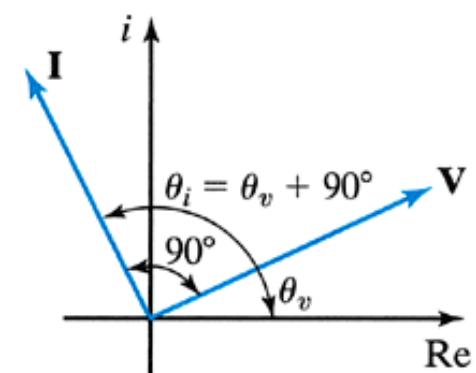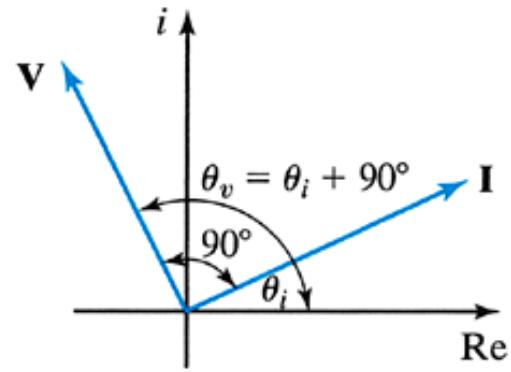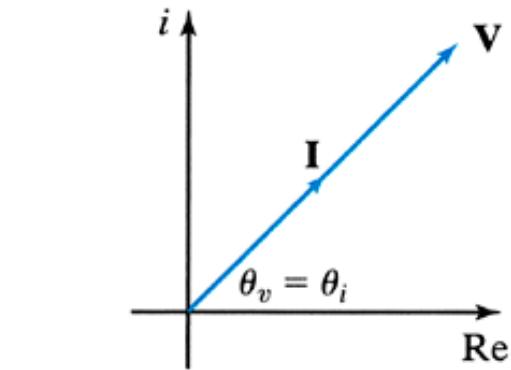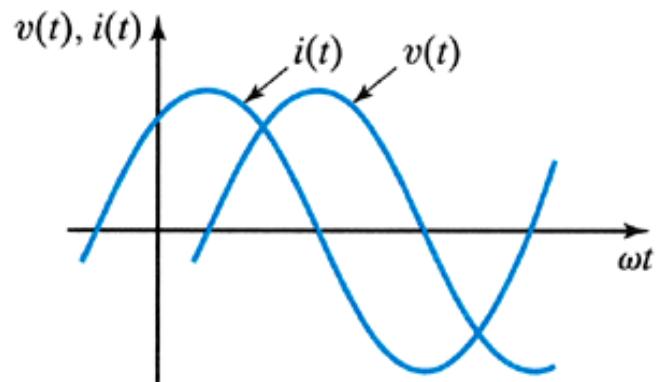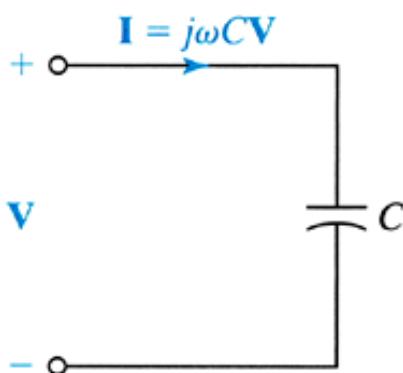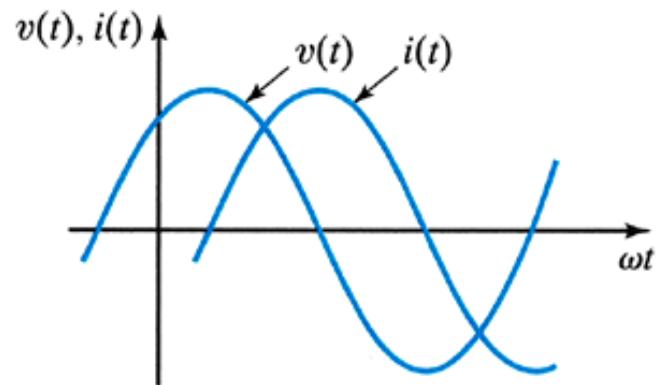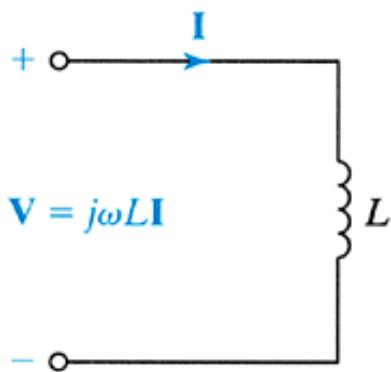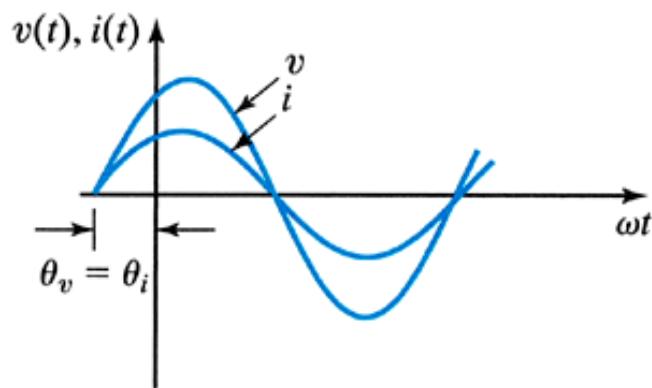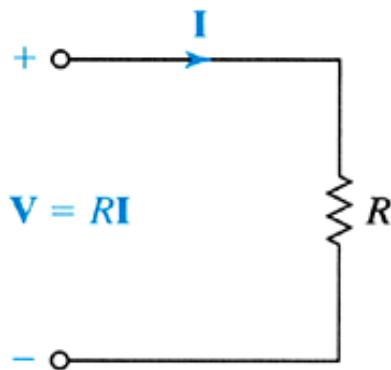



**FIGURE 4.6** Characteristics of the passive elements  $R$ ,  $L$ , and  $C$ .

# Kirchhoff's laws – phasor addition

KVL holds at any time  $t$

Transform

$$\begin{aligned}
 v(t) &= v_1(t) + v_2(t) \\
 &= V_1 \cos(\omega t + \theta_1) + V_2 \cos(\omega t + \theta_2) \\
 \Rightarrow v(t) &= V_1 e^{j(\omega t + \theta_1)} + V_2 e^{j(\omega t + \theta_2)} \\
 &= V_1(t) + V_2(t)
 \end{aligned}$$

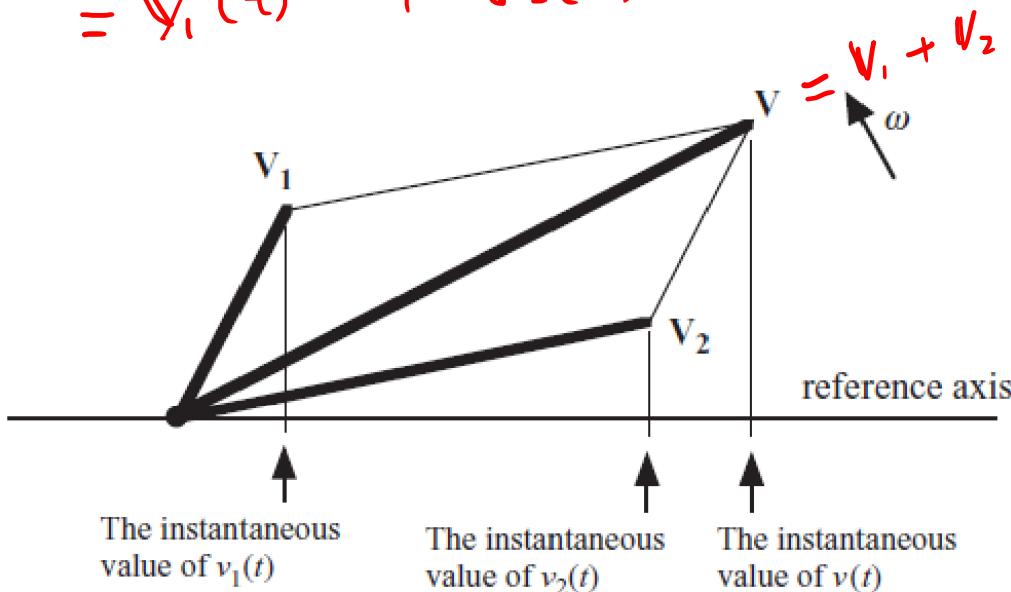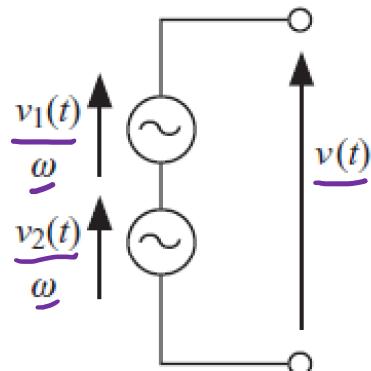

**Figure 9.15** A Phasor diagram showing that the phasor addition of voltages obeys KVL. Hairlines are used to indicate construction

# Kirchhoff's laws

DC / AC circuits

$$KCL: \sum_{\text{node}} I_i(t) = 0$$


$$KVL: \sum_{\text{loop}} V_n(t) = 0$$

Generalized Ohm's law

$$V(t) = \sum I(t)$$

Complex / phasor

NODAL ANALYSIS  
 SUPERPOSITION  
 THEVENIN'  
 NORTON EQUIV.  
 CKTS

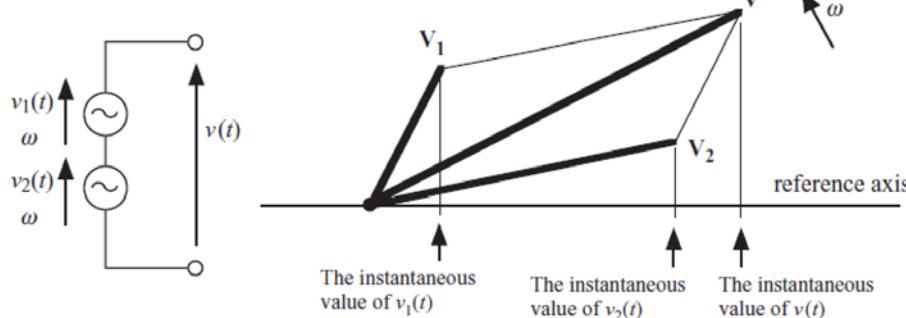


**Figure 9.15** A Phasor diagram showing that the phasor addition of voltages obeys KVL. Hairlines are used to indicate construction

# Sum of phasors

$$y(t) = y_1(t) + y_2(t)$$

Phasor ↓
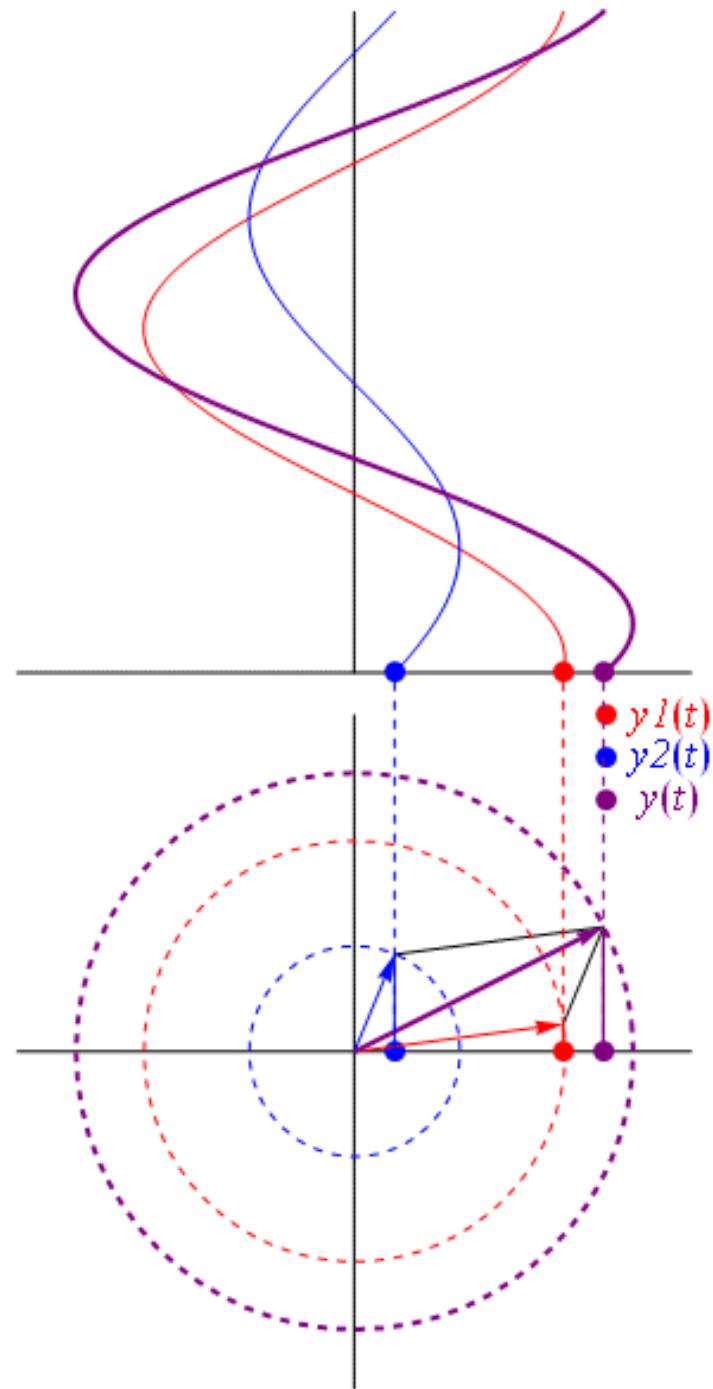
$$\mathbf{y}(t) = \mathbf{y}_1(t) + \mathbf{y}_2(t)$$



# Constructing a phasor diagram

$$v_s(t) = 2 \cos(1000t) \rightarrow v_s(t) = 2 e^{j1000t}$$

KCL @ X :  $\underline{I}(t) = \underline{I}_R(t) + \underline{I}_C(t)$


$$\left. \begin{array}{l} \omega = 1000 \\ R = 1000 \Omega \\ C = 10^{-6} F \\ L = 1 H \end{array} \right\}$$

$$\begin{aligned} &= \frac{V(t)}{R} + (j\omega C)V(t) \\ &= \left(\frac{1}{R} + j\omega C\right)V(t) \\ &= 10^{-3}(1+j)V(t) \end{aligned}$$

$$\underline{V}_L(t) = (j\omega L)\underline{I}(t)$$

$$= j(1+j)V(t)$$

$$\underline{I}(t) = (-1+j)V(t)$$

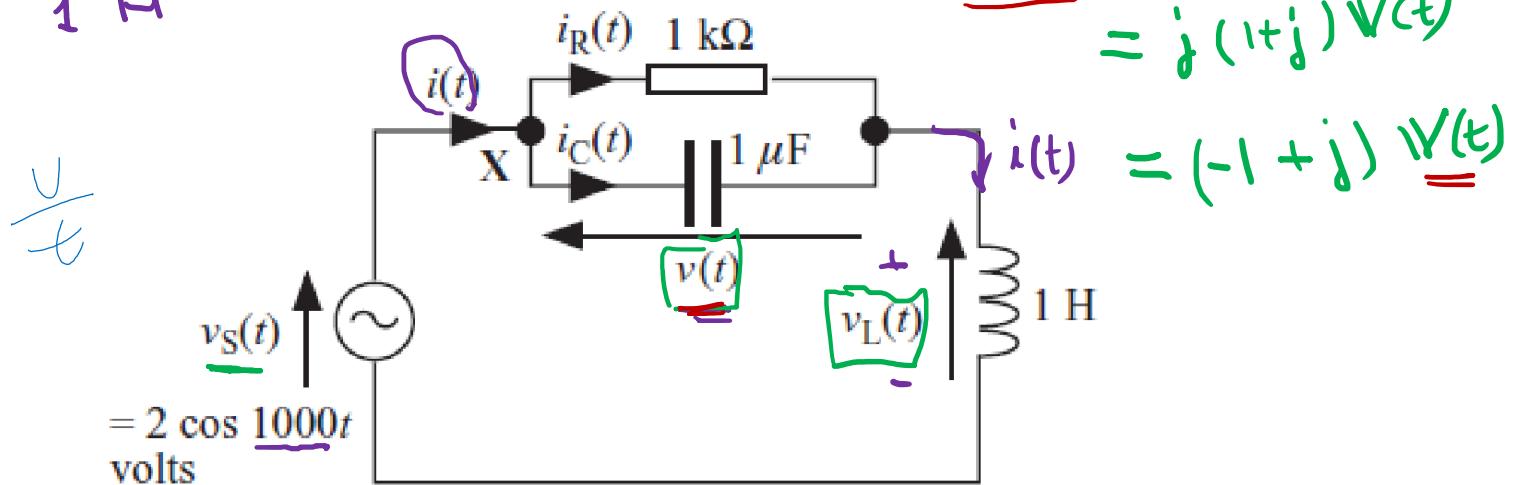

**Figure 9.16** The circuit whose phasor diagram is to be constructed


# Constructing a phasor diagram

$$\begin{aligned}
 \text{KVL : } V_s(t) &= V(t) + V_L(t) \\
 &= V(t) + (-1+j)V(t) \\
 &= jV(t) \\
 \Rightarrow V(t) &= \frac{1}{j}V_s(t) = -jV_s(t) = -e^{j\frac{\pi}{2}} \cdot 2e^{j1000t} \\
 &= -2e^{j(1000t + \frac{\pi}{2})} = e^{j(1000t - \frac{\pi}{2})}
 \end{aligned}$$




$\text{Re}[\cdot]$      $v(t) = -2 \cos(1000t + \frac{\pi}{2}) = 2 \cos(1000t - \frac{\pi}{2})$   
 $V_L(t) = \underline{(-1+j)} V(t)$   
 $= \underline{\sqrt{2}} e^{j\frac{3}{4}\pi} V(t)$

$\text{Re}[\cdot]$      $v_L(t) = 2\sqrt{2} \cos(600t + \frac{\pi}{4})$



Figure 9.16 The circuit whose phasor diagram is to be constructed

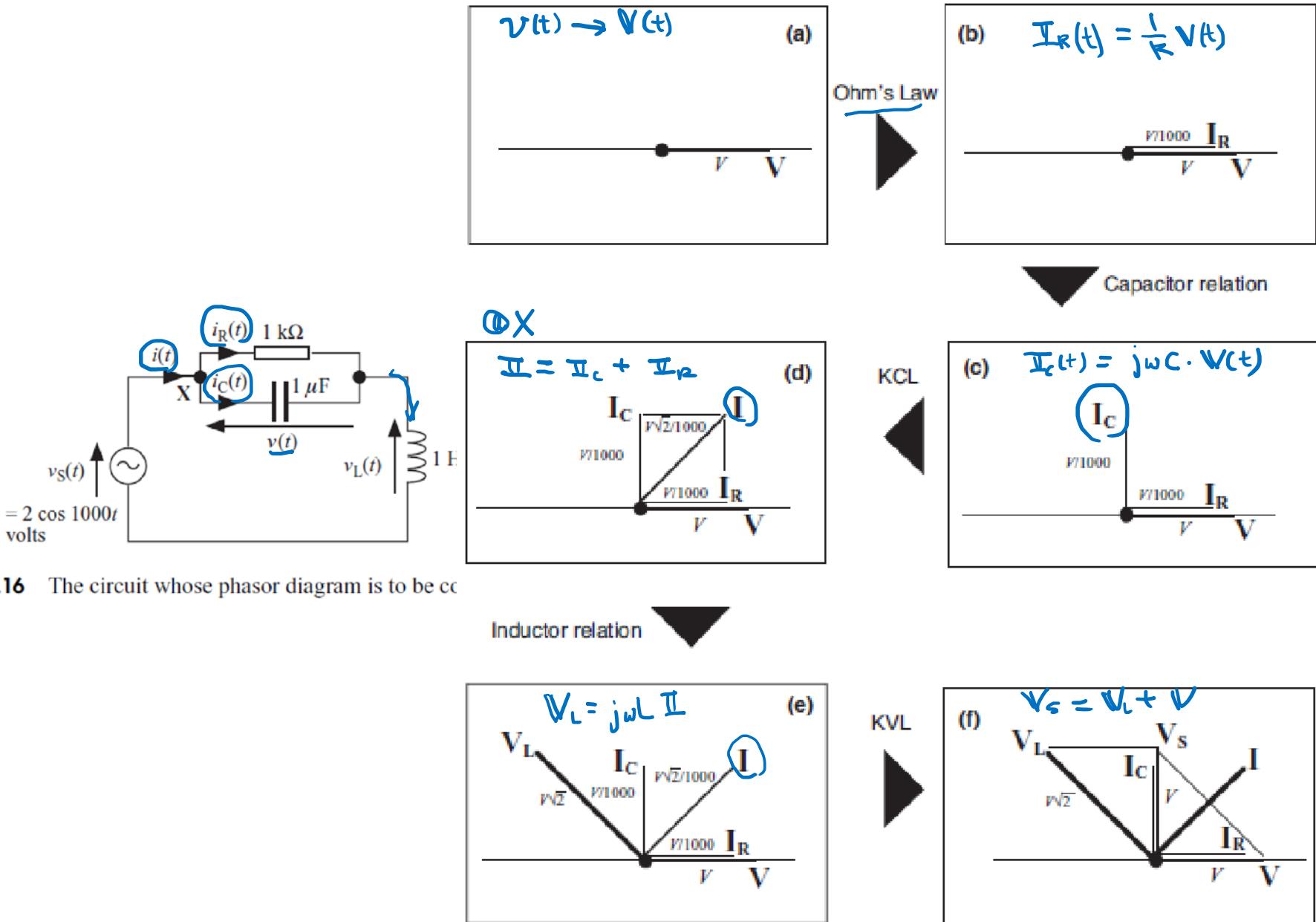



**Figure 9.17** Steps in the construction of a phasor diagram for the circuit of Figure 9.16. Where possible phasor lengths have been indicated beside the phasor. Some overlapping phasors have been offset slightly for clarity. Hairlines are included to indicate constructions.

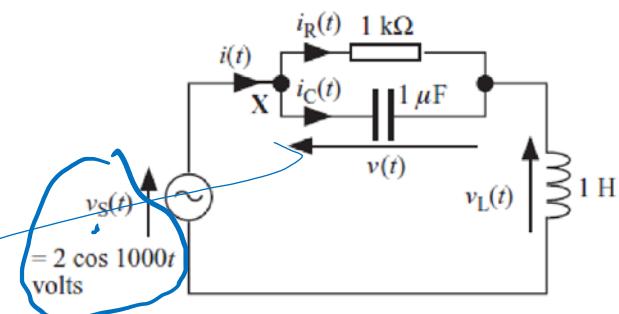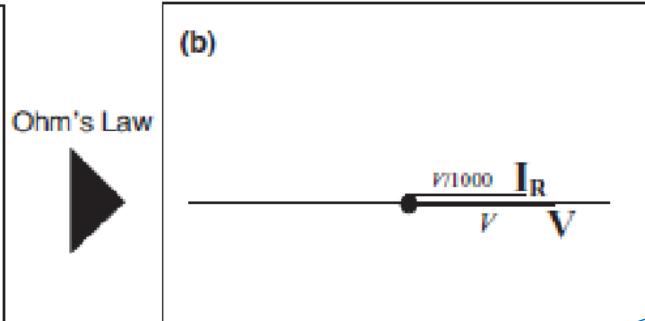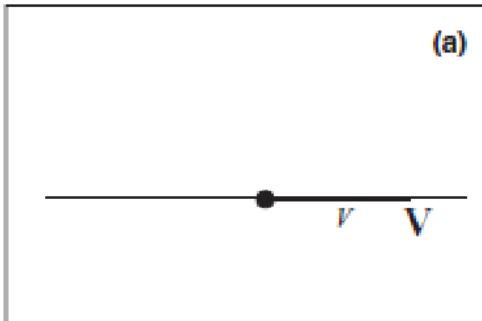

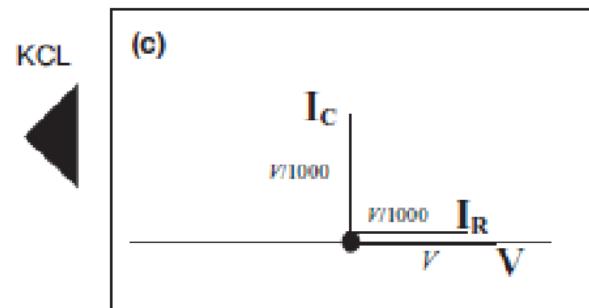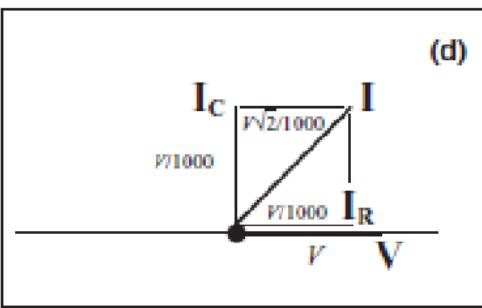9.16 The circuit whose phasor diagram is to be constructed



Inductor relation

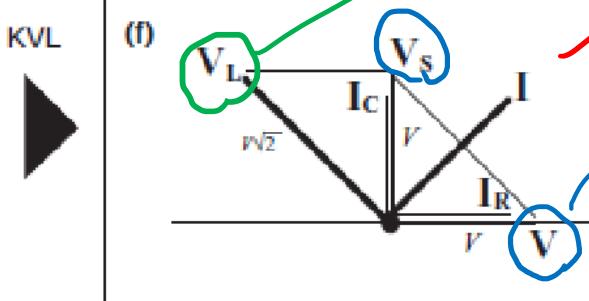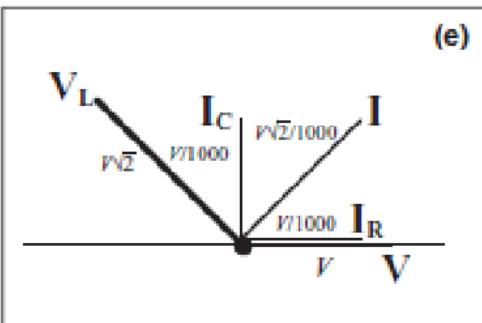

$$V_L = 2\sqrt{2} e^{j(1000t + \frac{\pi}{4})}$$

$$V_s(t) = 2 e^{j1000t}$$


$$I(t) = \frac{2\sqrt{2}}{1000} e^{j(1000t - \frac{\pi}{4})}$$

$$V(t) = 2 e^{j(1000t - \frac{\pi}{2})}$$

Figure 9.17 Steps in the construction of a phasor diagram for the circuit of Figure 9.16. Where possible phasor lengths have been indicated beside the phasor. Some overlapping phasors have been offset slightly for clarity. Hairlines are included to indicate constructions
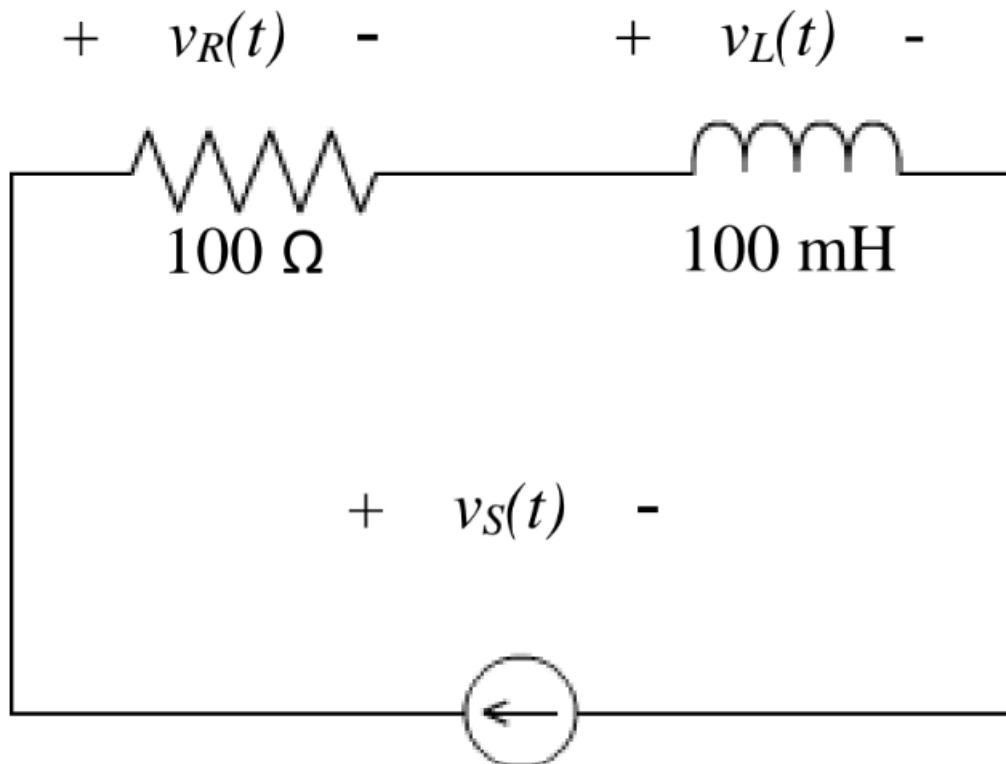
# Quiz

Sketch a dimensioned phasor diagram representing all the voltages  $v_R$ ,  $v_L$  and  $v_S$ , as well as the current  $i_S$ , in the circuit of the following figure.



$$i_S(t) = 2 \cos(1000t + 20^\circ) \text{ mA}$$

# Quiz review

