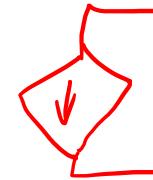


Recap

- Dependent sources vs Independent sources
- Circuit analysis for voltage controlled current source (VCCS)
 - Nodal analysis
 - Superposition
 - Thevenin's equivalent circuit
- Non-linear component

VCCS dependent



VCCS

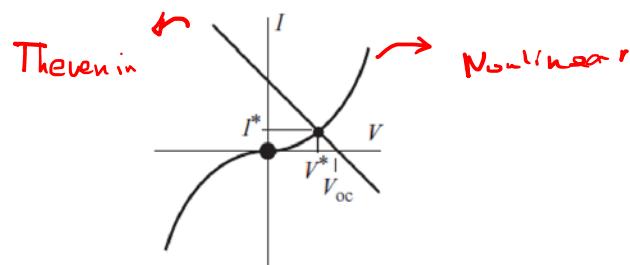


Figure 5.13 The point I, V must lie on both characteristics, and hence at their intersection (I^*, V^*)

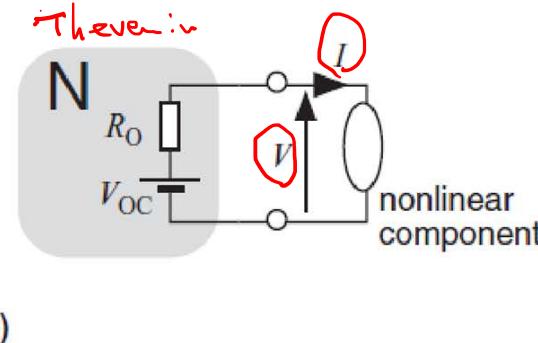
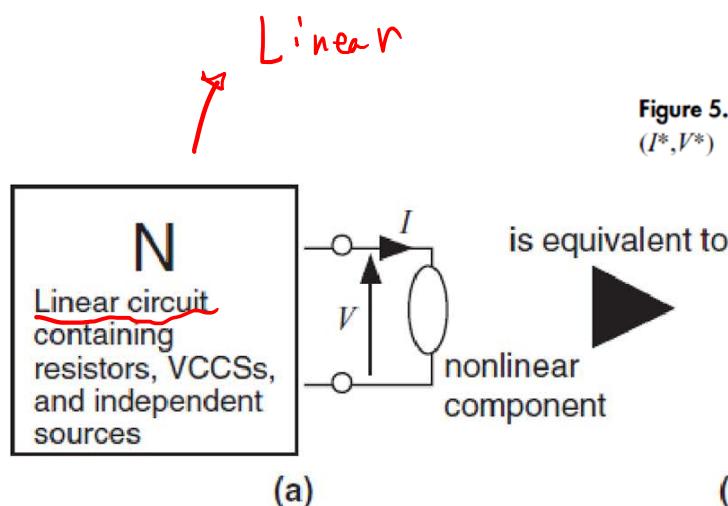


Figure 5.11 (a) A circuit containing one nonlinear component whose voltage and current are of interest; (b) a representation of the linear part of the circuit by a Thevenin model

Quiz 4 Review

The circuit of Fig. 1 contains a Zener diode (as in Fig. 2). A good approximation to its I - V relation is shown in Fig. 3. The maximum power that can be absorbed by the diode and dissipated as heat is 250 mW.

1. Calculate the minimum value of R that will keep the Zener diode in operation.
2. Calculate the power dissipated by the resistor R .

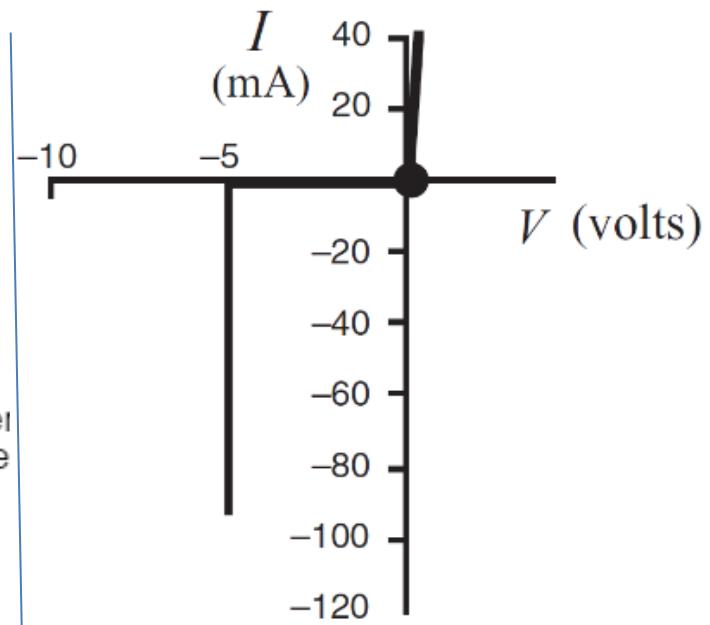
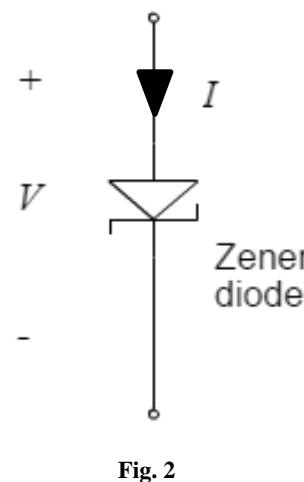
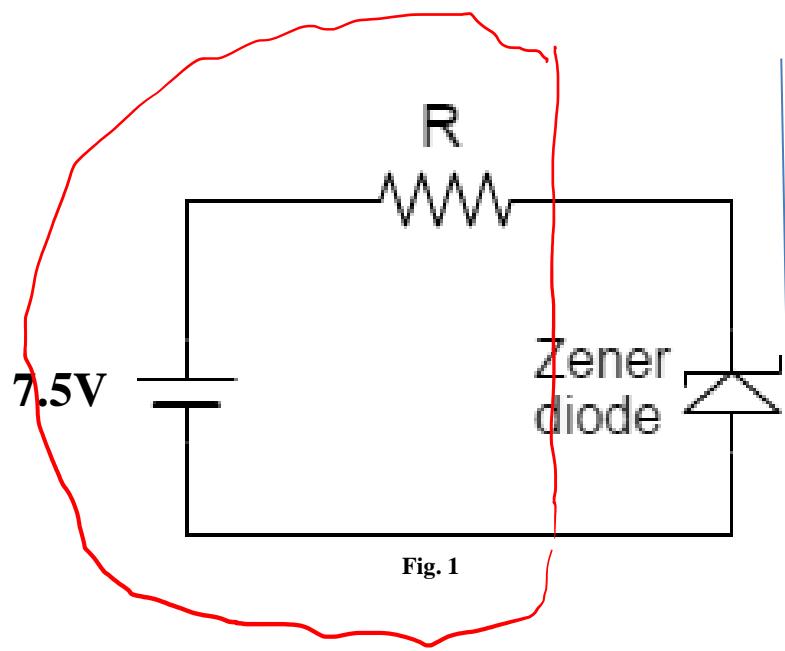


Fig. 3

Chapter 6

運算

放大器

Operational Amplifier

OPAMP

Opamp

Operational amplifier


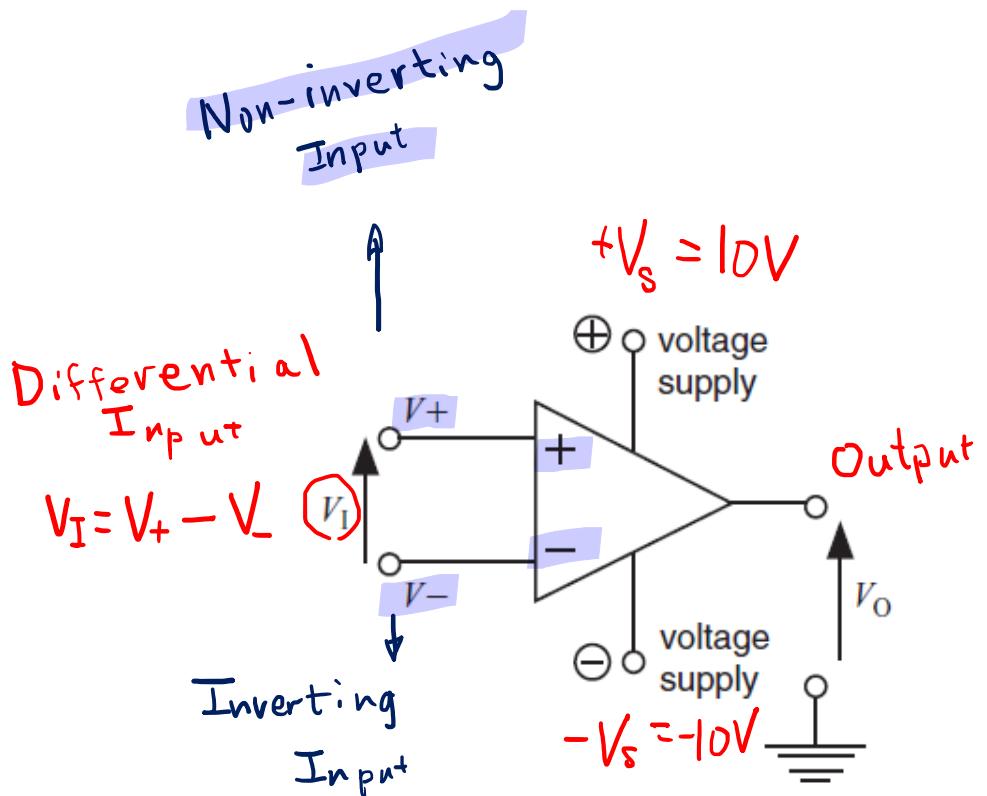
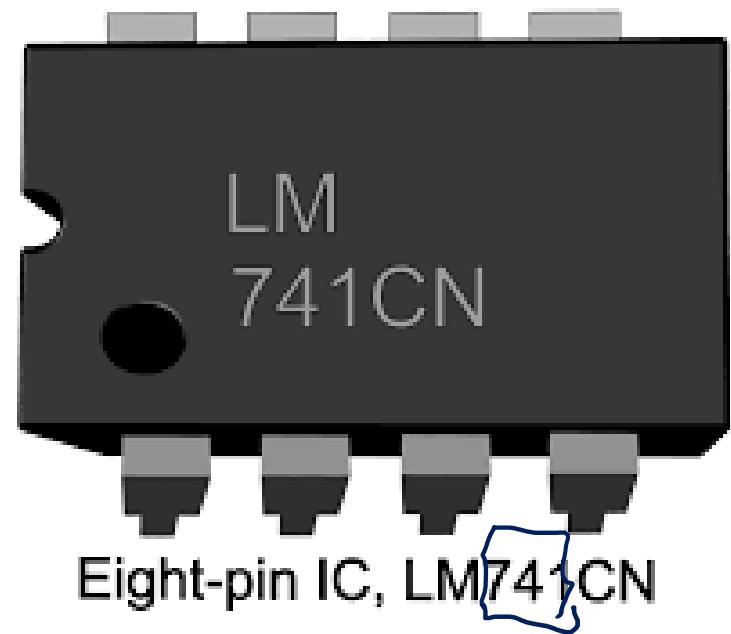


Figure 6.1 The voltages associated with an operational amplifier

Operational amplifier

Implemented in Integrated Chip

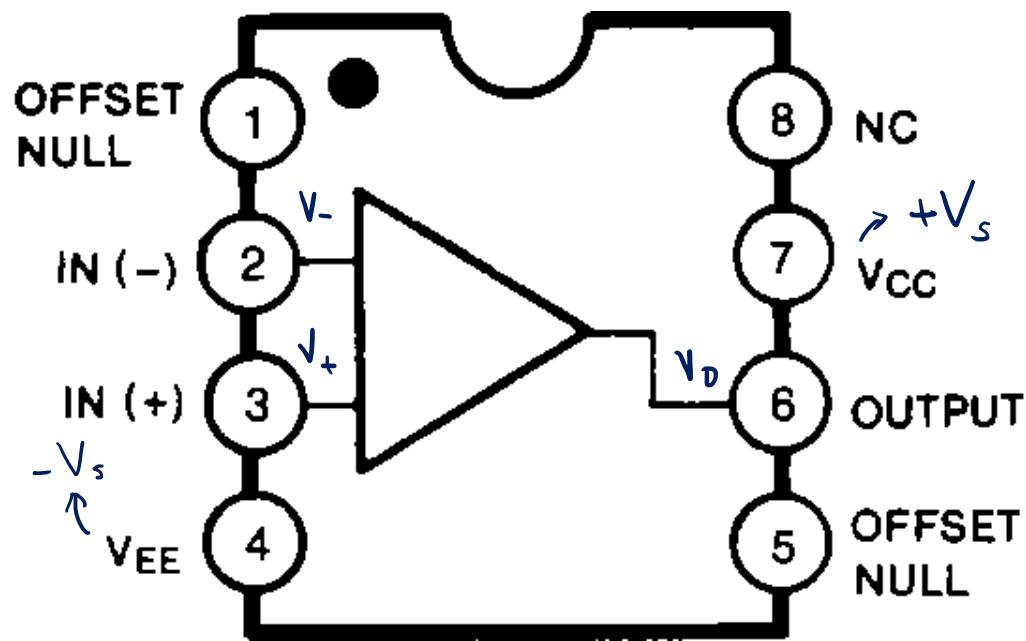- {
 - Transistor
 - Capacitor
 - Resistor
 - Diode




Eight-pin IC, LM741CN

Uses :

- {
 - Amplifier
 - Active Filter
 - Analog Computing

Operational amplifier characteristic

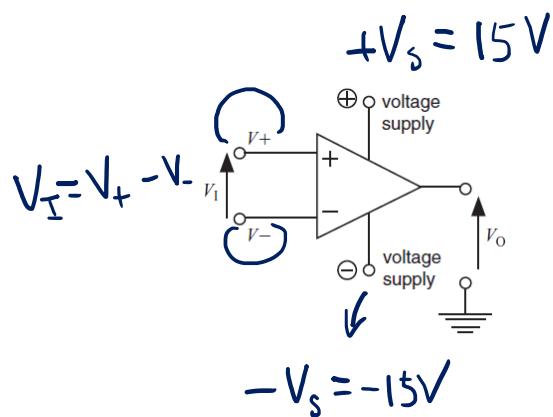

$$V_0 = \begin{cases} +V_s & \text{if } V_I > \frac{V_s}{A} \\ A V_I, & \text{if } -\frac{V_s}{A} < V_I < \frac{V_s}{A} \\ -V_s & \text{if } V_I < -\frac{V_s}{A} \end{cases}$$


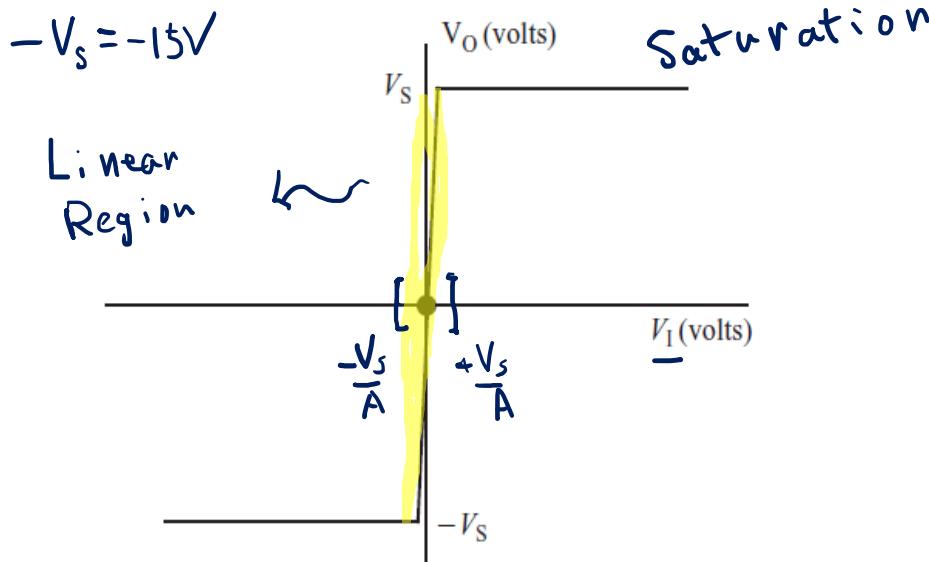


Figure 6.2 The form of the relation between the input V_I and output V_O voltages of an opamp

Simplified symbol

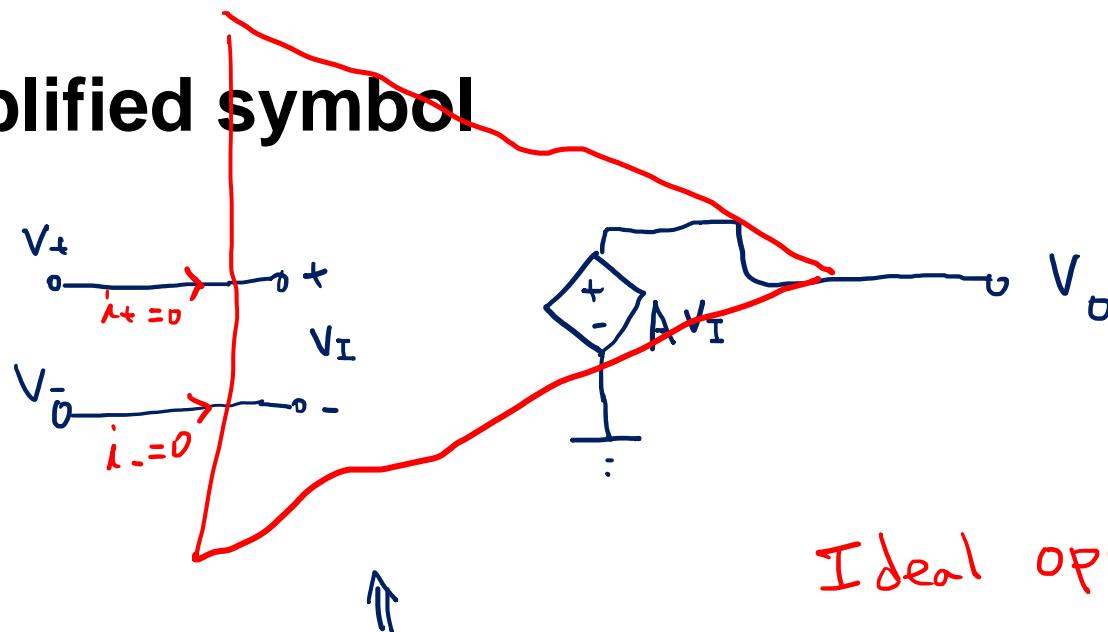

Ideal opamp


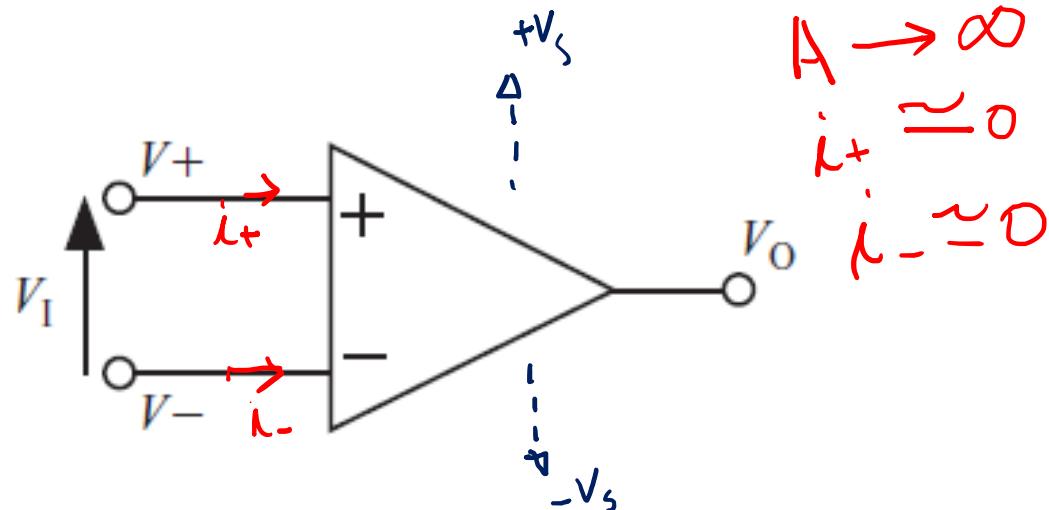


Figure 6.3 The conventional representation of an opamp

schematic

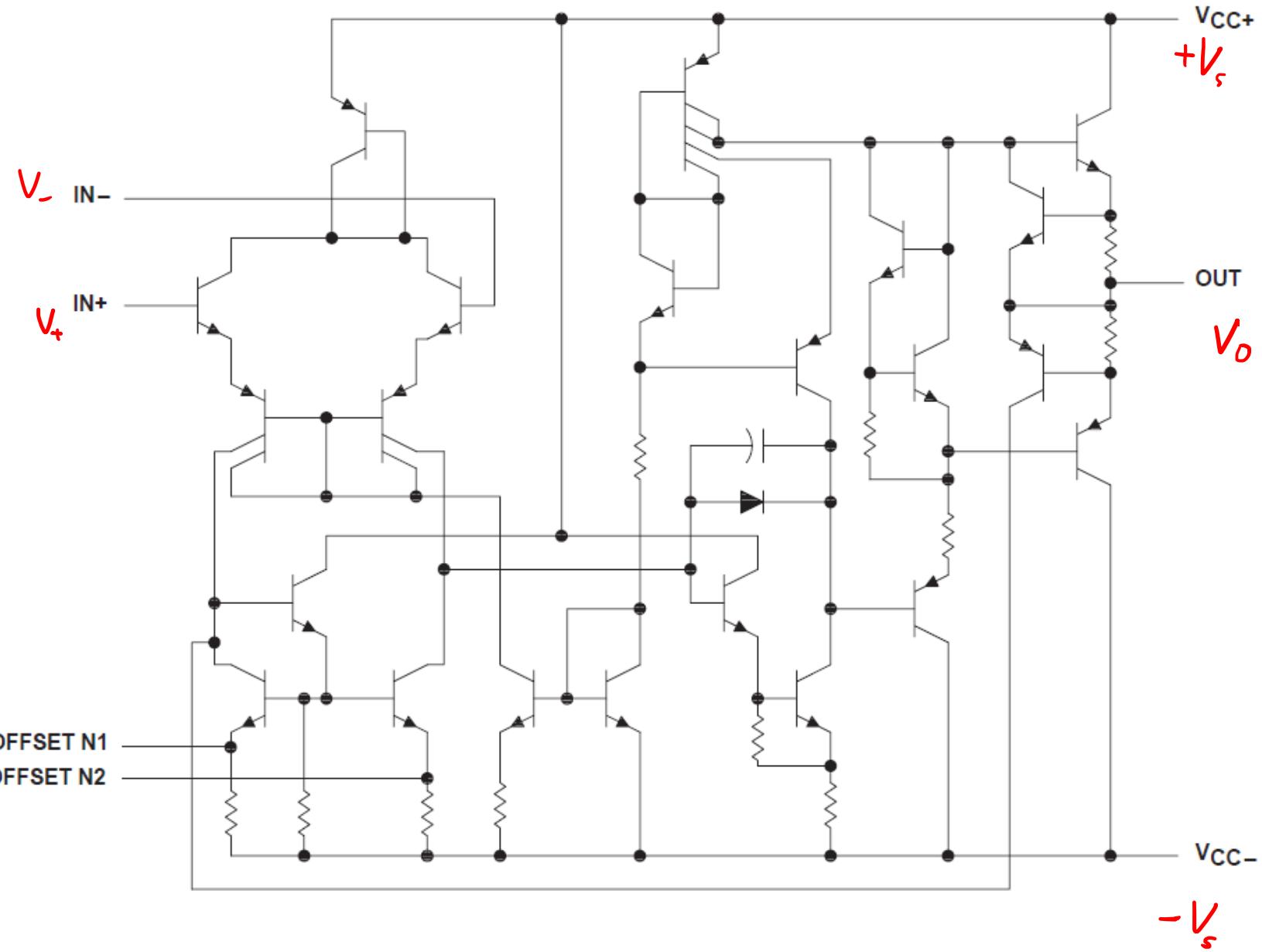

TI μ A741

<http://www.ti.com/product/ua741>

Data Sheet
諸元規格

electrical characteristics at specified free-air temperature, $V_{CC\pm} = \pm 15 V$ (unless otherwise noted)

PARAMETER	TEST CONDITIONS	T_A^\dagger	$\mu A741C$			$\mu A741I, \mu A741M$			UNIT
			MIN	TYP	MAX	MIN	TYP	MAX	
V_{IO} Input offset voltage	$V_O = 0$	25°C		1	6		1	5	mV
		Full range			7.5			6	
$\Delta V_{IO(\text{adj})}$ Offset voltage adjust range	$V_O = 0$	25°C		± 15			± 15		mV
I_{IO} Input offset current	$V_O = 0$	25°C		20	200		20	200	nA
		Full range			300			500	
I_{IB} Input bias current	$V_O = 0$	25°C		80	500		80	500	nA
		Full range			800			1500	
V_{ICR} Common-mode input voltage range		25°C	± 12	± 13		± 12	± 13		V
		Full range	± 12			± 12			
V_{OM} Maximum peak output voltage swing	$R_L = 10 k\Omega$	25°C	± 12	± 14		± 12	± 14		V
	$R_L \geq 10 k\Omega$	Full range	± 12			± 12			
	$R_L = 2 k\Omega$	25°C	± 10	± 13		± 10	± 13		
	$R_L \geq 2 k\Omega$	Full range	± 10			± 10			
AVD Large-signal differential voltage amplification	$R_L \geq 2 k\Omega$	25°C	20	200		50	200		V/mV
	$V_O = \pm 10 V$	Full range	15			25			
r_i Input resistance		25°C	0.3	2		0.3	2		MΩ
r_o Output resistance	$V_O = 0$, See Note 5	25°C		75			75		Ω
C_i Input capacitance		25°C		1.4			1.4		pF
CMRR Common-mode rejection ratio	$V_{IC} = V_{ICR\min}$	25°C	70	90		70	90		dB
		Full range	70			70			
k_{SVS} Supply voltage sensitivity ($\Delta V_{IO}/\Delta V_{CC}$)	$V_{CC} = \pm 9 V \text{ to } \pm 15 V$	25°C	30	150		30	150		$\mu V/V$
		Full range		150			150		
I_{OS} Short-circuit output current		25°C	± 25	± 40		± 25	± 40		mA
I_{CC} Supply current	$V_O = 0$, No load	25°C	1.7	2.8		1.7	2.8		mA
		Full range		3.3			3.3		
P_D Total power dissipation	$V_O = 0$, No load	25°C	50	85		50	85		mW
		Full range		100			100		

Gain

1000 V/V

Comparator circuits

$$\text{Δ } V_I = V_+ - V_-$$

88

Ideal opamp $A \rightarrow \infty$

$$V_O = \begin{cases} +V_s & \text{if } V_I > 0 \\ -V_s & \text{if } V_I < 0 \end{cases} \quad \begin{matrix} \leftarrow V_+ > V_- \\ \leftarrow V_+ < V_- \end{matrix}$$

$$V_O \begin{cases} +V_s & \text{if } V_I > 0 \\ -V_s & \text{if } V_I < 0 \end{cases}$$

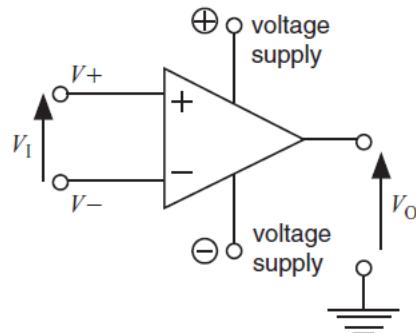


Figure 6.1 The voltages associated with an operational amplifier

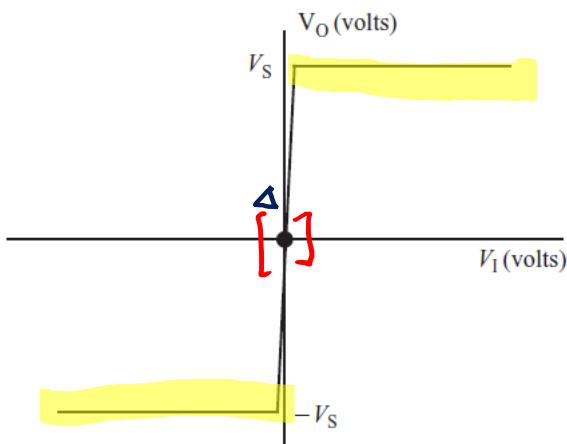


Figure 6.2 The form of the relation between the input V_I and output V_O voltages of an opamp

Comparator

$$V_o = \begin{cases} +V_s & \text{if } V_{IN} > V_{REF} \\ -V_s & \text{if } V_{IN} < V_{REF} \end{cases}$$

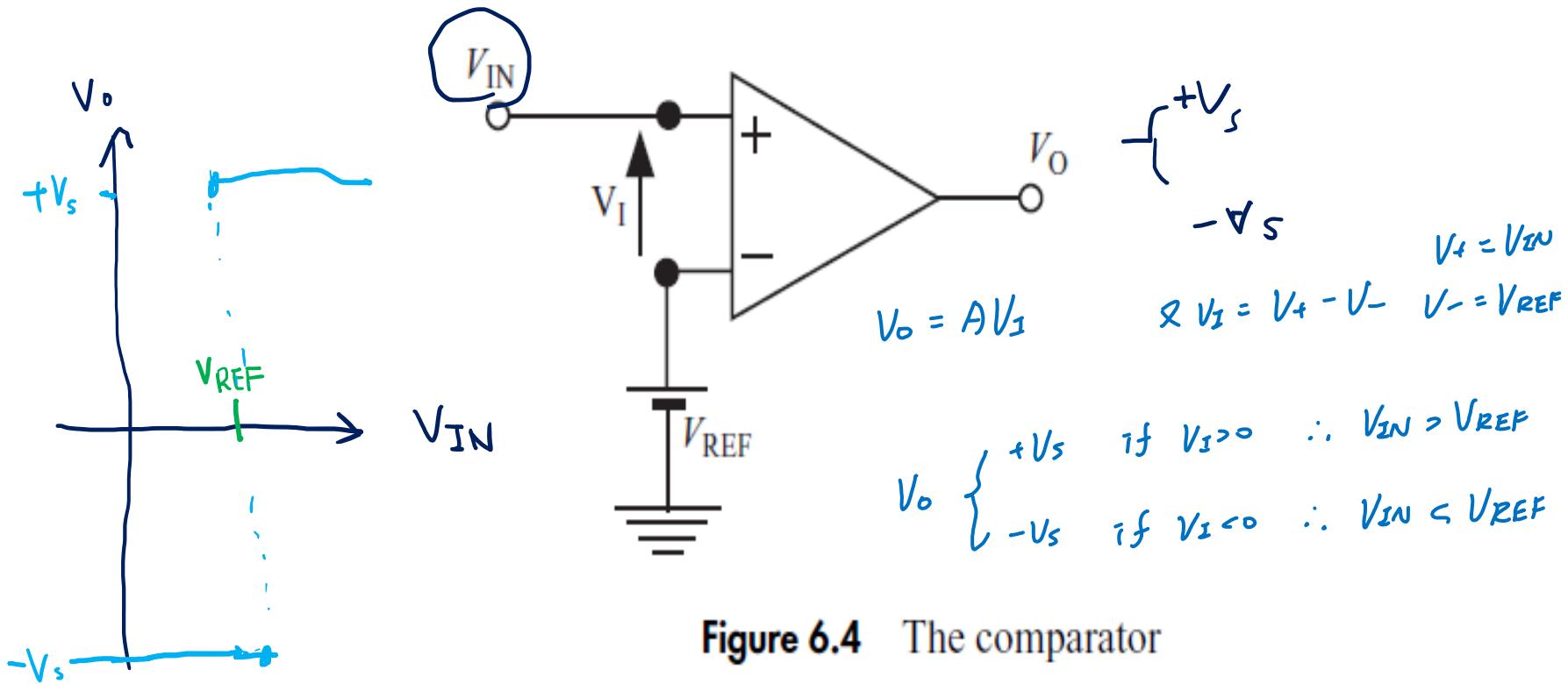


Figure 6.4 The comparator

類比

數位

01001011

v

Analog-to-digital (A-D) conversion

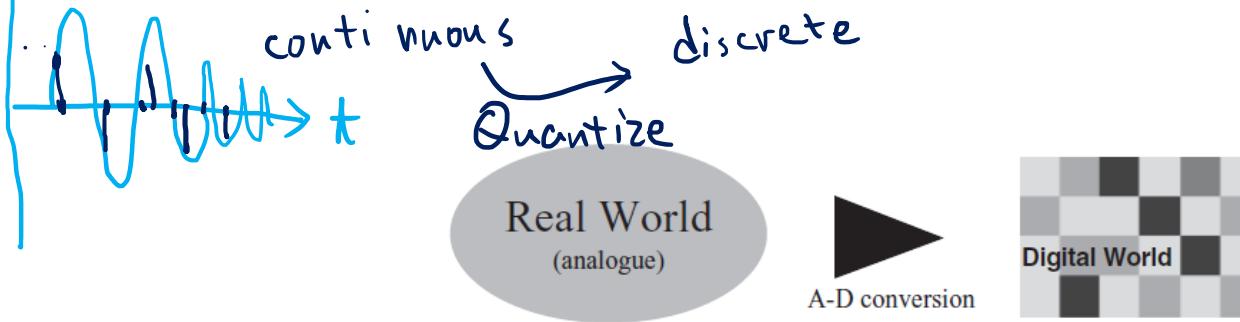


Figure 6.5 It is often convenient for analogue information to be transformed to digital form for easier processing



Analog-to-digital (A-D) conversion

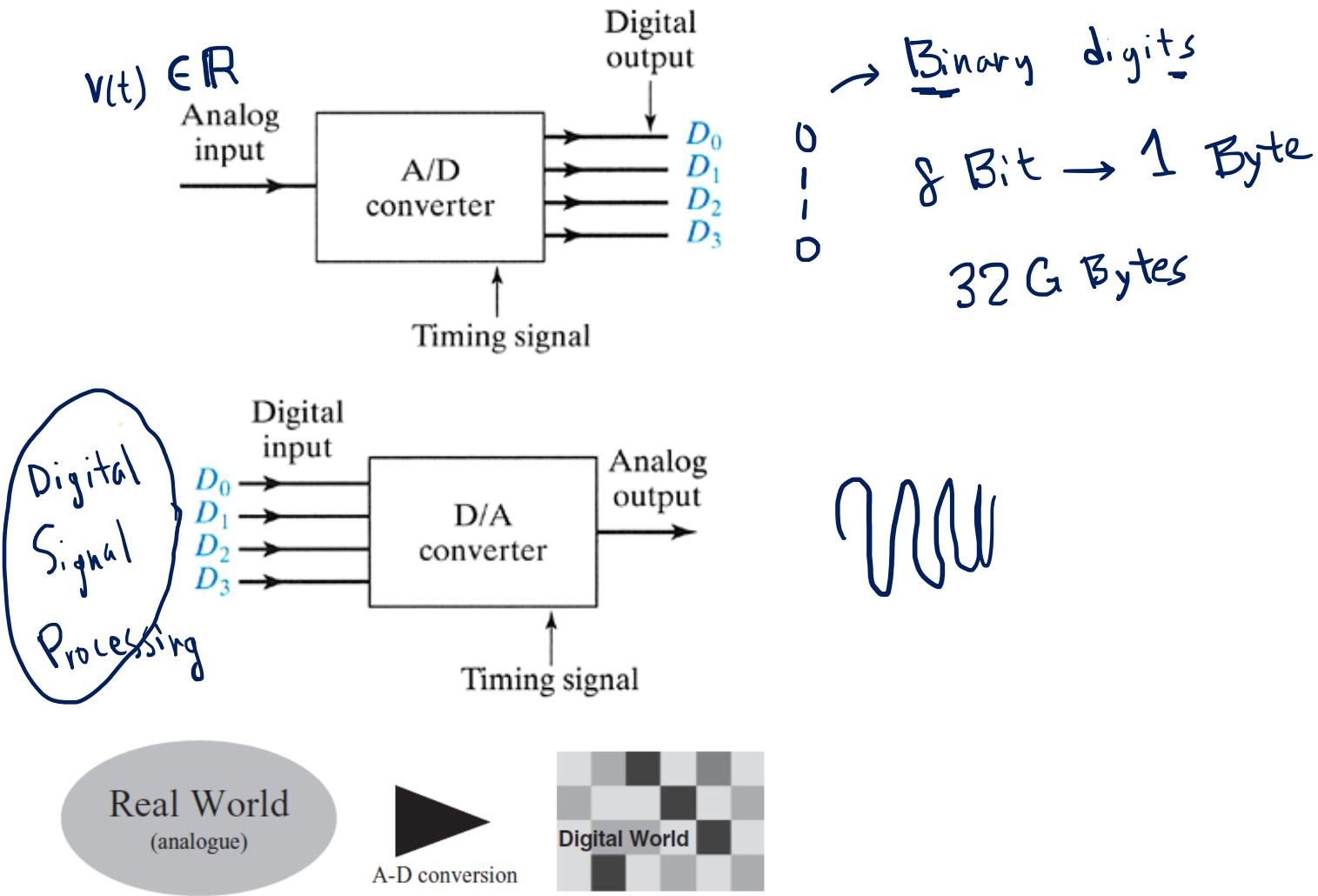


Figure 6.5 It is often convenient for analogue information to be transformed to digital form for easier processing

Analog-to-digital (A-D) conversion

	V_{IN}	V_A	V_B	V_C	A	B	C
(0, 1)		$-V_s$	$-V_s$	$-V_s$	0	0	0
(1, 2)		$+V_s$	$-V_s$	$-V_s$	1	0	0
(2, 3)		$+V_s$	$+V_s$	$-V_s$	1	1	0
(3, 4)		$+V_s$	$+V_s$	$+V_s$	1	1	1

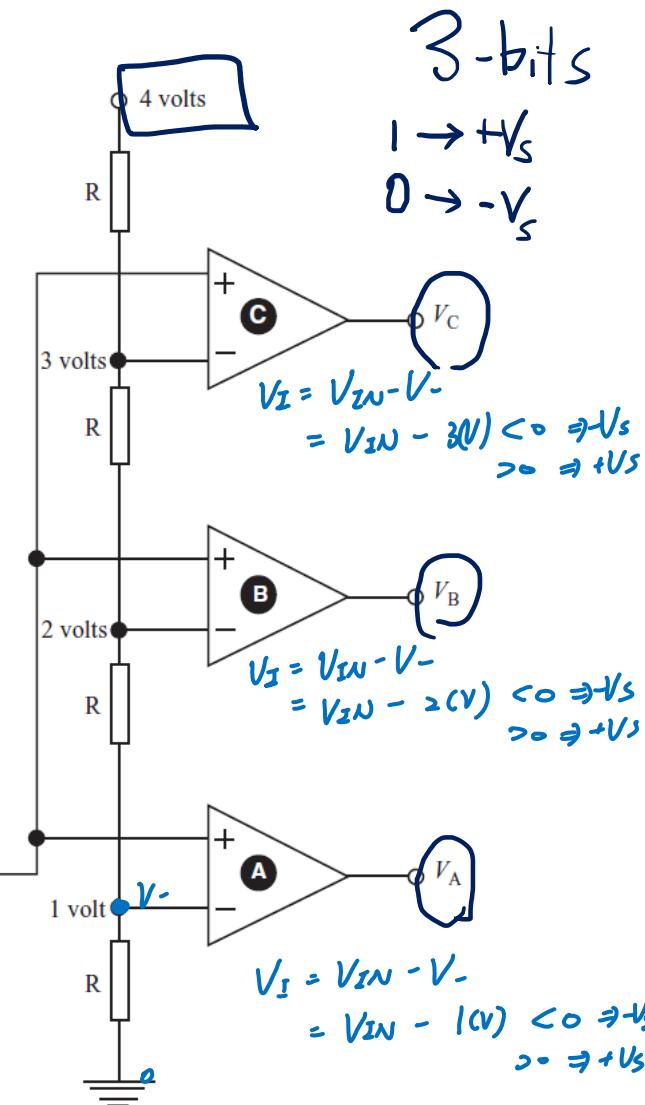
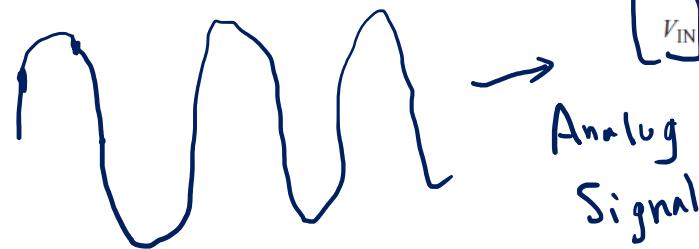


Figure 6.6 A very simple A-D converter based on the use of comparators

Ideal Opamp

Assumption

Gain $A \rightarrow \infty$

Input $i_+ = 0$

Current $i_- = 0$

就視為沒有中間

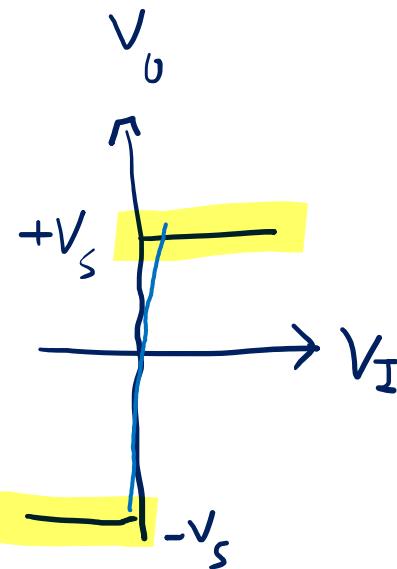
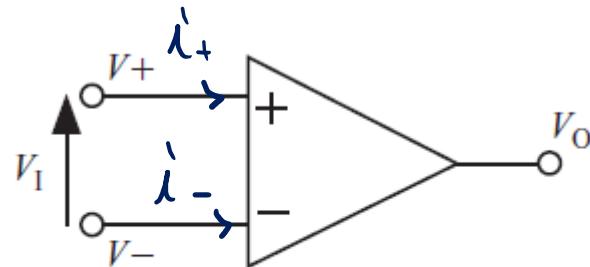


Figure 6.3 The conventional representation of an opamp

Comparator

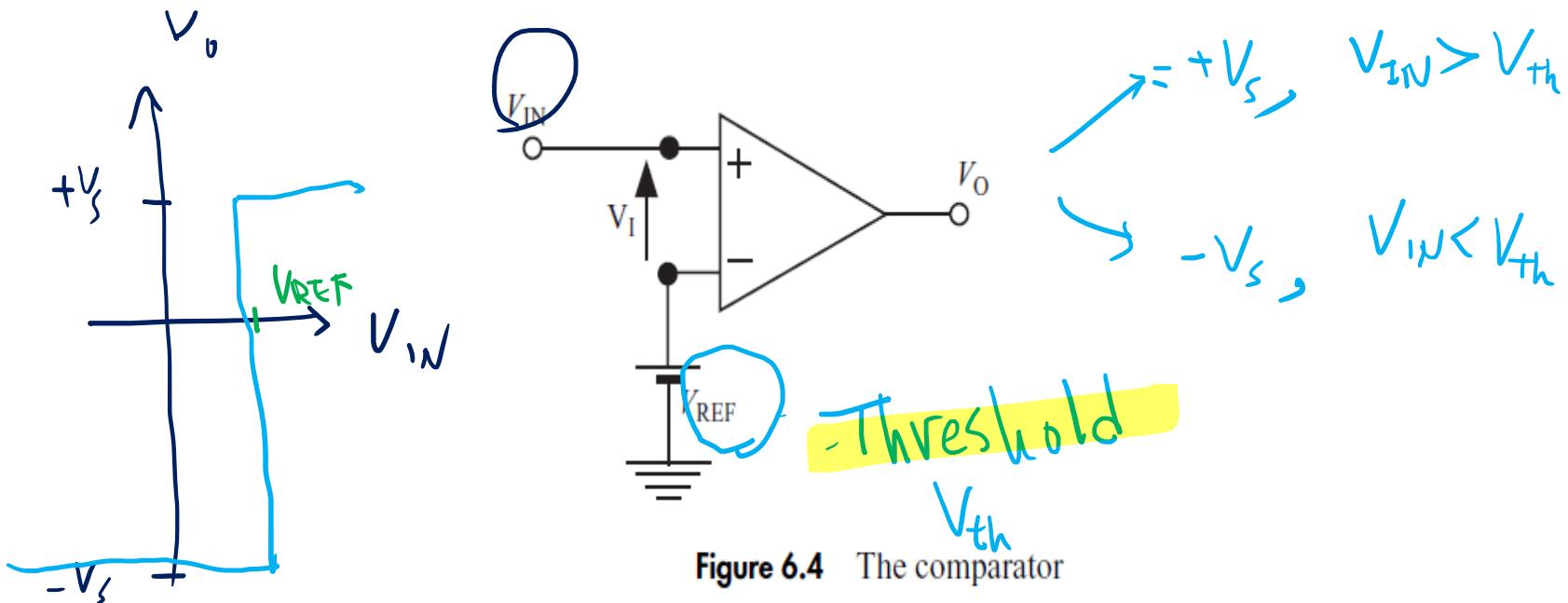


Figure 6.4 The comparator

Schmitt trigger

$$V_I = V_+ - V_- = V_+ - V_{IN}$$

- $V_{IN} > V_+ \Rightarrow V_I < 0 \Rightarrow V_o = -V_s$
- $V_{IN} < V_+ \Rightarrow V_I > 0 \Rightarrow V_o = +V_s$

$$V_o = \begin{cases} +V_s & \text{if } V_I > 0 \\ -V_s & \text{if } V_I < 0 \end{cases}$$

$\frac{3}{5}V_o > V_{IN} \Rightarrow \frac{3}{5}V_s > V_{IN}$

$\frac{3}{5}V_o < V_{IN} \Rightarrow \frac{3}{5}(-V_s) < V_{IN}$


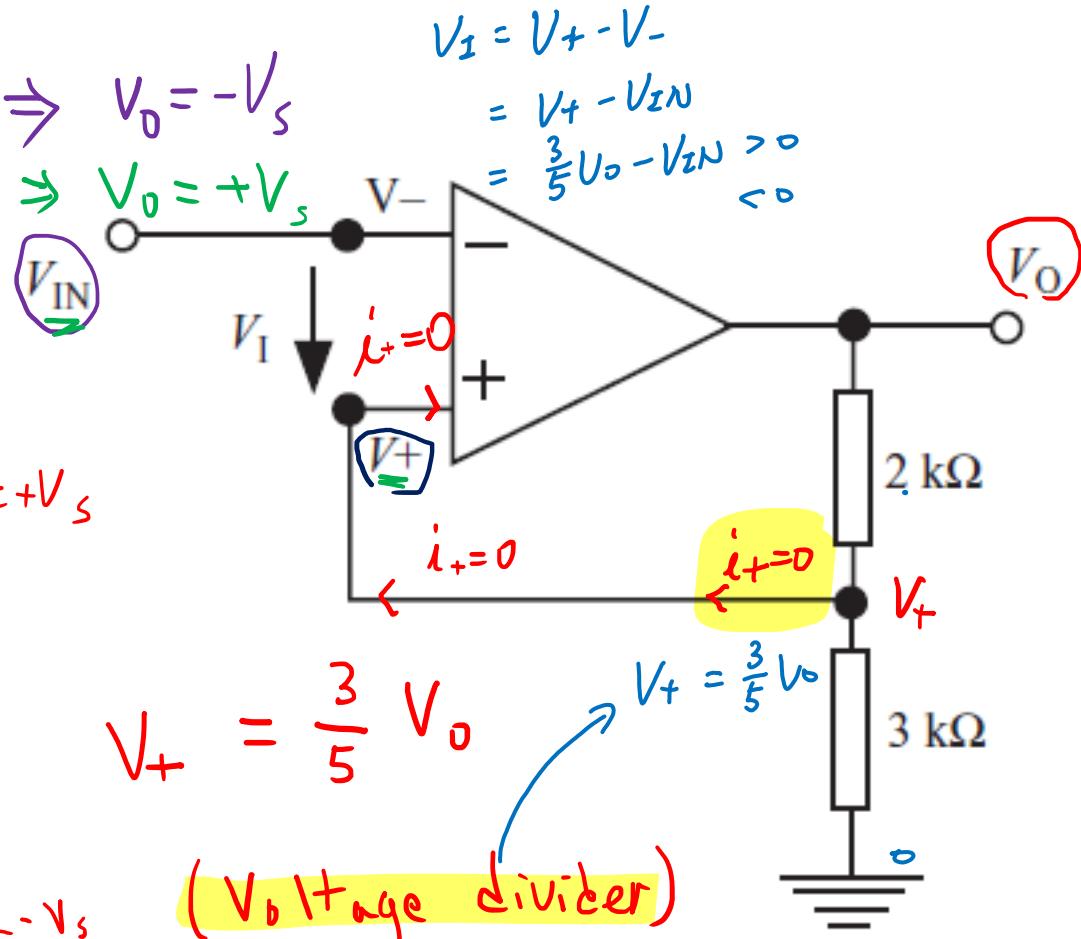


Figure 6.7 The Schmitt trigger

Schmitt trigger

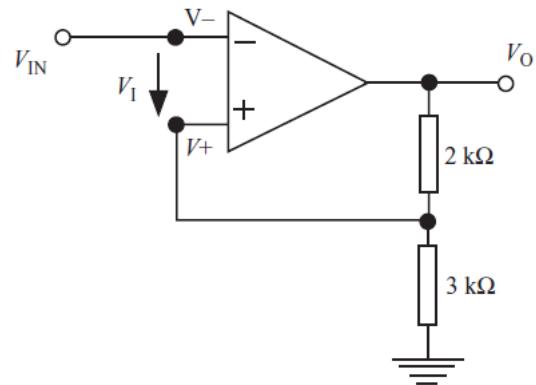

$$V_O \begin{cases} +V_s & \text{if } V_I > 0 \\ -V_s & \text{if } V_I < 0 \end{cases}$$

$\frac{3}{5}V_o > V_{IN} \Rightarrow \frac{3}{5}V_s > V_{IN}$

$\frac{3}{5}V_o < V_{IN} \Rightarrow \frac{3}{5}(-V_s) < V_{IN}$

$-6V < V_{IN}$

$$\begin{aligned} V_I &= V_+ - V_- \\ &= V_t - V_{IN} \\ &= \frac{3}{5}V_o - V_{IN} > 0 \\ &< 0 \end{aligned}$$

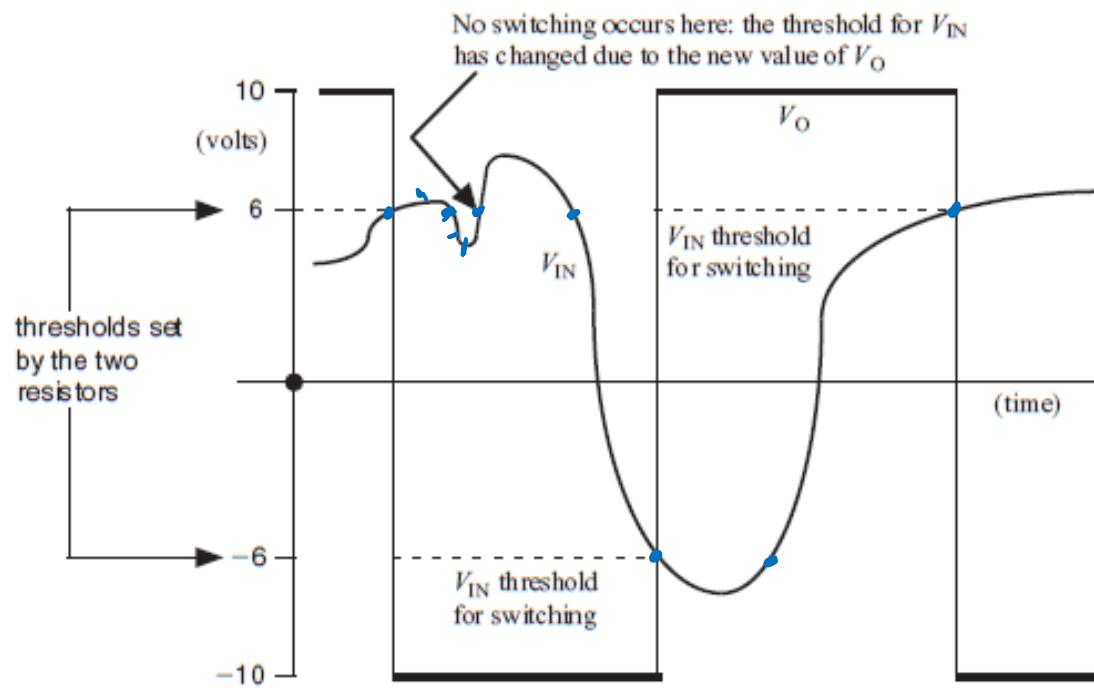


Figure 6.7 The Schmitt trigger

Figure 6.10 The behaviour of the Schmitt trigger for an arbitrary input voltage waveform. Take particular note of the fact that the threshold for V_{IN} changes when the output voltage changes

Another trigger circuit

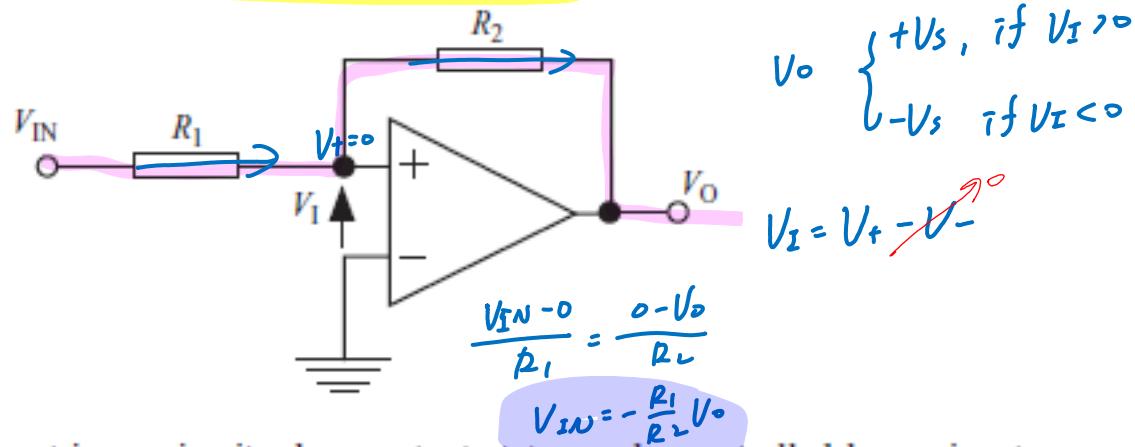


Figure 6.11 Another trigger circuit whose output state can be controlled by an input voltage

If $V_O = -10V$
threshold $V_{IN} = +10 \frac{R_1}{R_2}$

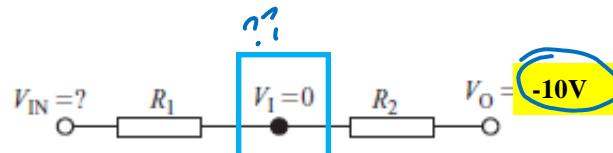


Figure 6.12 Circuit relevant to the calculation of the value of V_{IN} needed to cause the output voltage of the circuit of Figure 6.11 to change from $+10$ to -10 V

LAB 1. Schmitt trigger simulation

1. Build a Schmitt trigger on the simulator online.
2. For the opamp, set ‘Max Output’ to 10 and ‘Min Output’ to -10.
3. Add an ‘AC Voltage Source (1-terminal)’ as V_{IN} , and set Waveform as ‘Triangle’.
4. Add an ‘Analog Output’ as V_O .
5. Change R_1 , R_2 , and Max Voltage V_{IN} according to your student ID (details in the next slide).
6. Show input and output waveforms.
7. Save the work by ‘Export as Text’, and submit the text file to ‘Moodle’.

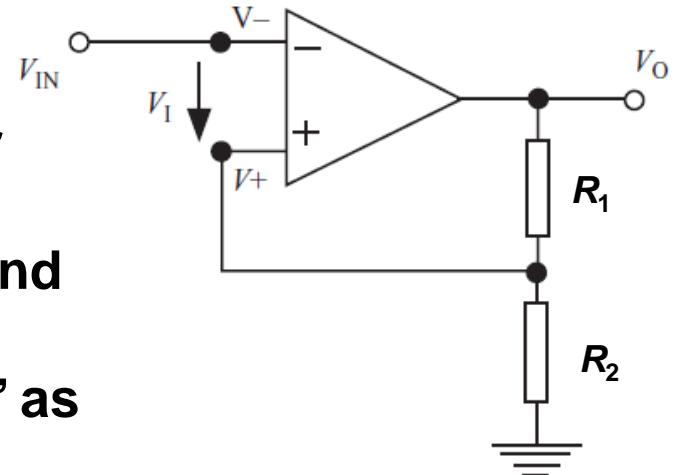


Figure 6.7 The Schmitt trigger

[Simulator Link 1](#)

[Simulator Link 2](#)

LAB 1. Schmitt trigger simulation (cont.)

Setting of parameters:

Suppose your student ID is
 $E(NN) 0 (BBB) (CC)$

For AC Voltage Source V_{IN}

- If NN=14, set Max Voltage=7.5
- If NN=34, set Max Voltage=8
- If NN=44, set Max Voltage=8.5
- If NN=54, set Max Voltage=9
- If NN=64, set Max Voltage=9.5
- If NN=84, set Max Voltage=10

Set resistors

$R1 = B.BB \text{ K}$

$R2 = 2.CC \text{ K}$

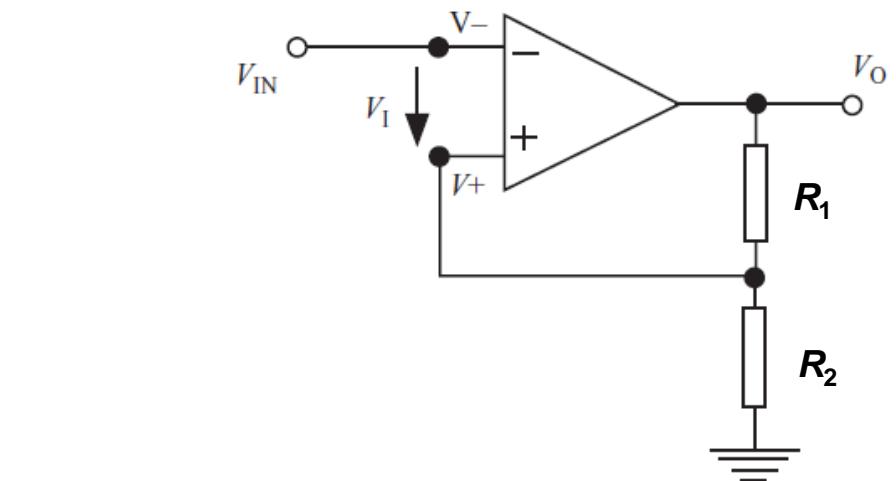


Figure 6.7 The Schmitt trigger

Example: ID E34048154
NN=34, Max Voltage=8
 $R1=4.81 \text{ K}$
 $R2=2.54 \text{ K}$

Example 6.2

A voltage V_{IN} having the triangular waveform (but with nonzero average value) shown in Figure 6.13(a) is applied to the input of the circuit shown in Figure 6.13(b). Find the resulting waveform of the voltage V_O . The output voltage V_O of the opamp limits at ± 8 V.

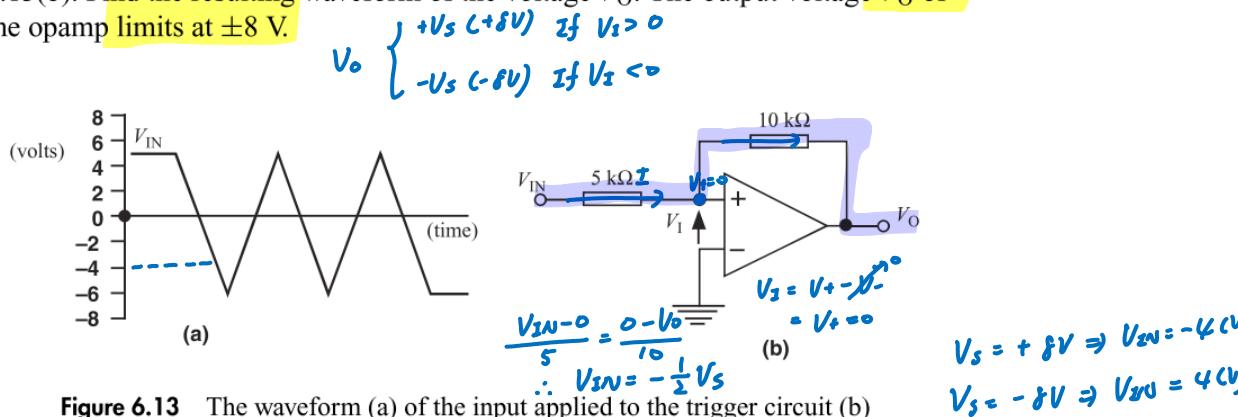


Figure 6.13 The waveform (a) of the input applied to the trigger circuit (b)

The subcircuit shown in Figure 6.14 controls the threshold values of V_{IN} . With V_O at 8 V it is easily seen that for V_1 to be zero the value of V_{IN} must be -4 V. Similarly, when V_O is at -8 V, V_{IN} would have to rise above +4 V in order to make V_1 , and hence V_O , positive. The resulting waveform of V_O is shown in Figure 6.15, with the threshold values of V_{IN} shown as dashed lines.

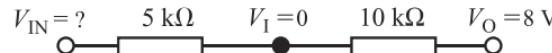


Figure 6.14 Model allowing calculation of the threshold voltages for the circuit of Figure 6.13(a)

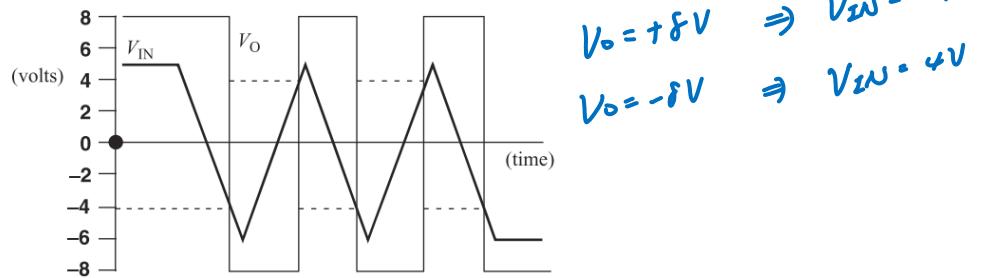


Figure 6.15 The waveform of the output voltage of the trigger circuit of Figure 6.13(a)