

# 電子電工學

## Lecture 12



# Recap: Phasors for AC

$$e^{j\theta} = \cos\theta + j \sin\theta$$

$$F_i = j = e^{j\frac{\pi}{2}}$$

Time-variant  
signal  
 $v(t), i(t)$

$\rightarrow$  Complex  $\rightarrow$  Phasor  
 $V, I$  Diagram

Differential  
Eq.

$$V(t) = \frac{1}{j\omega C} I(t)$$

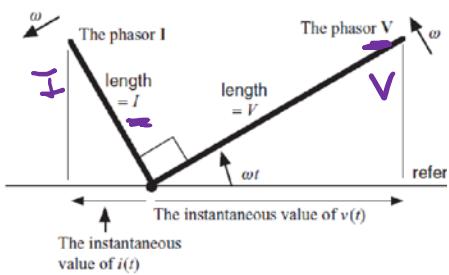
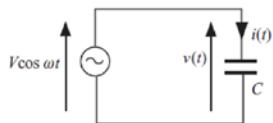


Figure 9.12 A phasor diagram showing phasors representing capacitive voltage and current. Note that the phasors rotate at an angular frequency  $\omega$  and it is the reference axis that determines the actual scalar instantaneous values  $v(t)$  and  $i(t)$ .

$$V(t) = j\omega L I(t)$$

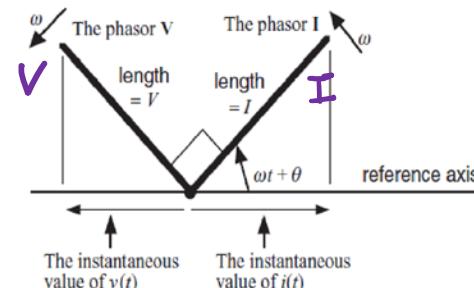
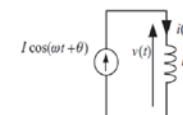


Figure 9.13 A phasor diagram showing phasors representing inductor voltage and current.

$$V(t) = R I(t)$$

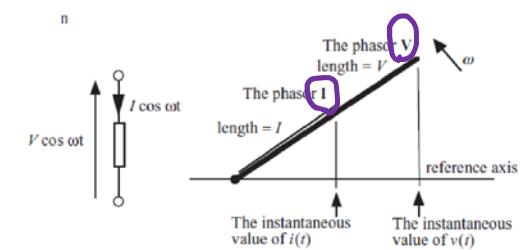



Figure 9.14 The phasors representing the sinusoidal voltage and current of a resistor are in phase. The current phasor has been offset slightly for clarity.

KCL, KVL


## Recap: Phasor addition

$$v_1(t) = V_1 \cos(\omega t + \theta_1)$$
$$+ v_2(t) = V_2 \cos(\omega t + \theta_2)$$
$$\underline{v(t)} = \underline{v_1(t) + v_2(t)} \neq \underline{(V_1 + V_2) \cos(\omega t + \theta)}$$


$$V_1 = V_1 e^{j(\omega t + \theta_1)}$$
$$V_2 = V_2 e^{j(\omega t + \theta_2)}$$
$$\underline{V} = \underline{V_1 + V_2}$$

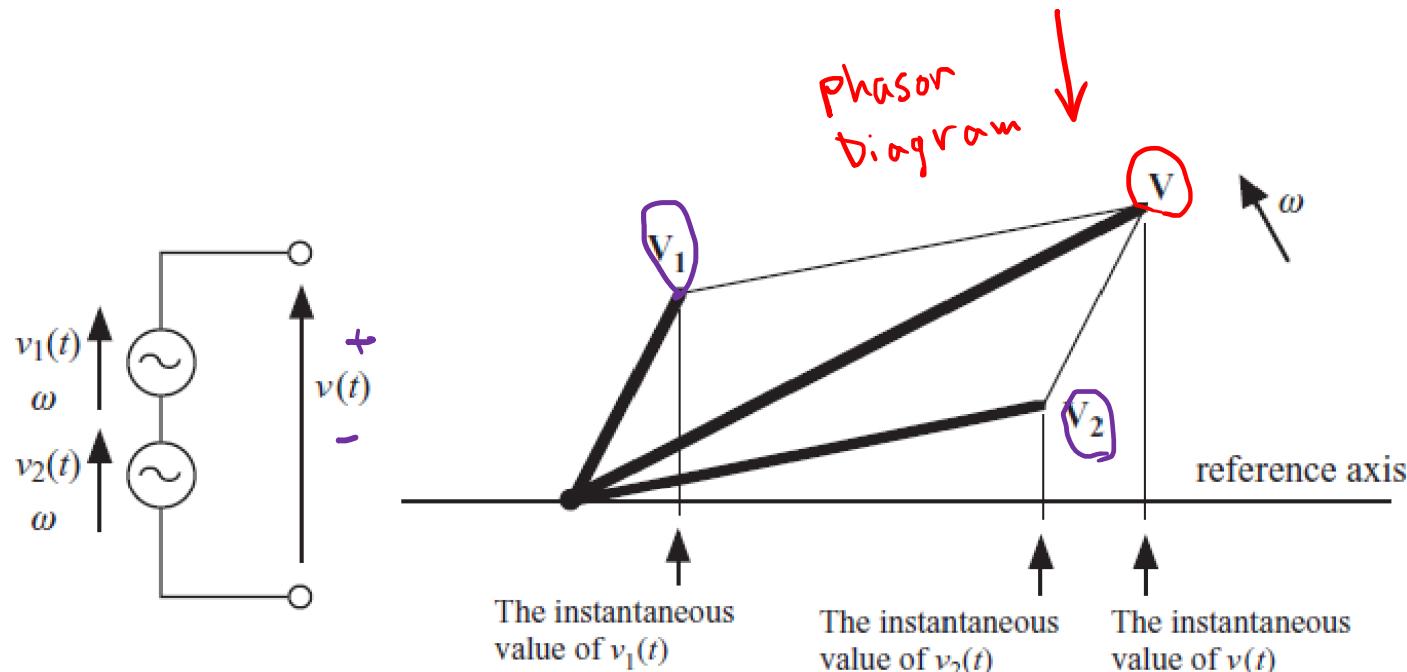


**Figure 9.15** A Phasor diagram showing that the phasor addition of voltages obeys KVL. Hairlines are used to indicate construction

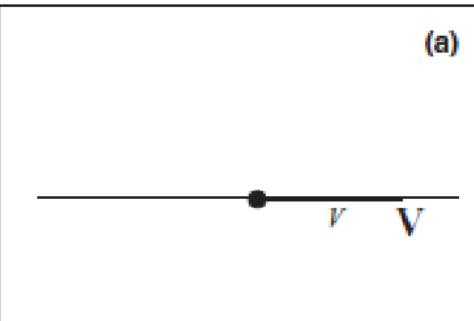


Ohm's Law

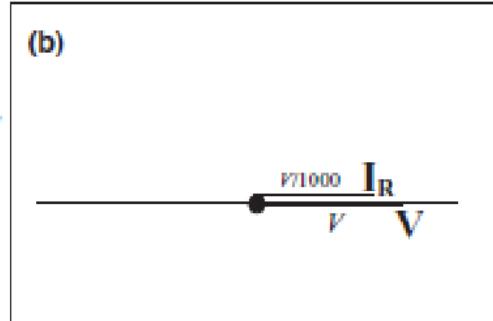


Capacitor relation

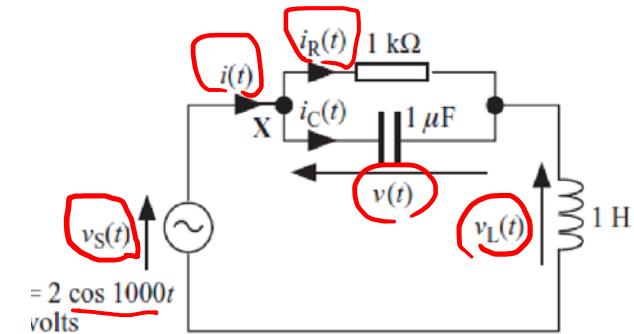

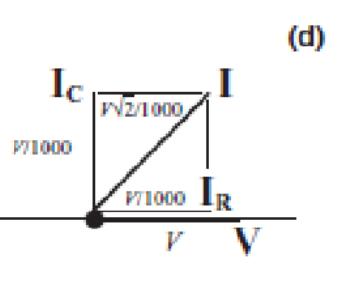
- 6 The circuit whose phasor diagram is to be constructed




KCL

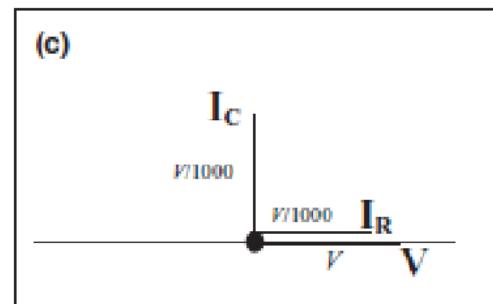

Inductor relation

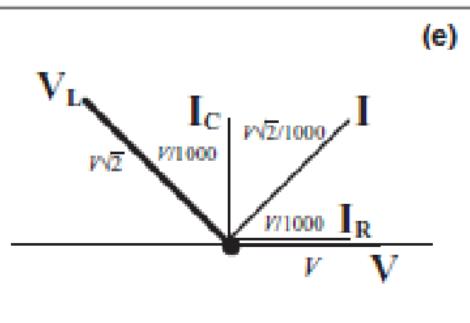

KVL

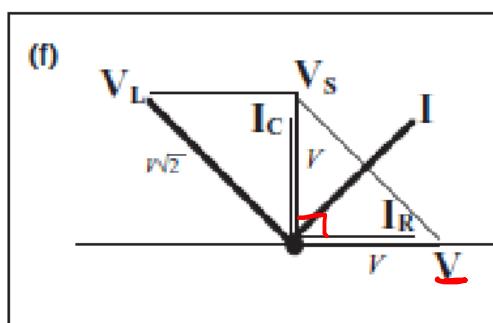

$$V_s \rightarrow 2 \cos(\omega_0 t) \quad V \rightarrow 2 \cos(\omega_0 t - 90^\circ)$$

$$V_L \rightarrow V_L(t)$$

$$I \rightarrow i(t)$$

$$I_c \rightarrow i_c(t)$$

$$I_L \rightarrow i_L(t)$$

## Constructing a phasor diagram

Figure 9.17 Steps in the construction of a phasor diagram for the circuit of Figure 9.16. Where possible phasor lengths have been indicated beside the phasor. Some overlapping phasors have been offset slightly for clarity. Hairlines are included to indicate constructions

# Resonance

R - L - C Parallel

Time domain  $v(t) \rightarrow i(t)$


Involves 2<sup>nd</sup> order ODE

$$I_R(t) = \frac{V}{R}$$

$$I_L(t) = \frac{V}{j\omega L}$$



$$I_C(t) = (j\omega C)V$$

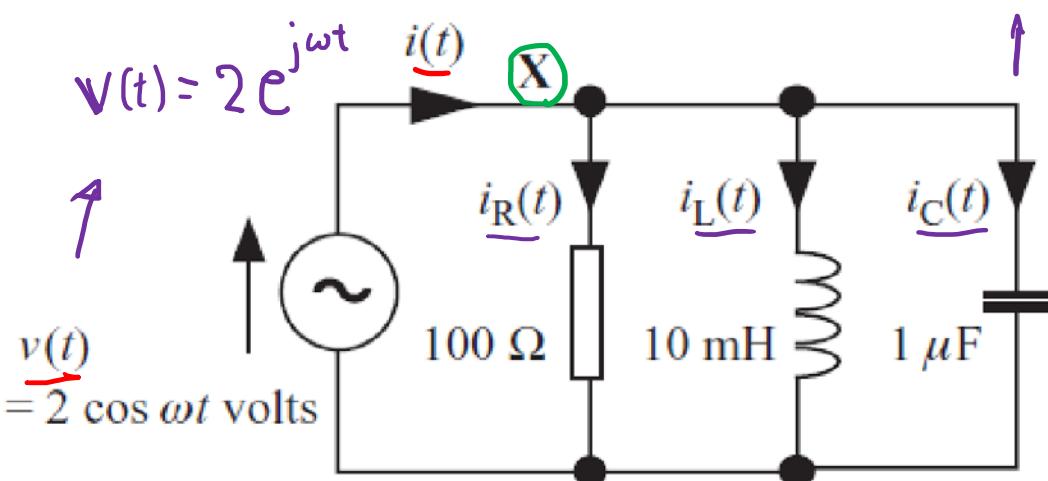

KCL @

$$\begin{aligned} I(t) &= I_R(t) + I_L(t) + I_C(t) \\ &= V(t) \cdot \left[ \frac{1}{R} + \frac{1}{j\omega L} + j\omega C \right] \end{aligned}$$

Figure 9.18 A resonant circuit

# Resonance


Cartesian  
Coord.  
( $a, b$ )  $\rightarrow$  ( $r, \theta$ )

For  $\omega = 10000\sqrt{2} \approx 14142$  rad/s

$$\begin{aligned}
 I(t) &= V(t) \cdot \left[ \frac{1}{R} + \frac{1}{j\omega L} + j\omega C \right] \\
 &= V(t) \cdot \left[ \frac{1}{R} + j[-\frac{1}{\omega L} + \omega C] \right] \\
 &= \underline{V(t)} \cdot \left[ \frac{1}{100} + j \left[ -\frac{1}{100 \cdot 5} + \frac{\sqrt{2}}{100} \right] \right] \\
 &\approx \underline{24.5} e^{j(\omega t + 35^\circ)} \text{ (mA)}
 \end{aligned}$$

$a + bj = re^{j\theta}$   
 $\downarrow$   
 $\approx 12.25 e^{j35^\circ}$

**Table 9.1** Relevant to the analysis of the circuit of Figure 9.18

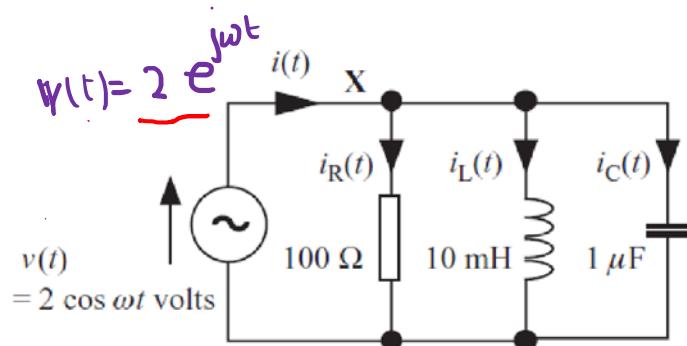

**Figure 9.18** A resonant circuit

$\omega$ radians/sec	$\omega C$ siemens	$1/\omega C$ ohms	$\omega L$ ohms
104	10 <sup>-2</sup>	100	100
$10^4 \sqrt{2}$	$\sqrt{2}/100$	$100/\sqrt{2}$	$100\sqrt{2}$


The values of  $V/I$  for the inductor and capacitor of Figure 9.18 for two values of  $\omega$ , the radian frequency of the current source

# Resonance

For  $\omega = 10000 \text{ rad/s}$

$$\begin{aligned} I(t) &= V^{(+) } \left[ \frac{1}{R} + j \left( -\frac{1}{\omega L} + \omega C \right) \right] \\ &= V(t) \cdot \frac{1}{R} \\ &= 20 e^{j\omega t} \text{ (mA)} \end{aligned}$$


**Table 9.1** Relevant to the analysis of the circuit of Figure 9.18

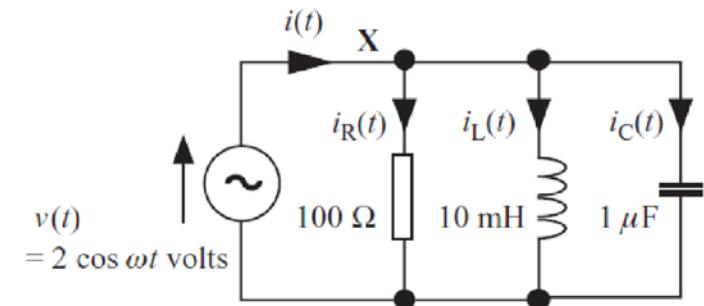

**Figure 9.18** A resonant circuit

$\omega$ radians/sec	$\omega C$ siemens	$1/\omega C$ ohms	$\omega L$ ohms
$10^4$	$10^{-2}$	100	100
$10^4 \sqrt{2}$	$\sqrt{2}/100$	$100/\sqrt{2}$	$100\sqrt{2}$





The values of  $V/I$  for the inductor and capacitor of Figure 9.18 for two values of  $\omega$ , the radian frequency of the current source

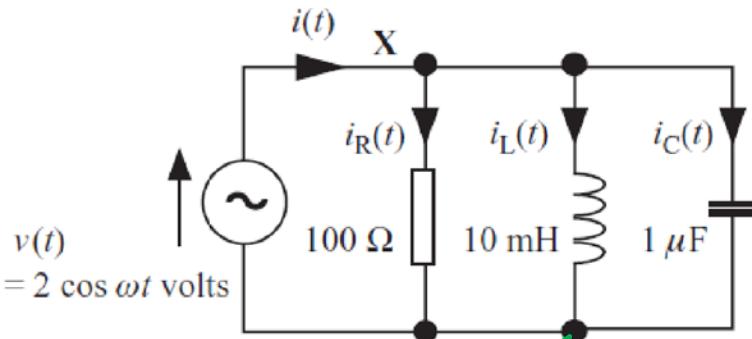


**Figure 9.18** A resonant circuit

$$I_L = \frac{V}{j\omega L}$$

$$I_C = (j\omega C)V$$

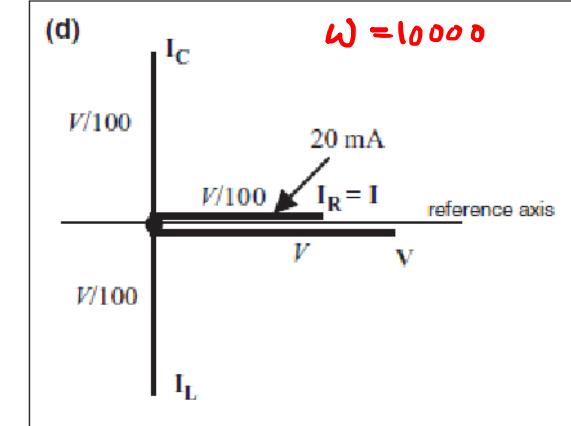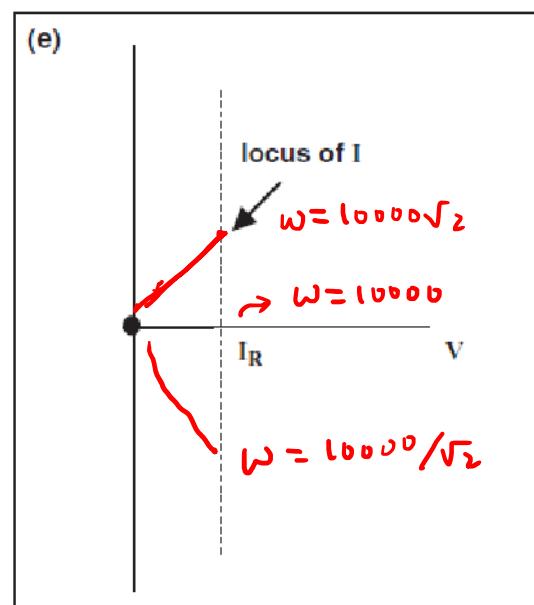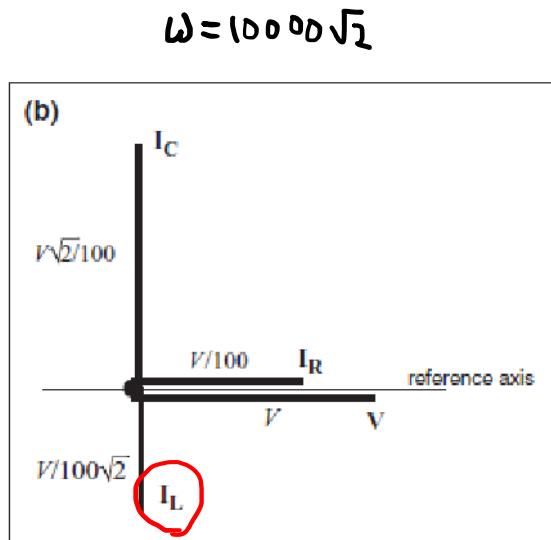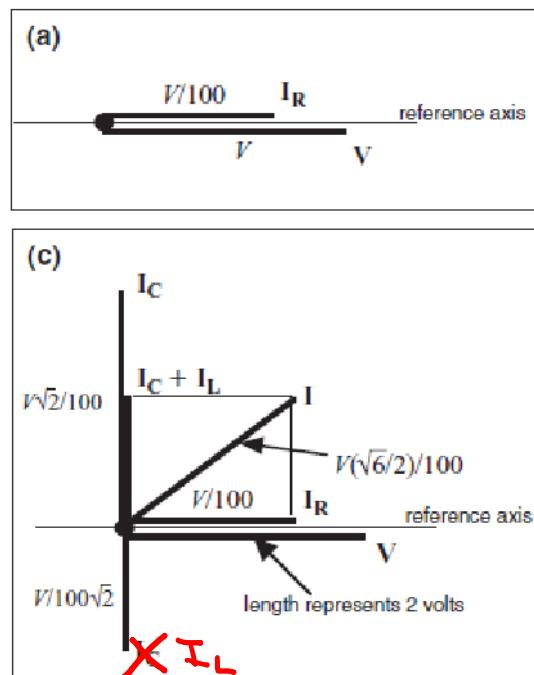

**Figure 9.19** Construction of phasor diagrams for the circuit of Figure 9.18. Some overlapping phasors have been offset for clarity

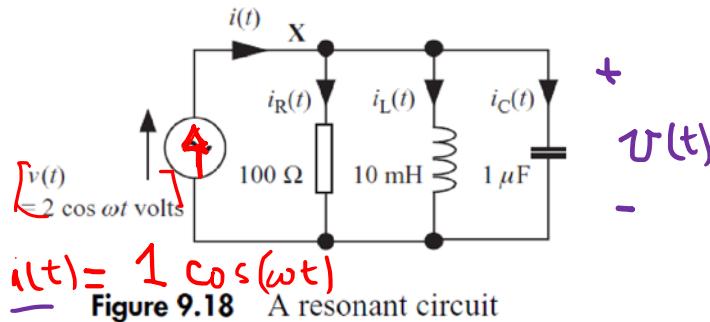

Replace source with 1 mA current source  
( $\omega$  adjustable)

$$I(t) = 1 e^{j\omega t}$$

$$V(t) = I(t) \cdot [100 \Omega \parallel j\omega L \parallel \frac{1}{j\omega C}]$$

$$= I(t) \cdot \left[ \frac{1}{\frac{1}{100} + j(\omega C - \frac{1}{\omega L})} \right]$$


$$\text{Amplitude } |V(t)| = |I(t)| \left| \frac{1}{\frac{1}{100} + j(\omega C - \frac{1}{\omega L})} \right|$$

Figure 9.20 Pertinent to the circuit of Figure 9.18 in which the sinusoidal voltage source is replaced by a sinusoidal current source of 1 mA amplitude. The sketch shows the variation of the amplitude of the voltage  $v(t)$  as the source frequency  $\omega$  varies

Resonance @  $\omega C - \frac{1}{\omega L} = 0$

$$\Rightarrow \omega^2 = \frac{1}{LC}$$
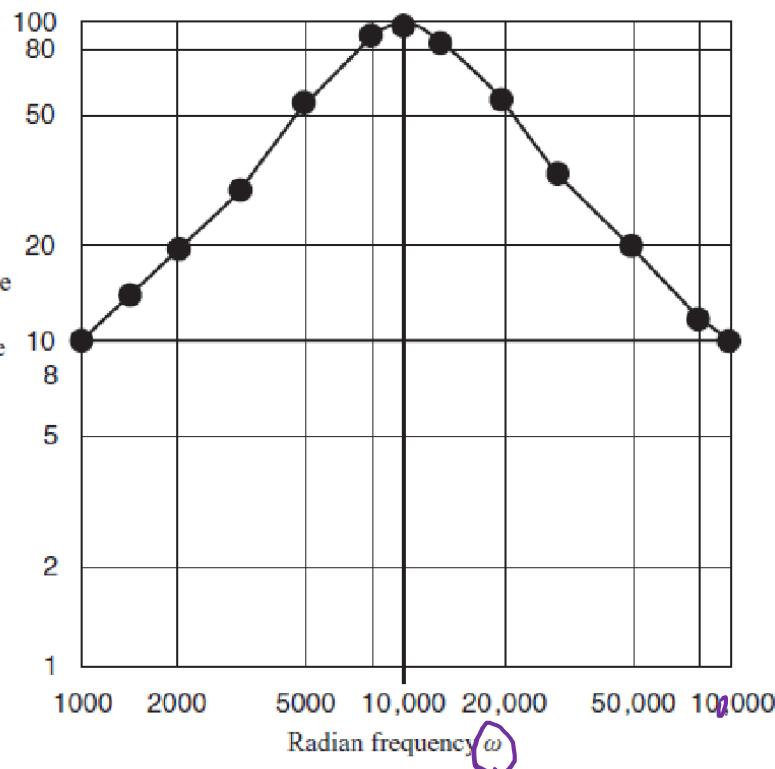
$$\Rightarrow \omega = \frac{1}{\sqrt{LC}} = 10^4 \text{ (rad/s)}$$



# Chapter 10

# AC circuit example

Sinusoidal wave source

$$v_s(t) = V \cos(\omega t + \theta)$$

↓      ↓      ↓  
Amplitude      Freq.      Phase


$$v_s(t) = v_R(t) + v_L(t)$$

{ ODE: 1<sup>st</sup>, 2<sup>nd</sup>  
Trigonometric Identity

Simplify



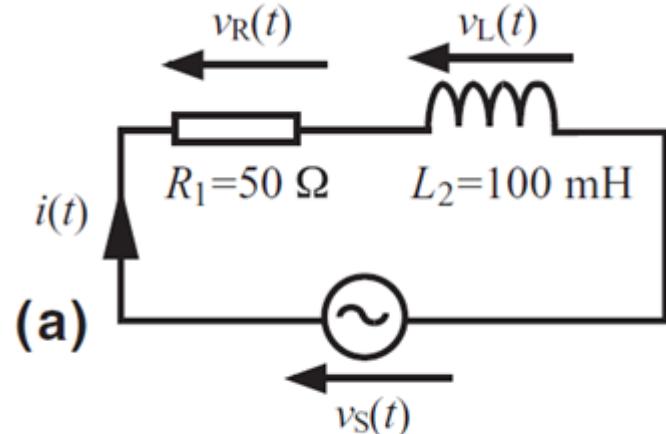Phasor diagram  
Complex voltage  
current  
Laplace transf.  
Fourier transf.



(40 V peak-to-peak amplitude, 500 rad/s)

$$20 \cos(500t)$$

# Euler's Theorem

i current

$$e^{j\theta} = \cos \theta + j \sin \theta \quad j = \sqrt{-1}$$

$$|e^{j\theta}| = \sqrt{\cos^2 \theta + \sin^2 \theta} \\ = 1$$

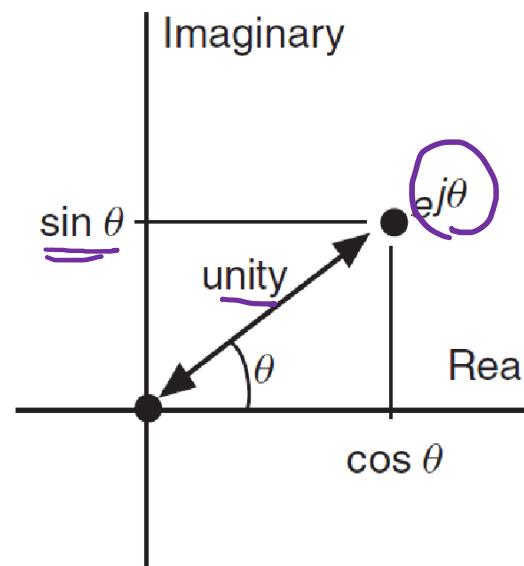


Figure 10.1 Representation of  $e^{j\theta}$  in the complex plane

## Recall: Complex numbers

- Conjugate

共軛

$$\overline{a + jb} = a - jb$$
$$\overline{e^{j\theta}} = \cos\theta - j\sin\theta$$
$$= e^{-j\theta}$$

- Absolute value

$$|a + jb| = \sqrt{a^2 + b^2} = \sqrt{(a + jb)(a - jb)}$$

$$e^{j\theta} = \sqrt{e^{j\theta} e^{-j\theta}} = 1$$


$$e^{j\theta} = \cos\theta + j\sin\theta$$

$$\theta = \omega t$$

$$\rightarrow e^{j\omega t} = \cos\omega t + j\sin\omega t$$

$$|e^{j\omega t}| = 1 \quad \forall t$$

$$r e^{j\omega t}$$

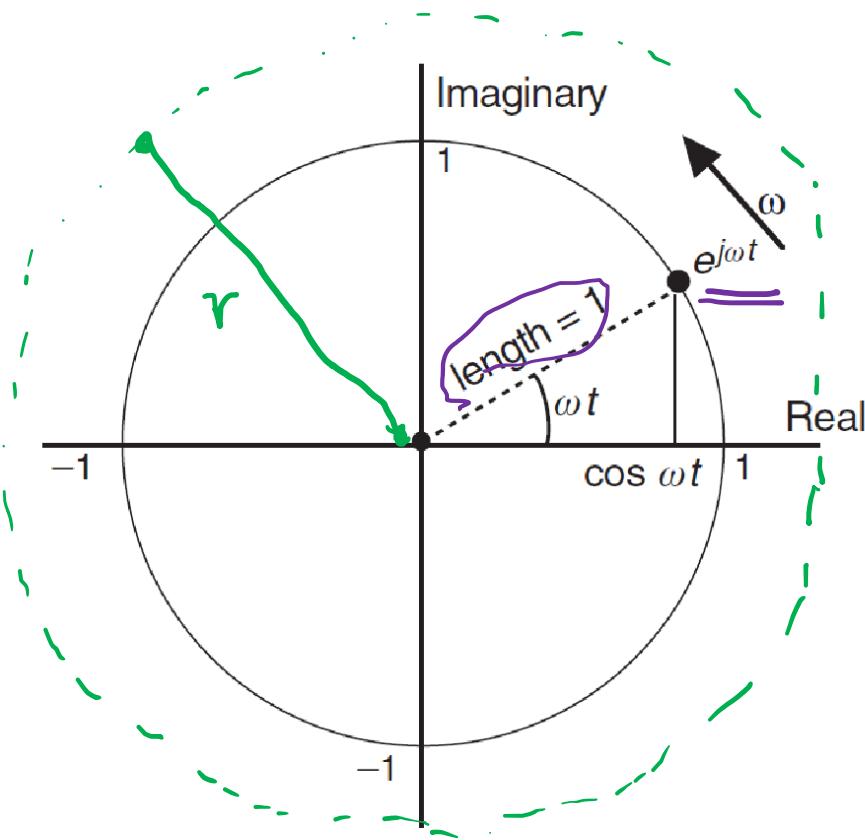

**Figure 10.2** Properties of  $e^{j\omega t}$  in the complex plane

$$a + jb = r e^{j\theta}$$

$$= r \cos \theta + j r \sin \theta$$

$$\begin{cases} a = r \cos \theta \\ b = r \sin \theta \end{cases}$$

$$\rightarrow \begin{cases} r = \sqrt{a^2 + b^2} \\ \theta = \arctan(\frac{b}{a}) \end{cases}$$

Polar coordinate

$$(a, b) \rightarrow (r, \theta)$$

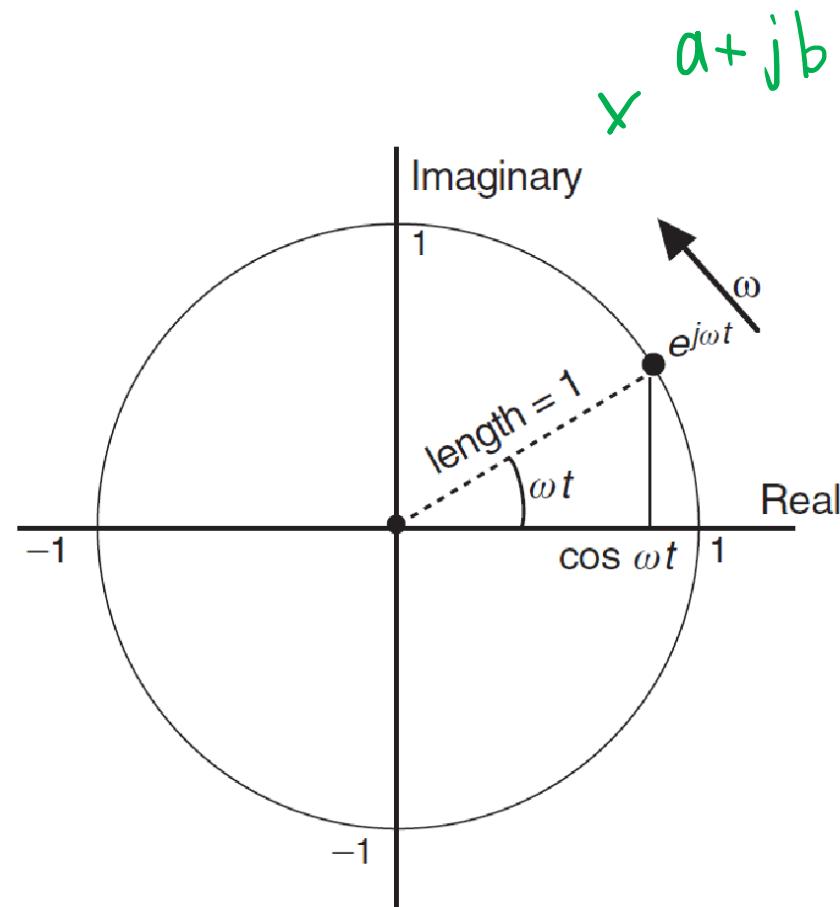


Figure 10.2 Properties of  $e^{j\omega t}$  in the complex plane

# Complex Voltages and Currents

Real-domain  
Signal  
(Actual)

$$v(t) = V \cos(\omega t + \theta)$$

$$= \operatorname{Re} [ V e^{j(\omega t + \theta)} ]$$

↑  
complex-domain

$$= \operatorname{Re} [ \underline{V} e^{j\theta} e^{j\omega t} ]$$

$$= \operatorname{Re} [ \underline{\underline{V}} e^{j\omega t} ]$$

↓

(Time-indep.) Complex-Voltage

Real-domain  
current

Complex current

(phasor)

$$i(t) = \operatorname{Re} [ \underline{\underline{I}} e^{j\omega t} ]$$

# AC circuit example

$$0.1 \frac{di(t)}{dt} + 50 i(t) = 20 \cos(500t)$$

↓

*Complex domain* [


$$0.1 \frac{d}{dt} [\underline{I} e^{j\omega t}] + 50 \underline{I} e^{j\omega t} = 20 e^{j500t} \quad (\omega = 500)$$

$$\Rightarrow 0.1 \underline{I} \cdot j\omega \cdot [e^{j\omega t}] + 50 \underline{I} [e^{j\omega t}] = 20 [e^{j\omega t}]$$

$$\Rightarrow (0.1 \cdot j\omega + 50) \underline{I} = 20$$

Time-independent Eq.

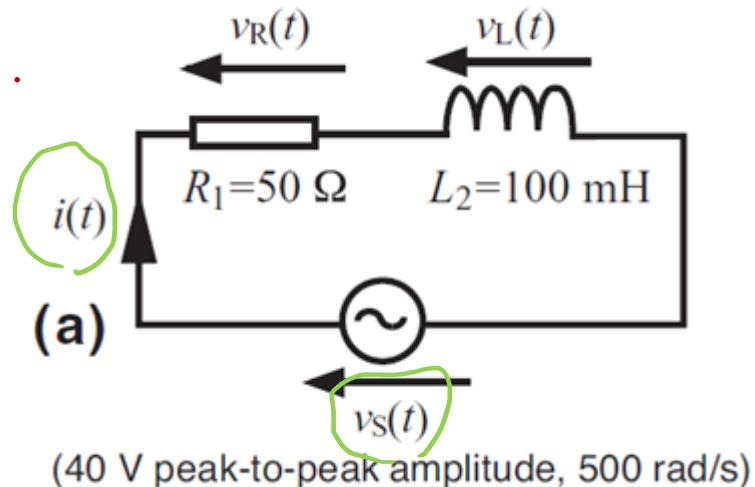
$$\Rightarrow \underline{I} = \frac{20}{50 + j \cdot 0.1 \cdot 500} = \frac{20}{50 + j50}$$


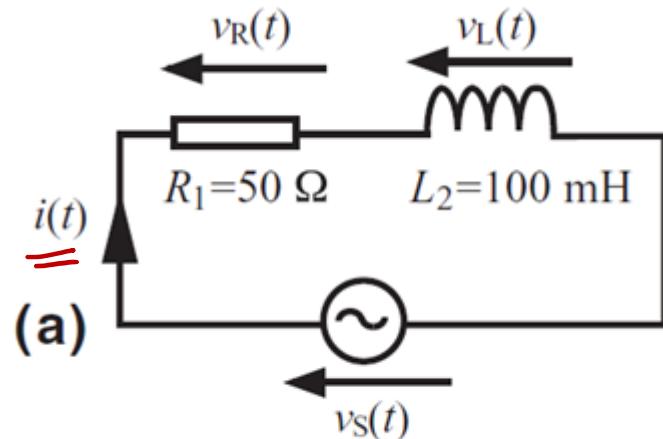
# AC circuit example

$$\begin{aligned}
 \text{II} &= \frac{20}{50 + j50} \\
 &= \frac{20}{50} \cdot \frac{1}{1+j} \cdot \frac{1-j}{1-j} \\
 &= \frac{20}{50} \cdot \frac{1}{2} (1-j) \\
 &= 0.2 (1-j)
 \end{aligned}$$


$$\begin{aligned}
 i(t) &= \operatorname{Re} \left[ \text{II} e^{j\omega t} \right] \\
 &= \operatorname{Re} \left[ 0.2(1-j) e^{j\omega t} \right]
 \end{aligned}$$



(40 V peak-to-peak amplitude, 500 rad/s)
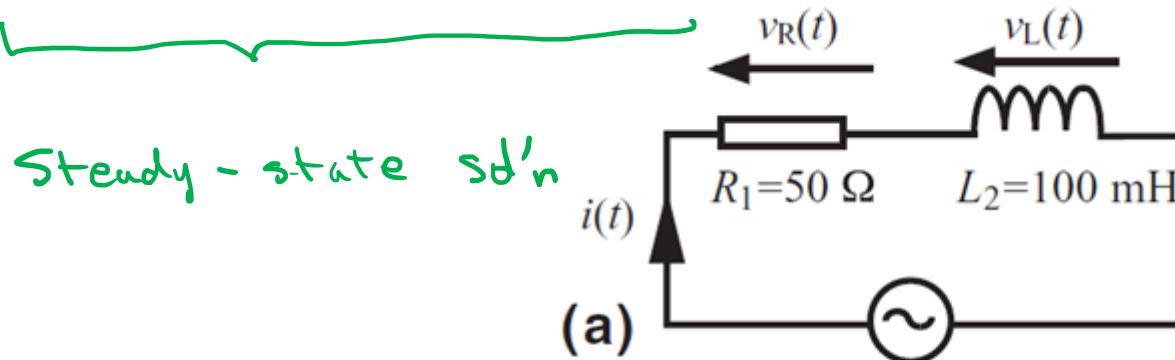
# AC circuit example

$$\begin{aligned} i(t) &= \operatorname{Re} \left[ 0.2 (1-j) e^{j\omega t} \right] \\ &= \operatorname{Re} \left[ 0.2 (1-j) (\cos \omega t + j \sin \omega t) \right] \\ &= 0.2 \times [\cos \omega t + \sin \omega t] \\ &= 0.2 [\cos 500t + \sin 500t] \end{aligned}$$



Steady-state sol'n

(40 V peak-to-peak amplitude, 500 rad/s)

# Component relations (capacitor)

$$i(t) = C \frac{d v(t)}{dt}$$

Complex  
Domain

$$\begin{aligned} \mathcal{I}[e^{j\omega t}] &= C \frac{d}{dt} [V e^{j\omega t}] \\ &= C V j\omega [e^{j\omega t}] \end{aligned}$$


$$\Rightarrow \mathcal{I} = (j\omega C)V$$

$$V = \left[ \frac{1}{j\omega C} \right] \mathcal{I}$$

Generalized  
Ohm's Law

Impedance

$$Z_C = \frac{1}{j\omega C}$$

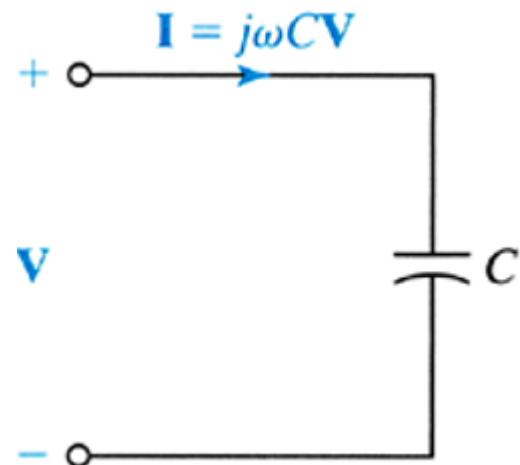

# Component relations (inductor)


Complex domain

$$v(t) = L \frac{di(t)}{dt}$$
$$V e^{j\omega t} = L \frac{d}{dt} [ I e^{j\omega t} ]$$

...

$$V = (j\omega L) I$$

↓  
Impedance of Inductor

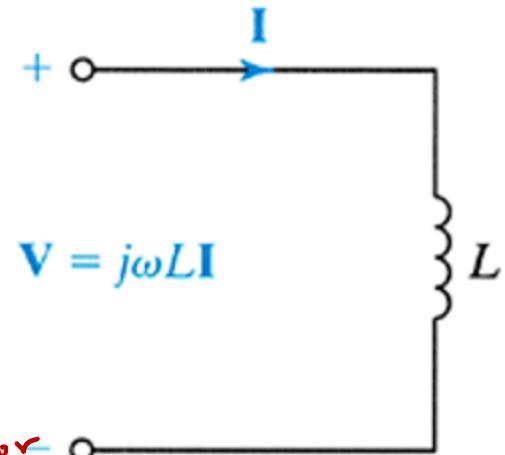

$$Z_L = j\omega L$$

# Component relations (resistor)


$$v(t) = R \cdot i(t)$$

Complex domain

$$V = RI$$

Impedance of Resistor

$$Z_r = R$$

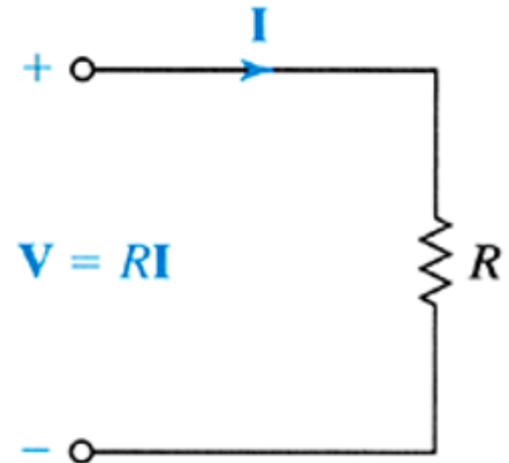

# Interconnection KCL

$$\text{At Node A: } i_1(t) + i_2(t) + i_3(t) = 0$$


Complex

$$R_c \left[ \mathbb{I}_1 e^{j\omega t} \right] + R_c \left[ \mathbb{I}_2 e^{j\omega t} \right] + R_c \left[ \mathbb{I}_3 e^{j\omega t} \right] = 0$$

$$R_c \left[ (\mathbb{I}_1 + \mathbb{I}_2 + \mathbb{I}_3) e^{j\omega t} \right] = 0$$

$$\Rightarrow \mathbb{I}_1 + \mathbb{I}_2 + \mathbb{I}_3 = 0$$

KCL holds in complex domain.

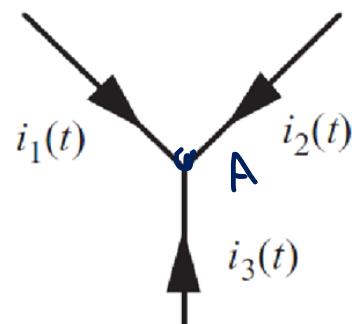


**Figure 10.3** Relevant to the discussion of whether KCL is valid for complex currents

# Complex KVL

$$\text{L. o. p : } v_1(t) + v_2(t) + v_3(t) = 0$$

Complex  $\downarrow$        $v_1 + v_2 + v_3 = 0$

doma. "

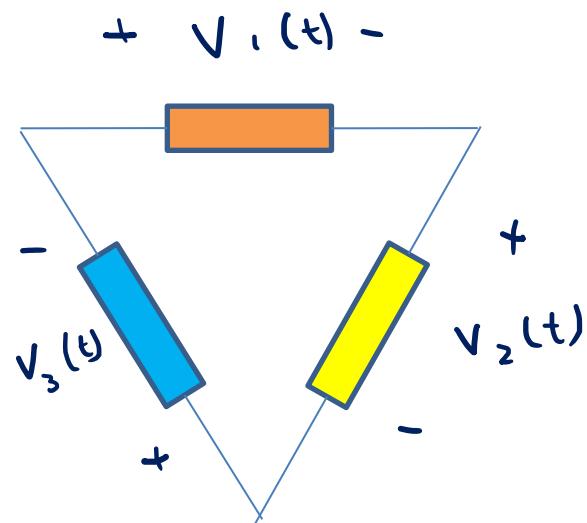

# AC Circuit Analysis

NODAL ANALYSIS  
 SUPERPOSITION  
 THEVENIN's EQUIV CKT  
 NORTON EQUIV CKT

**Table 10.1** Similarities between the component relations and connection constraints in DC circuits and AC circuits

DC Currents and voltages	AC Currents and voltages
<p><i>representation</i></p> <p><i>relation</i></p> $\sum_{\text{node}} I = 0$ $\sum_{\text{loop}} V = 0$ $V = RI$	<p><i>Connections</i></p> <p><i>at node</i></p> $\sum_{\text{node}} \mathbf{I} = 0$ <p><i>around loop</i></p> $\sum_{\text{loop}} \mathbf{V} = 0$ <p><i>Components</i></p> <p><i>resistor</i></p> $\mathbf{V} = R \mathbf{I}$ <p><i>capacitor</i></p> $\mathbf{I} = j\omega C \mathbf{V}$ <p><i>inductor</i></p> $\mathbf{V} = j\omega L \mathbf{I}$ <p><i>voltage source</i></p> $\mathbf{V} = \text{constant}$ <p><i>current source</i></p> $\mathbf{I} = \text{constant}$

KCL  
KVL

Generalized  
Ohm's Law  
(Impedance)

fixed  $\omega$

# Example 10.1

Given  $V_s(t)$

Find  $i(t)$

ODE → Solution


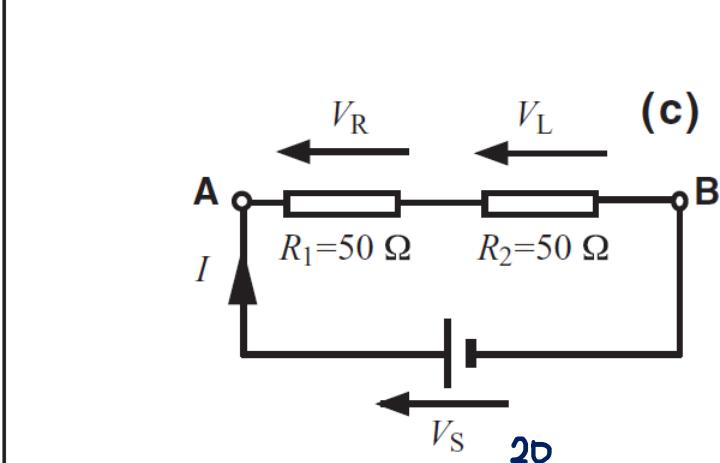
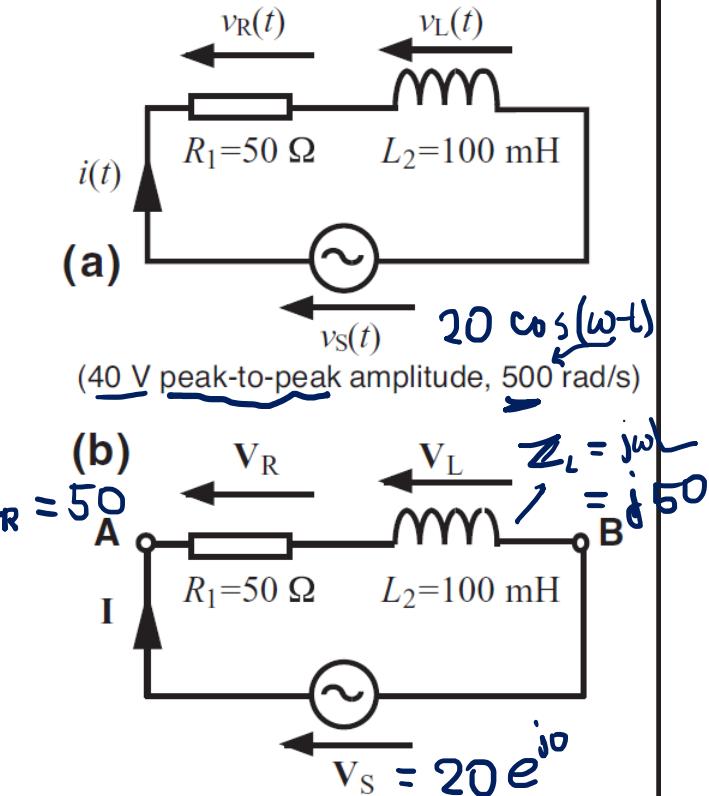
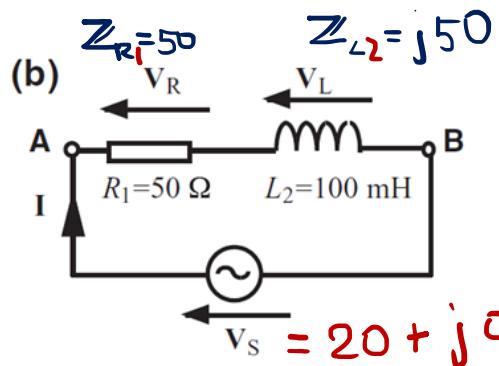


Figure 10.4 Relevant to a demonstration of the similarities between DC and AC analysis

# Example 10.1

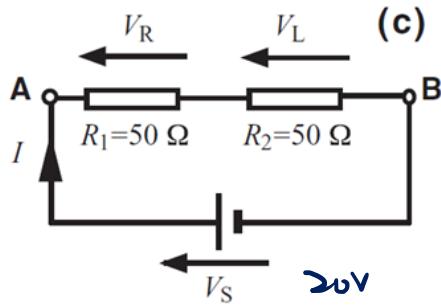

$$R_{AB} = R_1 + R_2 = 100 \Omega$$

$$I = V_s / R_{AB} = \frac{20}{100} = 0.2 \text{ A}$$

$$V_R = R_1 \cdot I = 10 \text{ V}$$

$$V_L = R_2 \cdot I = 10 \text{ V}$$

DC

$$\begin{aligned} Z_{AB} &= Z_{R1} + Z_{L2} \\ &= 50 + j50 \end{aligned}$$

$$\begin{aligned} II &= V_s / Z_{AB} = \frac{20}{50 + j50} \\ &= 0.2 - j0.2 \end{aligned}$$

$$V_R = R_1 \cdot II = 10 - j10$$

$$\begin{aligned} V_L &= Z_L \cdot II = (j50)(0.2 - j0.2) \\ &= 10 + j10 \end{aligned}$$

$$V_s = V_R + V_L$$

check!

AC

## Example 10.1


$$I = 0.2 - j 0.2$$

$$\rightarrow i(t) = \operatorname{Re} [ I e^{j\omega t} ]$$


$r = \sqrt{a^2 + b^2}$       ↓ Polar coordinate  
 $\theta = \arctan(b/a)$        $= 0.2\sqrt{2} e^{-j\frac{\pi}{4}} = 0.2\sqrt{2} \angle -45^\circ$

$$i(t) = \operatorname{Re} [ 0.2\sqrt{2} e^{-j\frac{\pi}{4}} \cdot e^{j\omega t} ]$$

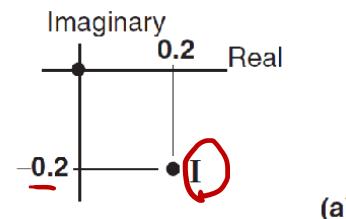
$$= \underbrace{0.2\sqrt{2}}_{\text{Amplitude}} \cdot \cos \left( \omega t - \underbrace{\frac{\pi}{4}}_{\text{phase}} \right)$$



(a)

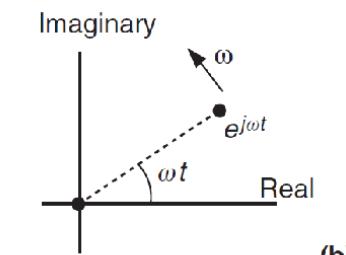

(b)

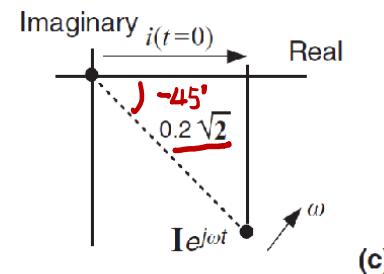

(c)

**Figure 10.5** Steps in the transformation from a complex current to the actual value at a particular time

## Example 10.1

$$V_R = 10 - j10 = 10\sqrt{2} e^{-j\frac{\pi}{4}} = 10\sqrt{2} \angle -45^\circ$$


time domain

$$v_R(t) = 10\sqrt{2} \cos(\omega t - \frac{\pi}{4})$$

$$V_L = 10 + j10 = 10\sqrt{2} e^{+j\frac{\pi}{4}} = 10\sqrt{2} \angle 45^\circ$$

time domain

$$v_L(t) = 10\sqrt{2} \cos(\omega t + \frac{\pi}{4})$$

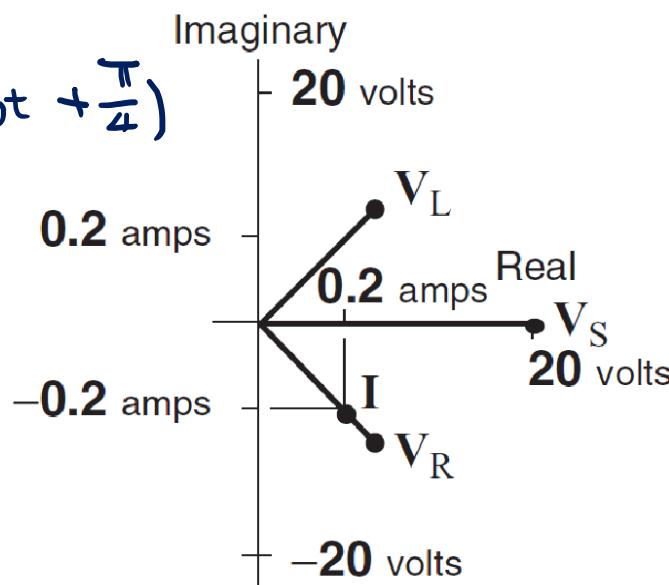

**Figure 10.6** Complex representation of voltages in the circuit of Figure 10.4a

## Simplified phasor notations

$$1 e^{j\theta} = 1 \angle \theta$$



$$(A \angle \theta) (B \angle \phi) = AB \angle (\theta + \phi)$$

$$\frac{A \angle \theta}{B \angle \phi} = \frac{A}{B} \angle (\theta - \phi)$$

e.g.  $(2 \angle 45^\circ) (3 \angle 20^\circ) = 6 \angle 65^\circ$

$$\frac{2 \angle 45^\circ}{3 \angle 20^\circ} = \frac{2}{3} \angle 25^\circ$$

# Example 10.1

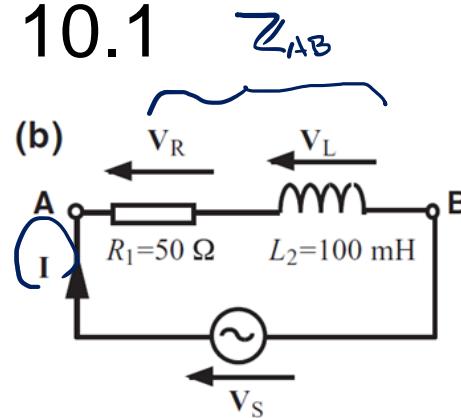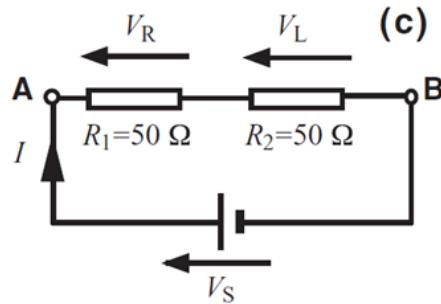

$$V_s = 20 \angle 0^\circ$$

$$\begin{aligned} Z_{AB} &= 50 + j\omega L_2 \\ &= 50 + j50 \\ &= 50\sqrt{2} \angle 45^\circ \end{aligned}$$

$$I = \frac{20 \angle 0^\circ}{50\sqrt{2} \angle 45^\circ} = 0.2\sqrt{2} \angle -45^\circ$$

$$\Rightarrow i(t) = 0.2\sqrt{2} \cos(500t - 45^\circ)$$

Using simplified phasor notations

# Example 10.1


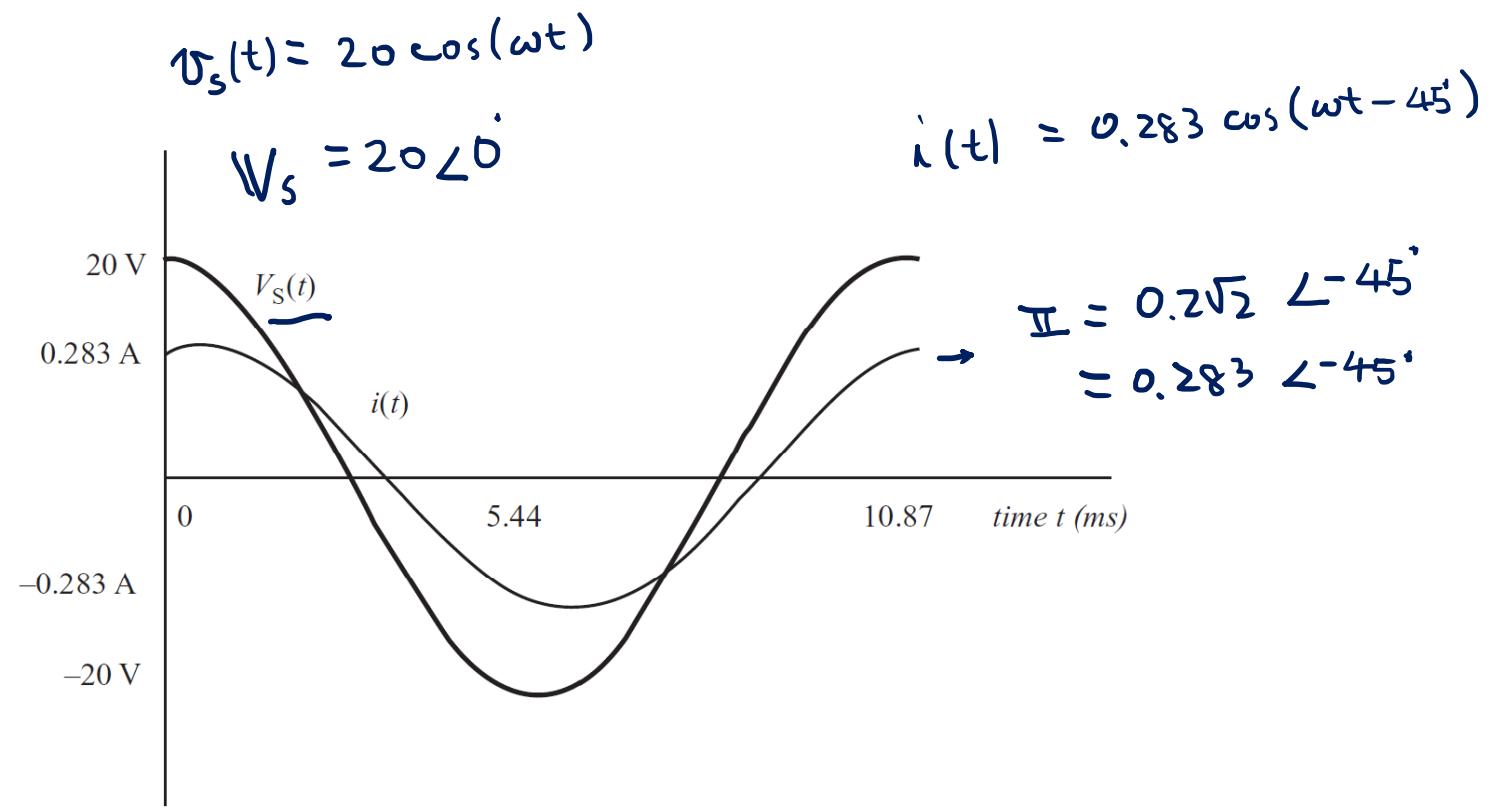


Figure 10.7 One cycle of the waveforms of  $v_s(t)$  and  $i(t)$
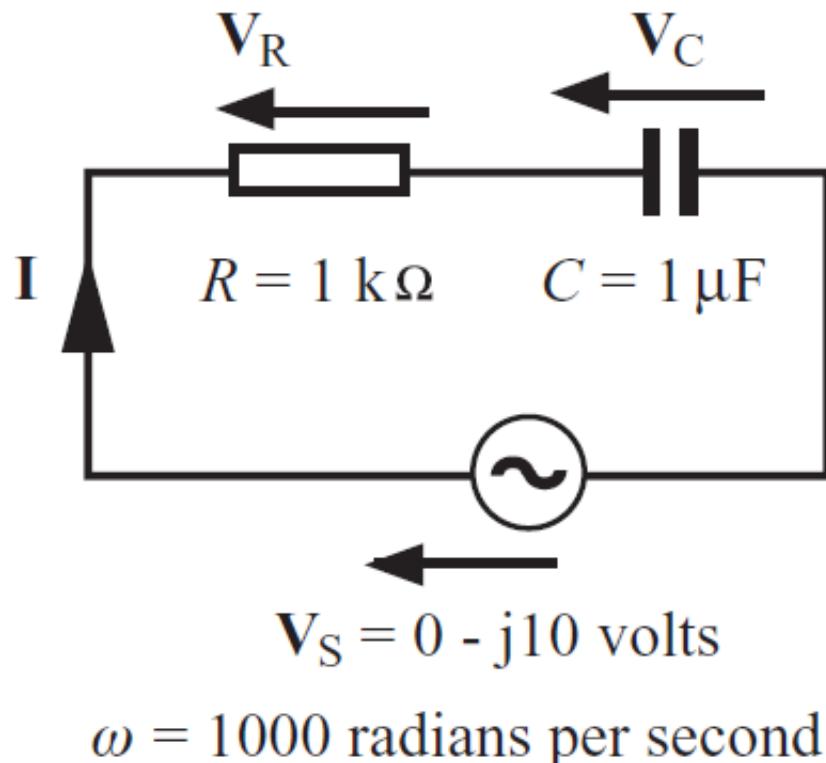
# Quiz

Find the values of  $V_R$ ,  $V_C$  and  $I$  in the circuit of the following figure. Express these quantities in polar (simplified) form.



# Quiz review


$$V_s = 10 \angle -90^\circ \text{ (V)}$$

$$\begin{aligned} Z &= R + \frac{1}{j\omega C} = 1000 + \frac{1}{j \cdot 1000 \cdot 10^{-6}} = 1000 - j1000 \\ &= 1000\sqrt{2} \angle -45^\circ \text{ (Ω)} \end{aligned}$$

$$I = \frac{V_s}{Z} = \frac{10 \angle -90^\circ}{1000\sqrt{2} \angle -45^\circ} = 5\sqrt{2} \angle -45^\circ \text{ (mA)}$$

$$V_R = R \cdot I = 5\sqrt{2} \angle -45^\circ \text{ (V)}$$
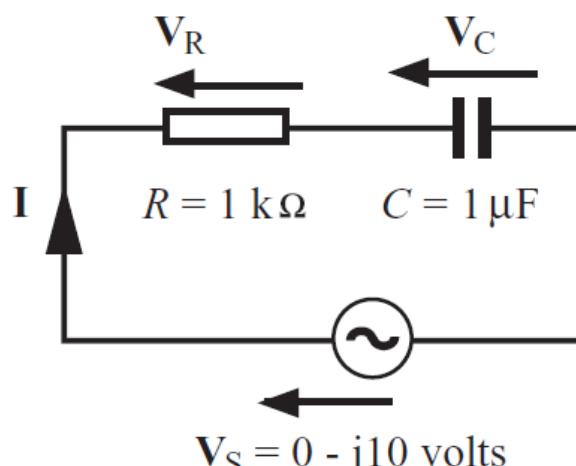
$$V_C = \frac{1}{j\omega C} I \quad \begin{matrix} Z \\ \curvearrowright \end{matrix} \quad 5\sqrt{2} \angle -135^\circ$$



$$\omega = 1000 \text{ radians per second}$$

# Simplified AC analysis


$$Y = \frac{1}{Z}$$

$Z = R + jX$   
 Resistance      Reactance  
 $Y = G + jB$   
 Conductance      Susceptance

C:  $\frac{1}{j\omega C}$  容抗  
 L:  $j\omega L$  感抗  
 C 容納  
 L 感應

**Impedance**  
**Admittance**  
**導納**

**Impedance**

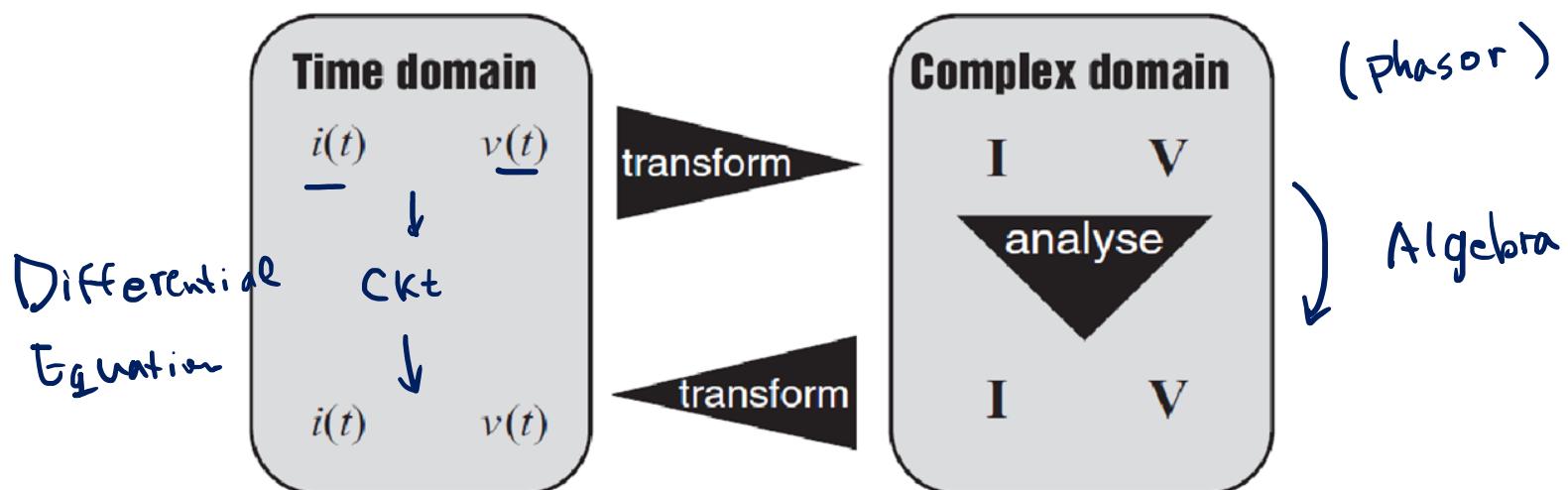

**Figure 10.8** Illustrating the approach to AC analysis based on the use of complex currents and voltages