

電子電工學





Lecture 13



Recap: AC Circuit Analysis

DC ← Complex Voltage
Current
Impedance ← AC

Table 10.1 Similarities between the component relations and connection constraints in DC circuits and AC circuits

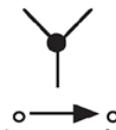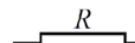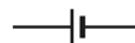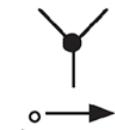DC Currents and voltages	AC Currents and voltages
<p><i>representation</i></p>     <p><i>relation</i></p> $\sum_{\text{node}} I = 0$ $\sum_{\text{loop}} V = 0$ $V = R I$ <p><i>Connections</i></p> <p><i>at node</i></p> <p><i>around loop</i></p> <p>Components</p> <p><i>resistor</i></p> <p><i>capacitor</i></p> <p><i>inductor</i></p> <hr/> <p><i>voltage source</i></p> <p><i>current source</i></p>	<p><i>relation</i></p> $\sum_{\text{node}} \mathbf{I} = 0$ $\sum_{\text{loop}} \mathbf{V} = 0$ $\mathbf{V} = R \mathbf{I}$ $\mathbf{I} = j\omega C \mathbf{V}$ $\mathbf{V} = j\omega L \mathbf{I}$ <p><i>representation</i></p>      

Example 10.1

R-L AC signals

ODE ←

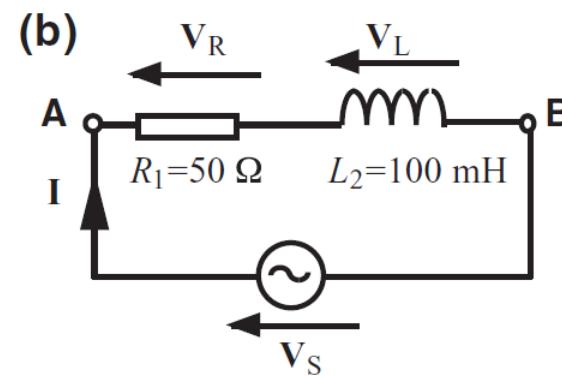
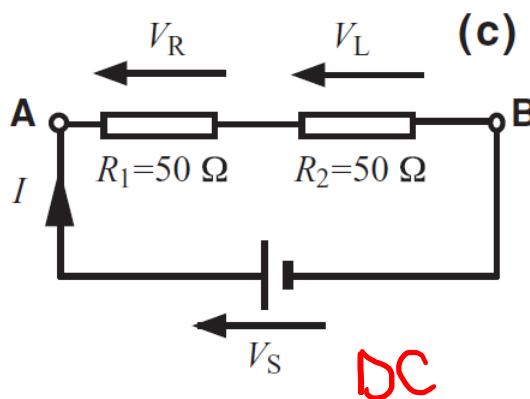
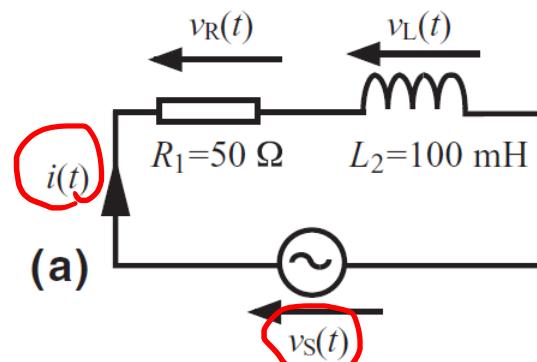


Figure 10.4 Relevant to a demonstration of the similarities between DC and AC analysis

Algebra ←


Known V_s

$$I = \frac{V_s}{Z_R + Z_L}$$

$$\hookrightarrow i(t) = \operatorname{Re}[I e^{j\omega t}]$$

Recap: Simplified phasor notations
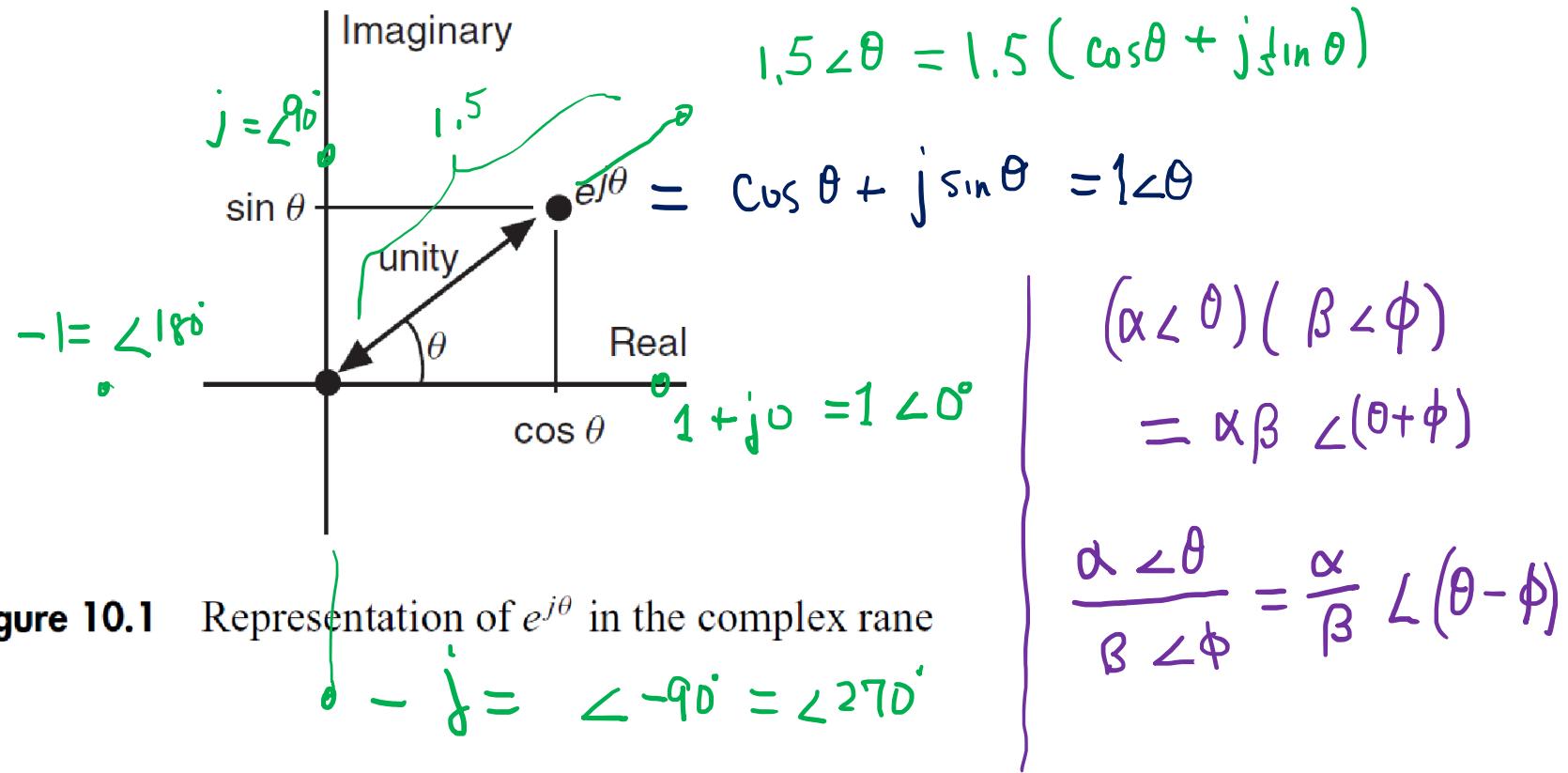
$$\angle \theta \equiv e^{j\theta} \quad (\text{polar})$$



Recap: Simplified AC analysis

$$\begin{array}{l} \text{Impedance} \quad \leftarrow Z = R + jX \\ \downarrow Y = 1/Z \\ \text{Admittance} \quad \leftarrow Y = G + jB \end{array}$$

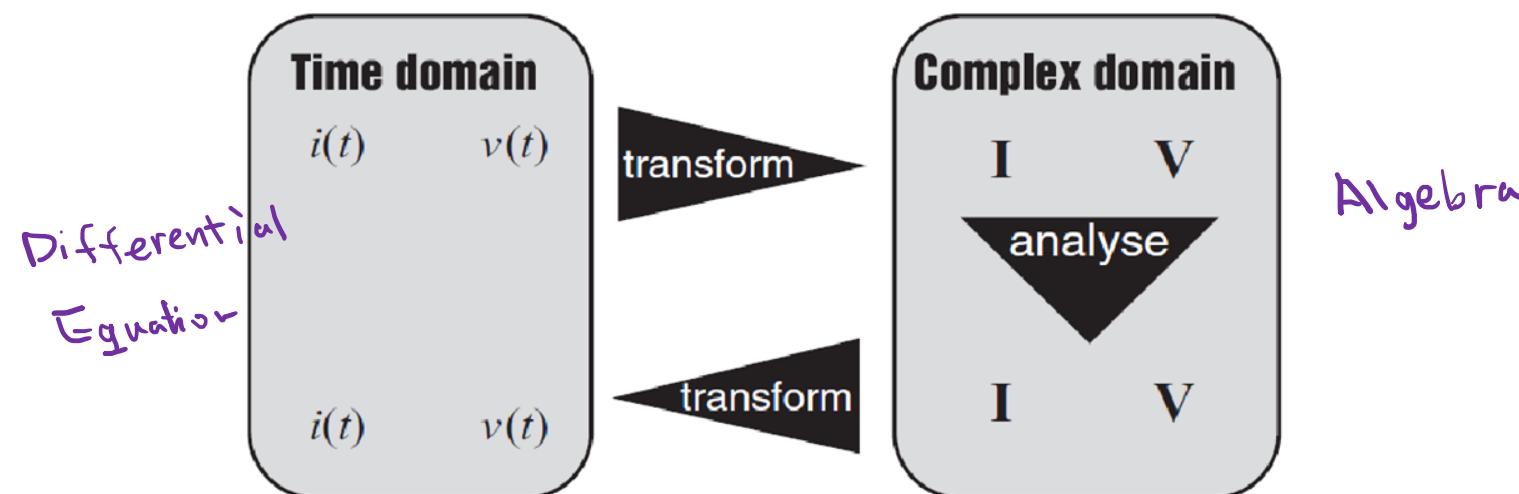


Figure 10.8 Illustrating the approach to AC analysis based on the use of complex currents and voltages

Example 10.2 (a)

Find the impedance and admittance between the terminals A and B at a frequency of $\underline{\omega}$ rad/s.

$$(a) \quad Z_{AB} = |k\Omega + \frac{1}{j \cdot 1000 \cdot 10^6}|$$


\downarrow Impedance

$$= 1k\Omega - j1k\Omega = (1-j) k\Omega$$


$$Y_{AB} = \frac{1}{(1-j) k\Omega} = \left(\frac{1}{2} + j\frac{1}{2}\right) mS$$

\downarrow

Admittance

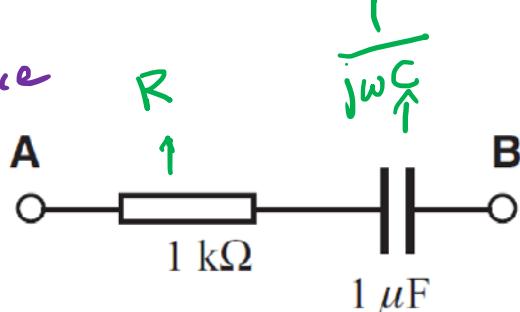

(a)

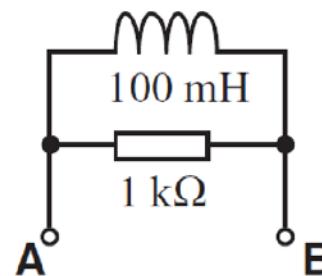

(b)

Figure 10.9 Relevant to Example 10.2

Example 10.2 (b)

Find the impedance and admittance between the terminals A and B at a frequency of 1000 rad/s.


$$\text{Admittance } Y_{AB} = Y_R + Y_L = \left(\frac{1}{1k} + \frac{1}{j \cdot 1000 \cdot 100\text{mH}} \right) S$$

$$\frac{1}{1k} \left(\quad \right) = \left(\frac{1}{1k} + \frac{1}{j \cdot 100} \right) S = (1 - j10) \text{ mS}$$


$$Z_{AB} = \frac{1}{(1 - j \cdot 10)} k\Omega = \frac{1 + j10}{101} k\Omega$$

$$\simeq 0.0099 + j0.099 k\Omega$$
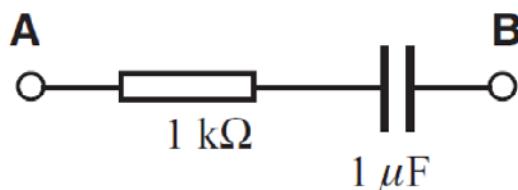
$$\text{Impedance } \simeq (1k\Omega \parallel j\omega 100\text{mH}) \simeq (9.9 + j99) \Omega$$



(a)

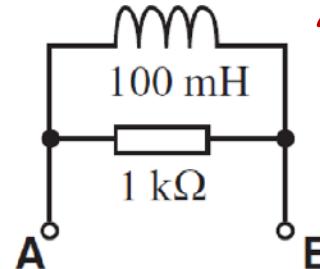

(b)

Figure 10.9 Relevant to Example 10.2

Example 10.3

$$\begin{aligned}
 Z_{XY} &= R \parallel \frac{1}{j\omega C} = \frac{1}{\frac{1}{R} + j\omega C} = \frac{R}{1 + j\omega RC} \\
 &= \frac{1k}{1 + j \cdot 1000 \cdot 1000 \cdot 10^{-6}} = \frac{1k}{1 + j} = (0.5 - j 0.5) \text{ k}\Omega
 \end{aligned}$$

$$Z_{AB} = Z_{XY} + j\omega L$$

$$= (0.5 - j 0.5) \text{ k} + j \cdot 1000 \cdot 1 \text{ H}$$

$$= (0.5 + j 0.5) \text{ k}$$

$$\boxed{\text{II} = \frac{V_s}{Z_{AB}}}$$

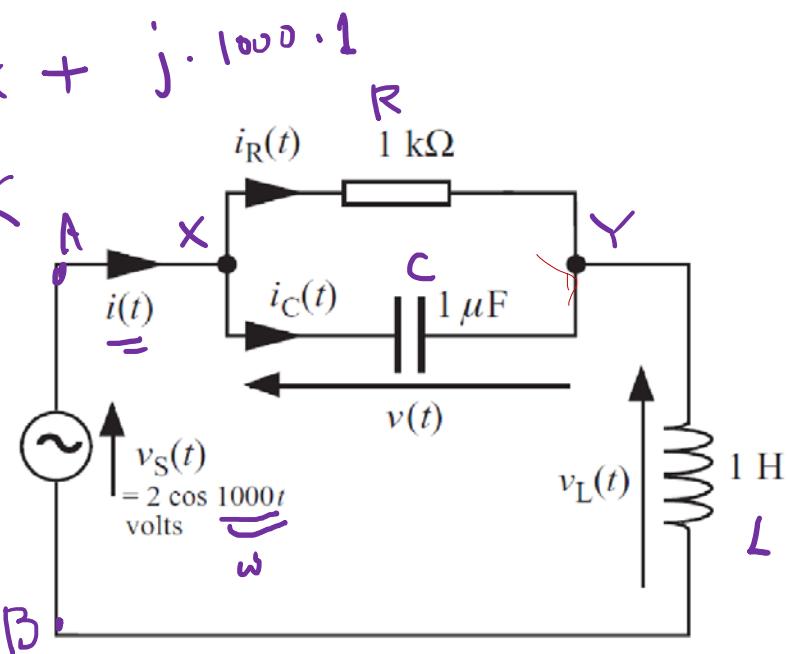


Figure 10.10 The circuit to be analysed in Example 10.3

Example 10.4

$Z_{AB} = (0.5 + j0.5) \text{ k}\Omega$

$$= 0.5\sqrt{2} \angle 45^\circ \text{ k}\Omega$$

$\text{II} = \omega_s / Z_{AB}$

$$= \frac{2 \angle 0^\circ}{0.5\sqrt{2} \angle 45^\circ}$$

$$= 2\sqrt{2} \angle -45^\circ (\text{mA})$$

$i(t) = 2\sqrt{2} \cos\left(\frac{1000t}{\omega} - 45^\circ\right)$

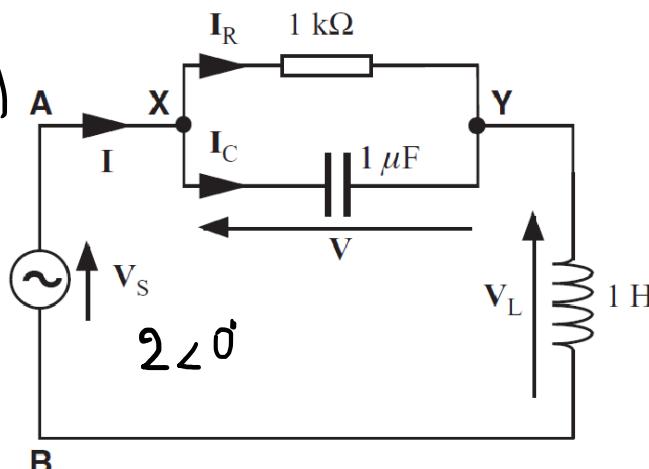


Figure 10.11 The circuit of Figure 10.10 with currents and voltages represented by complex quantities

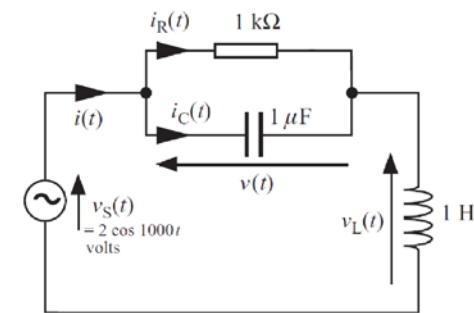


Figure 10.10 The circuit to be analysed in Example 10.3

Summary

AC ckt $\xrightarrow{\text{Complex } V, I,}$ DC analys.

Diff. eqn's (phasor $A\angle\theta$) Algebra

Basix

Circuit analysis using Laplace transform


$t\text{-domain}$, $f(t)$ $\xrightarrow{\mathcal{L}}$ $s\text{-domain}$

$$\text{Laplace Transform}$$
$$F(s) = \int_0^{\infty} f(t)e^{-st} dt$$

$$e^{at}$$

$$\cos(\omega t)$$

...

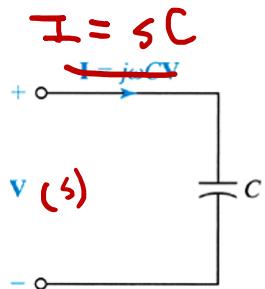

$$\frac{1}{s-a}$$

$$\frac{s}{s+\omega^2}$$


...

$$I(s) = sC \cdot V(s)$$

$$Z_C = \frac{1}{sC}$$

$$V(s) = sL \cdot I(s)$$

$$Z_L = sL$$

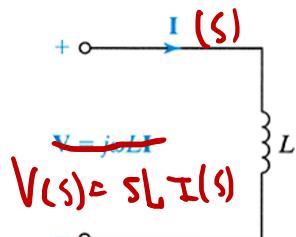

Circuit analysis using Laplace transform

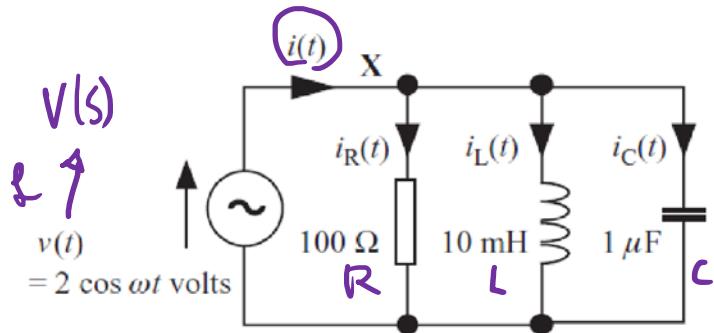



Figure 9.18 A resonant circuit

$$I(s) = \frac{V(s)}{R // sL // \frac{1}{sC}}$$

$$\begin{aligned} &= V(s) \left[\frac{1}{R} + \frac{1}{sL} + sC \right] \\ &\downarrow f^{-1} \quad \downarrow f^{-1} \\ i(t) &= v(t) * h(t) \end{aligned}$$

Convolution

Impulse Response

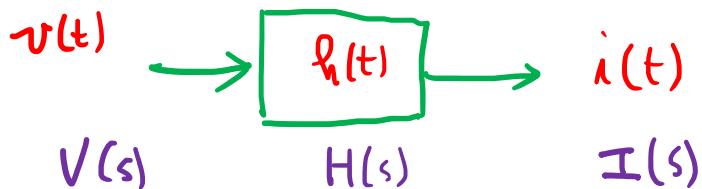

Frequency Domain Behaviour

Chapter 11

Review: resonance

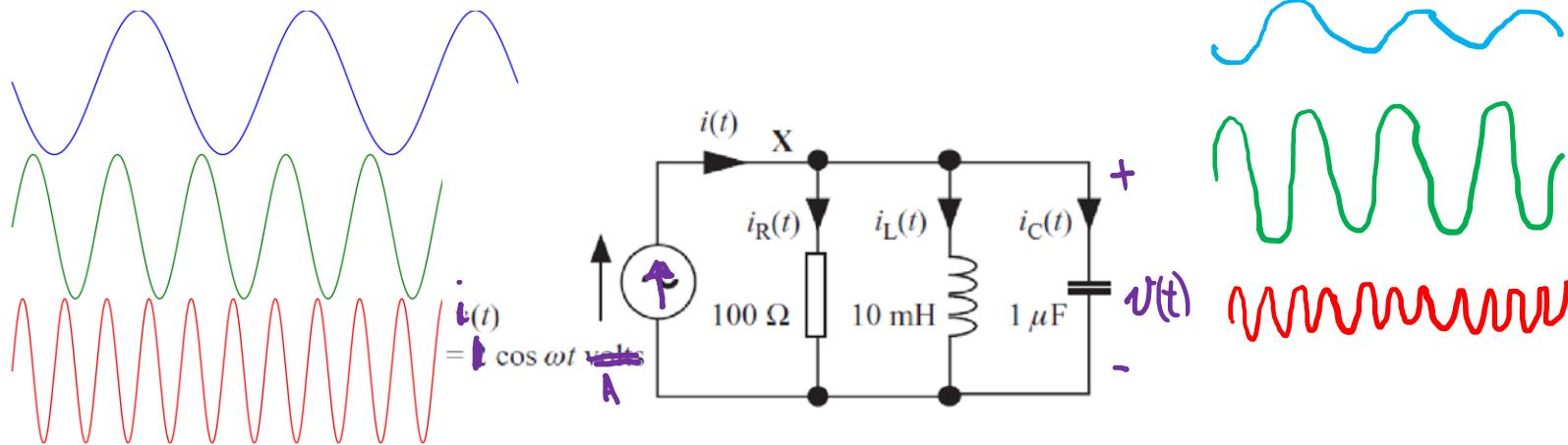


Figure 9.18 A resonant circuit

R-L-C
Frequency
Response

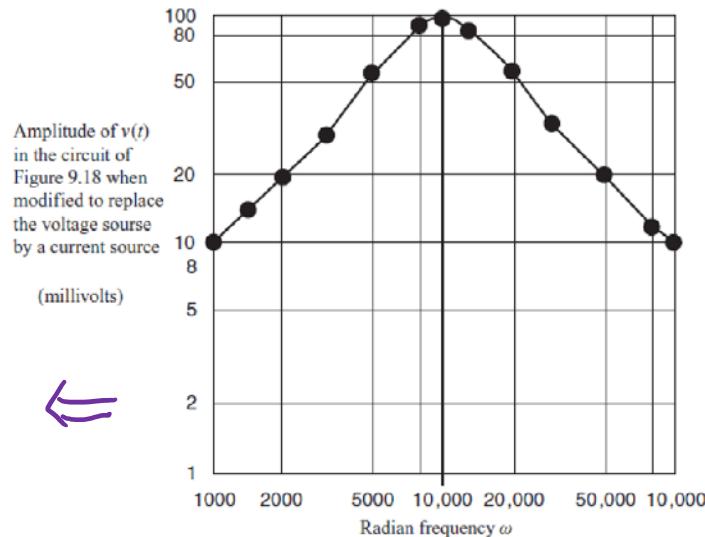


Figure 9.20 Pertinent to the circuit of Figure 9.18 in which the sinusoidal voltage source is replaced by a sinusoidal current source of 1 mA amplitude. The sketch shows the variation of the amplitude of the voltage $v(t)$ as the source frequency ω varies

Frequency behaviour

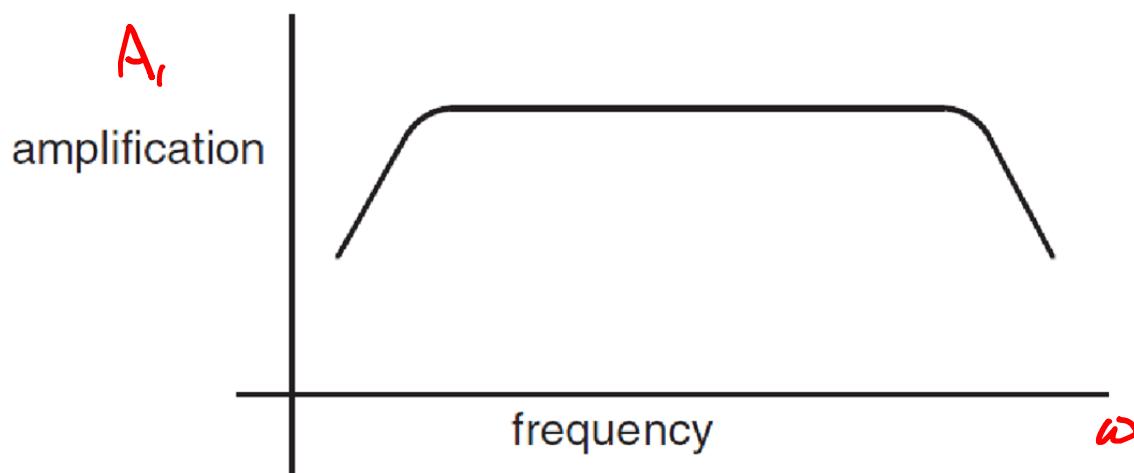
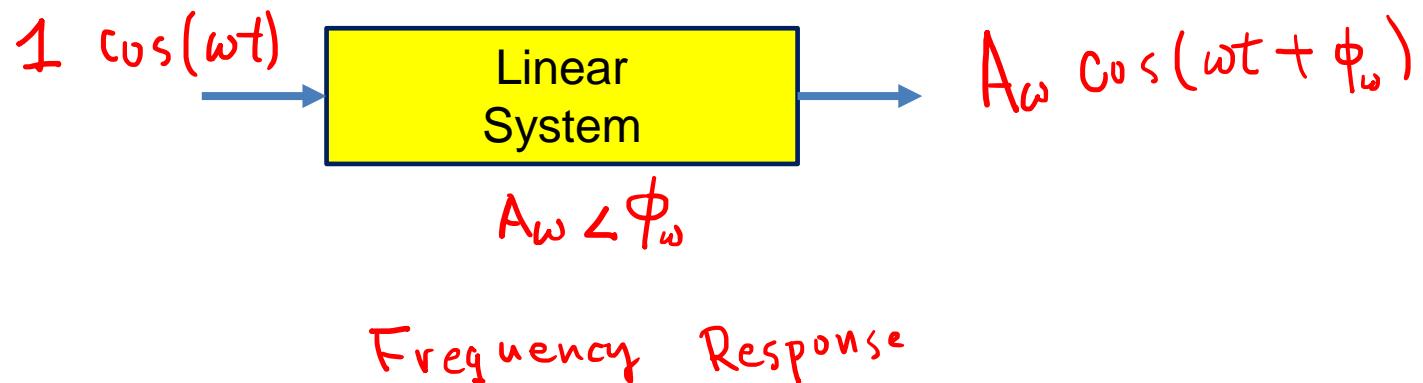


Figure 11.1 Typical form of the frequency dependence of an amplifier's gain

RC circuit

Voltage Divider

$$V_c = V_s \cdot \frac{Z_c}{R + Z_c} = V_s \frac{\frac{1}{j\omega C}}{R + \frac{1}{j\omega C}} = V_s \frac{1}{1 + j\omega RC}$$

$$\frac{V_c}{V_s} = \frac{1}{1 + j\omega RC} = A_\omega < \phi_\omega$$

$$\left\{ \begin{array}{l} A_\omega = \left| \frac{V_c}{V_s} \right| = \frac{1}{\sqrt{1 + \omega^2 R^2 C^2}} \\ \phi_\omega = -\tan^{-1}(\omega RC) \end{array} \right.$$

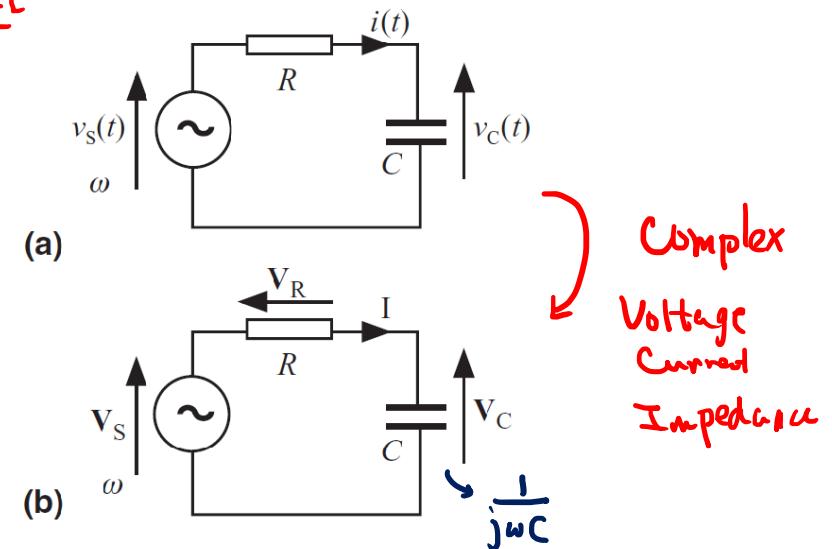


Figure 11.2 (a) The circuit whose currents and voltages are of interest; (b) the same circuit with currents and voltages represented by complex values

Frequency response

$$\left| \frac{V_C}{V_S} \right| = \frac{1}{\sqrt{1 + \omega^2 R^2 C^2}}$$

Gain

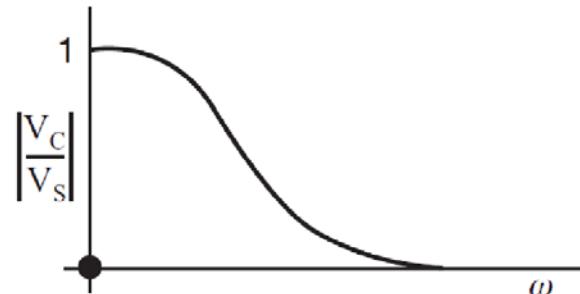


Figure 11.3 A plot of $|V_C/V_S|$ for the circuit of Figure 12.2 (linear scales)

$$\omega \rightarrow 0 \Rightarrow \left| \frac{V_C}{V_S} \right| = 1$$

$\omega \downarrow$

Gain ↑

$\omega \uparrow$

Gain ↓

"Low-pass Filter"

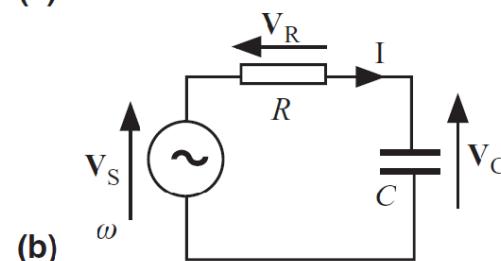
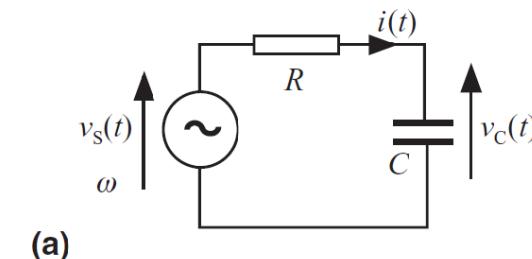


Figure 11.2 (a) The circuit whose currents and voltages are of interest; (b) the same circuit with currents and voltages represented by complex values

Asymptotic behavior (1)

$$\log \left| \frac{V_C}{V_S} \right| = \log \frac{1}{\sqrt{1 + \omega^2 R^2 C^2}}$$

$$= -\frac{1}{2} \log (1 + \omega^2 R^2 C^2)$$

For $\omega \gg \frac{1}{RC}$

$$\log \left| \frac{V_C}{V_S} \right| \approx -\frac{1}{2} \log (\omega^2 R^2 C^2)$$

y -axis
 x -axis
constant

$$= -\log(\omega) - \log(RC)$$

$$y \approx -x - \text{constant}$$


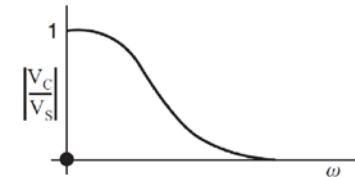


Figure 11.3 A plot of $|V_C/V_S|$ for the circuit of Figure 12.2 (linear scales)

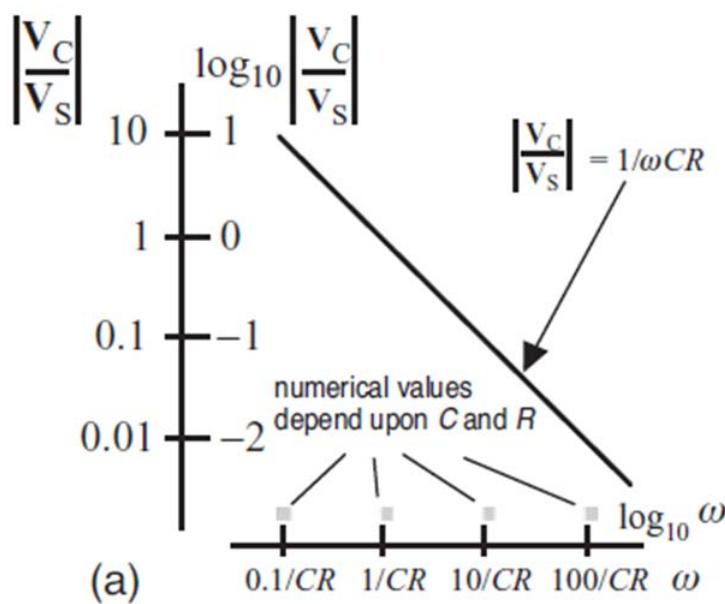

Asymptotic behavior (2)

For $\omega \ll \frac{1}{RC}$

$$\begin{aligned} \log \left| \frac{V_c}{V_s} \right| &= -\frac{1}{2} \log (1 + \omega^2 R^2 C^2) \\ &\approx -\frac{1}{2} \log 1 \\ &= 0 \end{aligned}$$


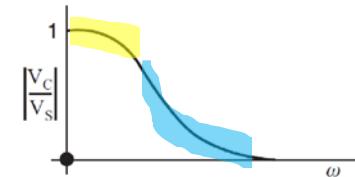


Figure 11.3 A plot of $|V_c/V_s|$ for the circuit of Figure 12.2 (linear scales)

Log-Log scale

"Bode" Plot

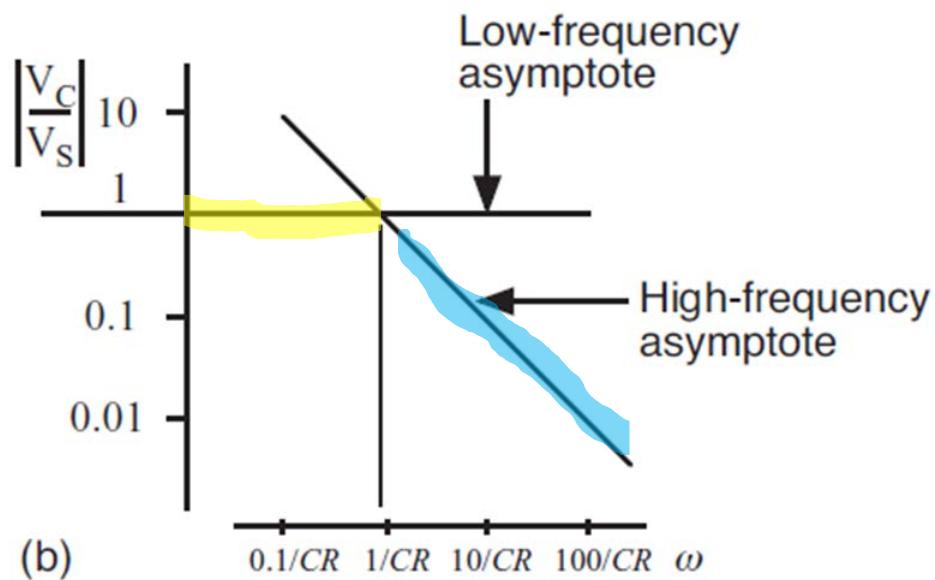

Asymptotic behavior (3)

If $\omega \approx 1/RC$

$$\log \left| \frac{V_C}{V_S} \right| = \log \frac{1}{\sqrt{1 + \omega^2 R^2 C^2}}$$

$$\approx \log \frac{1}{\sqrt{2}} = -\frac{1}{2} \log 2 \approx -0.15$$

↓

$$\left| \frac{V_C}{V_S} \right| \approx \frac{1}{\sqrt{2}} = 0.707$$



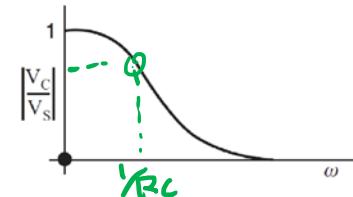




Figure 11.3 A plot of $|V_C/V_S|$ for the circuit of Figure 12.2 (linear scales)

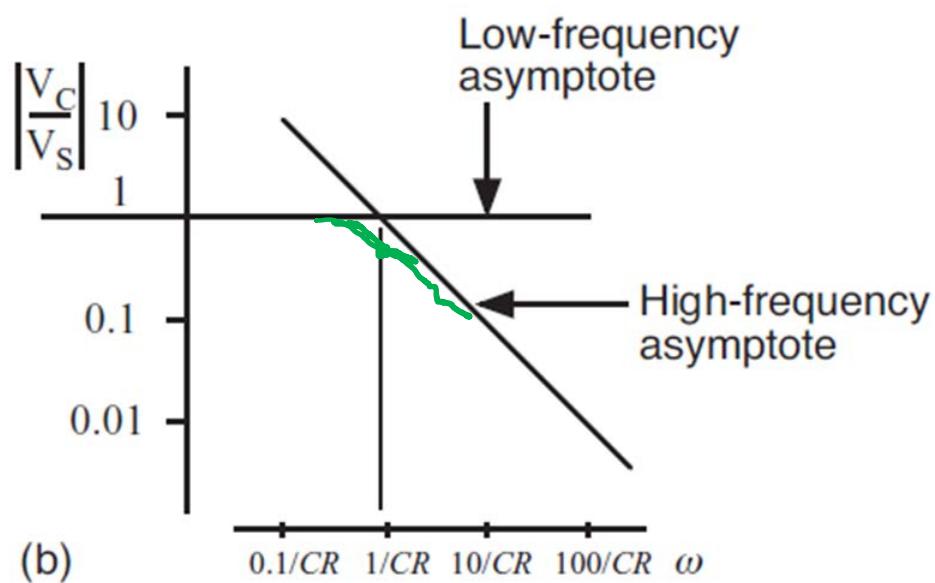

Frequency behaviour

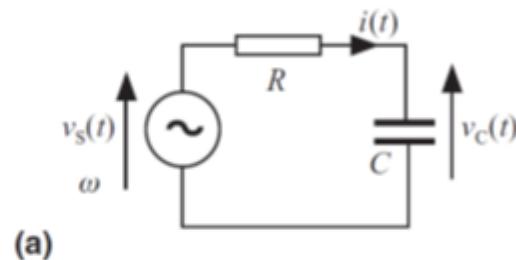


Linear scale

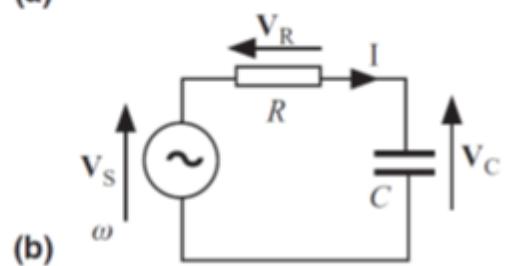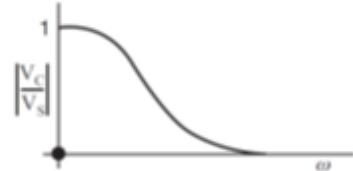

Log-log Scale

plot of $|V_C/V_S|$ for the circuit of Figure 12.2 (linear scales)

Figure 11.2 (a) The circuit whose currents and voltages are of interest; (b) the same circuit with currents and voltages represented by complex values

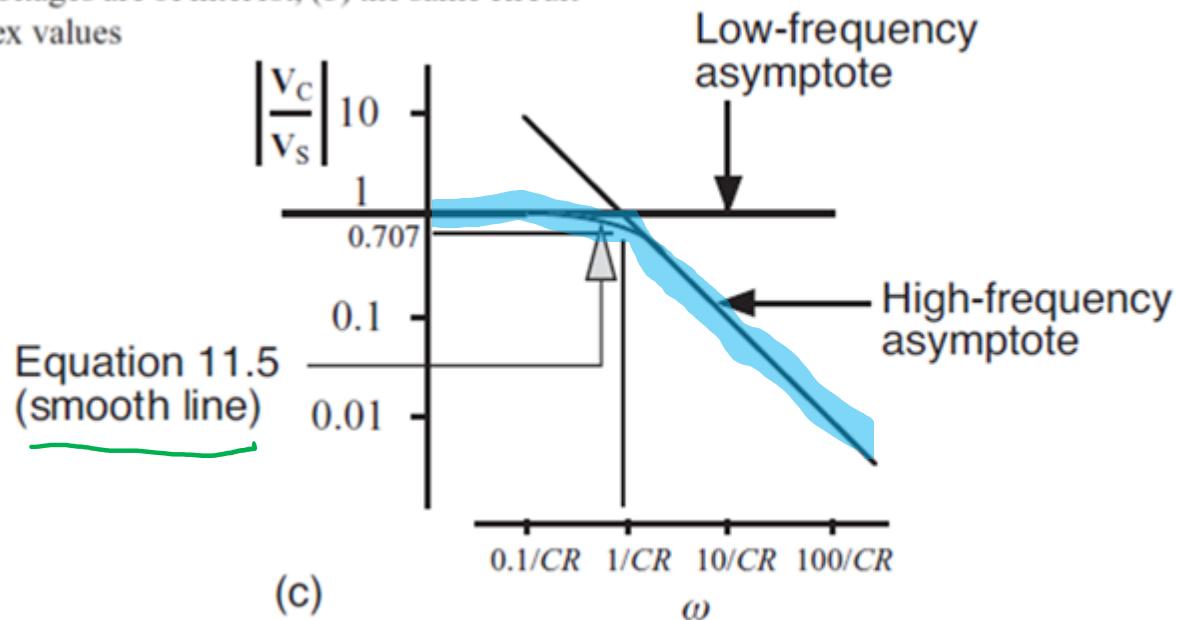

Extreme frequencies

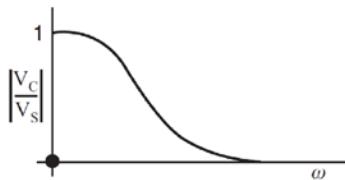


Figure 11.3 A plot of $|V_C/V_S|$ for the circuit of Figure 12.2 (linear scales)

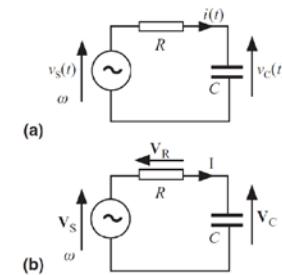


Figure 11.2 (a) The circuit whose currents and voltages are of interest; (b) the same circuit with currents and voltages represented by complex values

$$\omega \rightarrow 0$$


$$V_s(t) \approx V_s \cos(0) = V_s$$

DC source

$$|Z_{cl}| = \frac{1}{j\omega C} \Big|_{\omega \rightarrow 0} \rightarrow \infty$$

Open-ckt

$$\left| \frac{V_c}{V_s} \right| \xrightarrow{\omega \rightarrow 0} \frac{\infty}{R + \infty} \Rightarrow 1$$

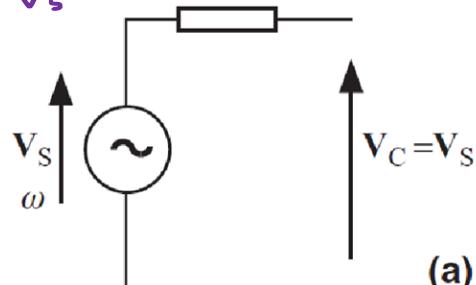


(a)

$$\omega \rightarrow \infty$$

$$|Z_{cl}| = \frac{1}{j\omega C} \Big|_{\omega \rightarrow \infty} \rightarrow 0$$

Short-ckt

$$\left| \frac{V_c}{V_s} \right| \xrightarrow{\omega \rightarrow \infty} 0$$

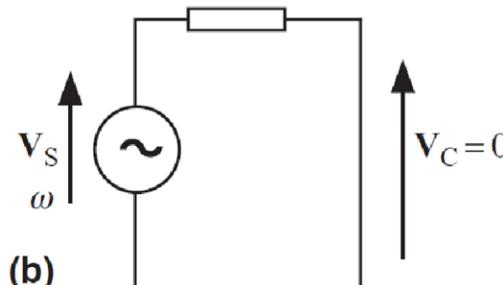

(b)

Figure 11.7 (a) At zero frequency the impedance of a capacitor is infinite and the capacitor acts as an open-circuit; (b) at infinite frequency the capacitor acts as a short-circuit

Example 11.1

R-L circuits

Voltage divider

$$\left| \frac{V_2}{V_1} \right| = \left| \frac{j\omega L}{R + j\omega L} \right| = \left| \frac{1}{1 + \frac{R}{j\omega L}} \right|$$
$$= \frac{1}{\sqrt{1 + \left[\frac{1}{\omega(L/R)} \right]^2}}$$

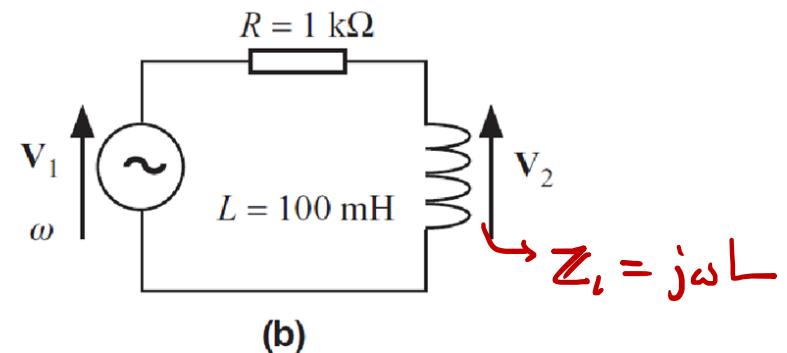
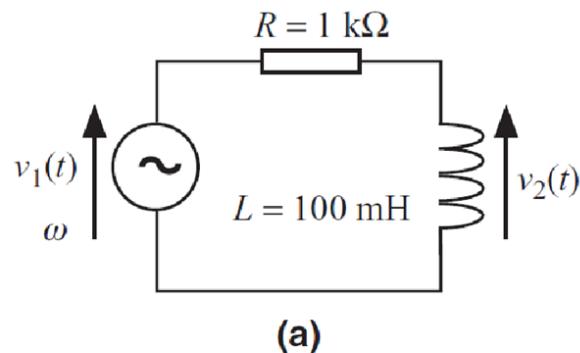


Figure 11.5 (a) The circuit of Example 11.1; (b) the same circuit with sinusoidal voltages represented by complex voltages

Example 11.1

$$\log \left| \frac{V_2}{V_1} \right| = -\frac{1}{2} \log \left[1 + \frac{1}{(\omega L/R)^2} \right]$$

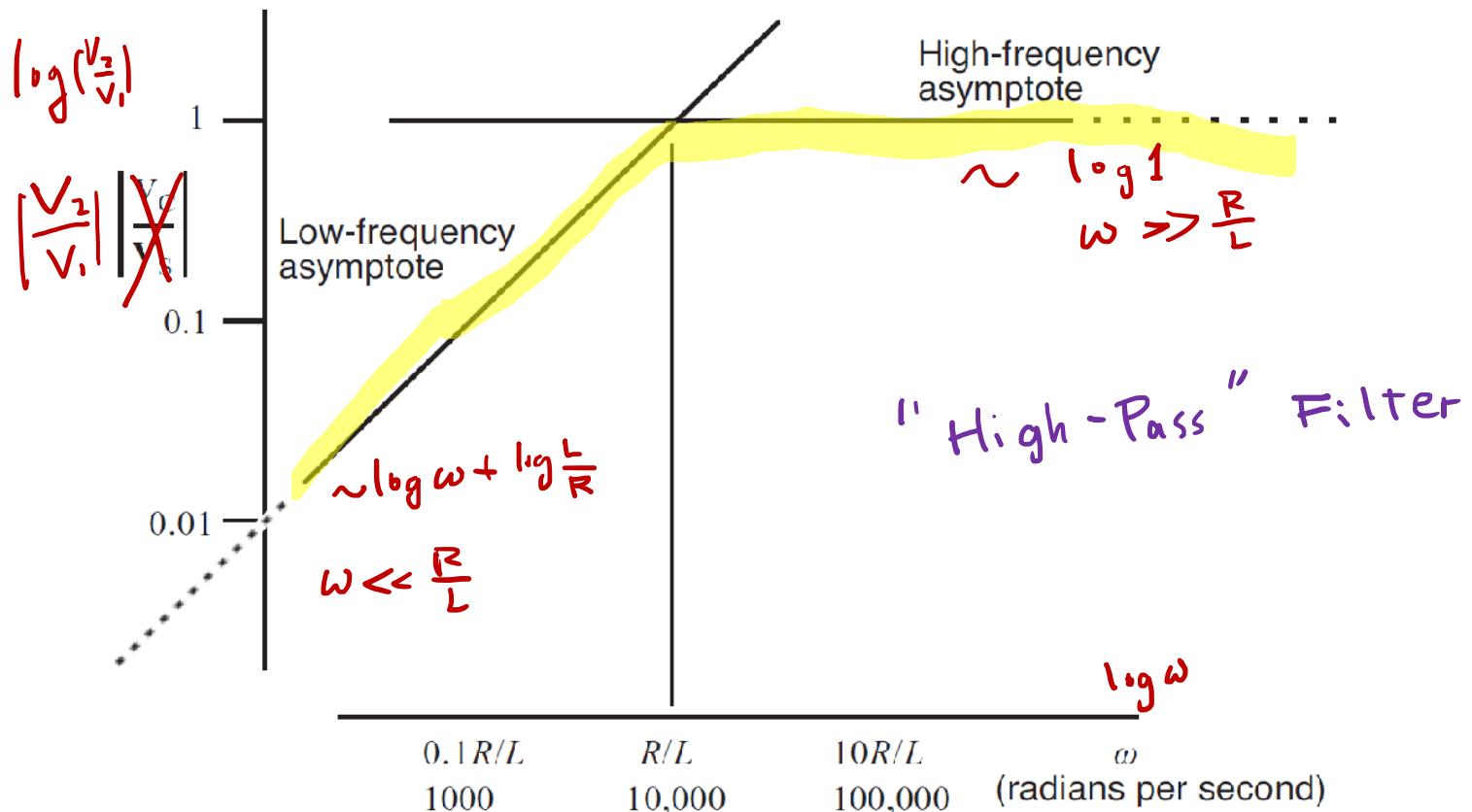


Figure 11.6 The asymptotes associated with the voltage ratio $|V_1/V_2|$ in the circuit of Figure 11.5

Extreme frequencies

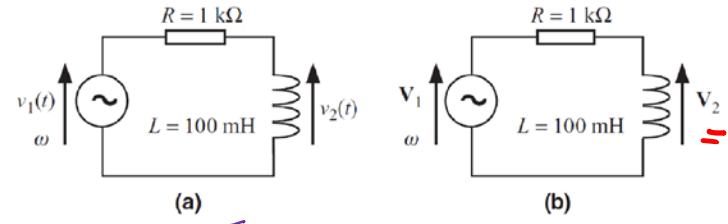


Figure 11.5 (a) The circuit of Example 11.1; (b) the same circuit with sinusoidal voltages represented by complex voltages


$$w \rightarrow \infty$$

$$|Z_1| = |j\omega L| \rightarrow \infty$$

Open - ck !

$$v_2 \approx v_1$$

$$|\nu_2/\nu_1| \rightarrow 1$$

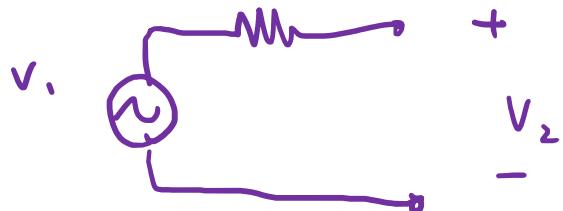


$\omega \rightarrow 0$ DC

$$|Z_L| = |j\omega L| \rightarrow 0$$

Short - ckt

→ ♂

$$(V_2/V_1) \rightarrow D$$

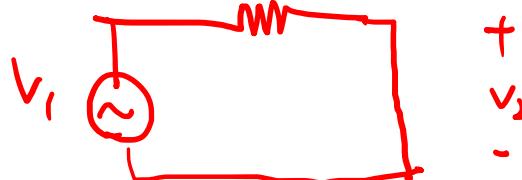

Quiz

For the following circuit sketch, on the log-log scale, the low- and high-frequency asymptotes of the magnitude of the voltage amplification $|V_2/V_1|$ where V_1 and V_2 are the complex voltages representing sinusoidal voltages. Put numerical values on the x-axis.

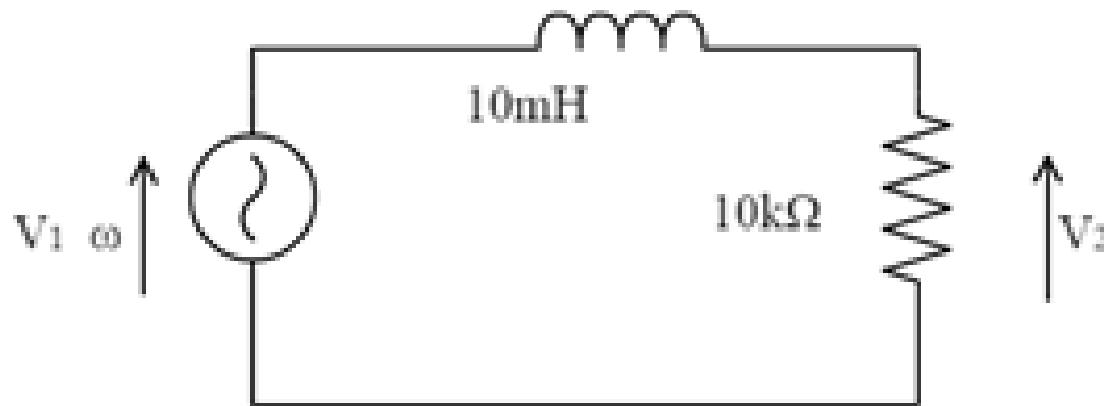
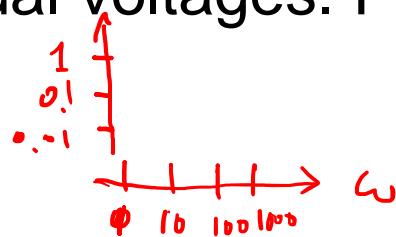


Figure 1

Quiz Review

$$\frac{V_2}{V_1} = \frac{R}{R+j\omega L} = \frac{1}{1+j\omega L/R}$$

$\omega \ll R/L$

$$|\frac{V_2}{V_1}| \approx 1$$

$\omega \gg R/L$

$$|\frac{V_2}{V_1}| = \frac{R}{\omega L}$$


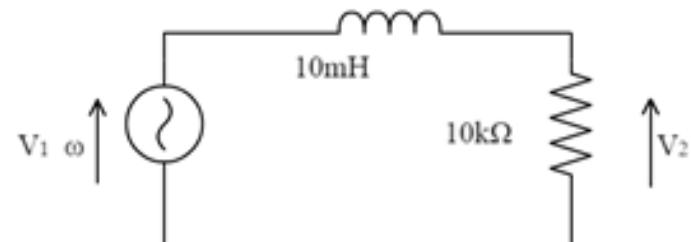


Figure 1

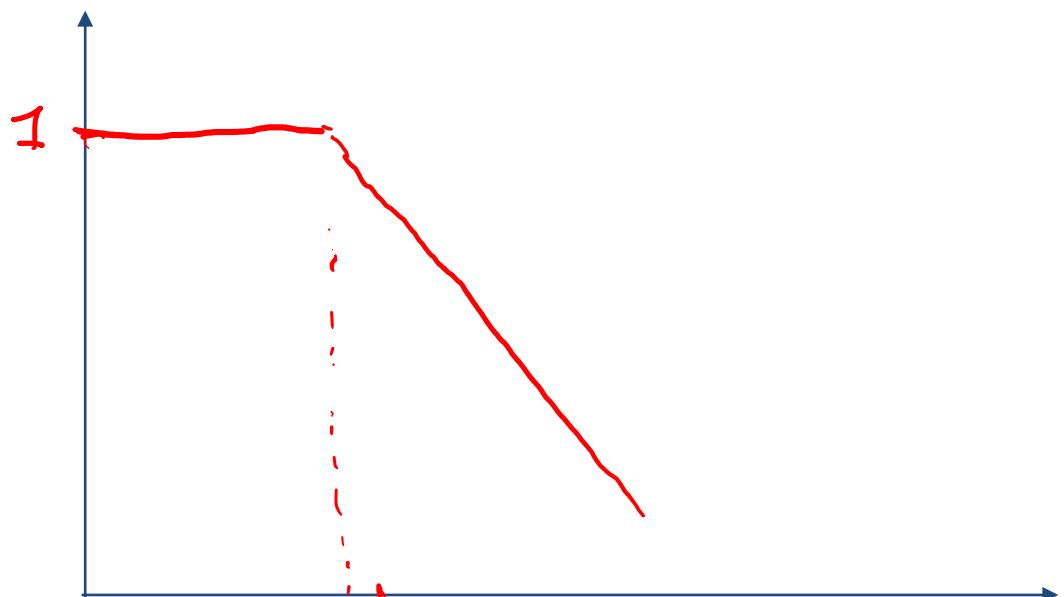

$$R/L = \frac{10^3}{10^4} = 10^{-1} \text{ rad/s}$$


ω

Opamp limitations

Ideal opamp


$A \rightarrow \infty$

For any frequency

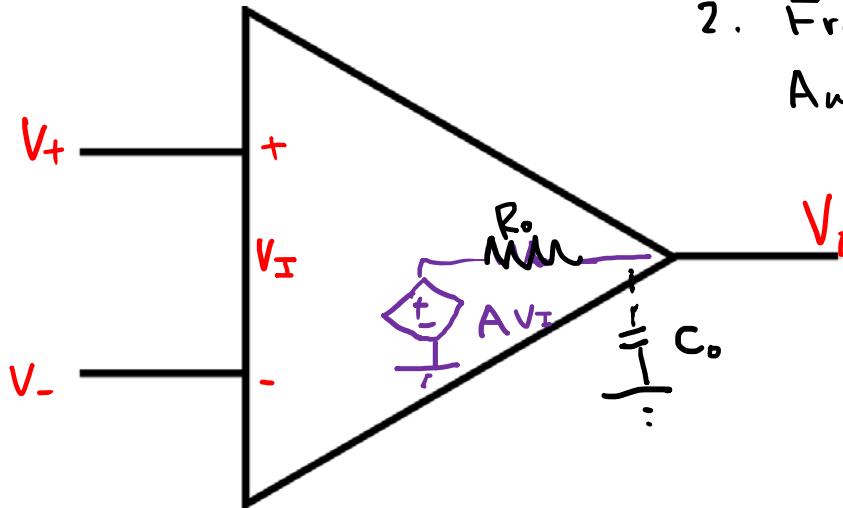

In real world

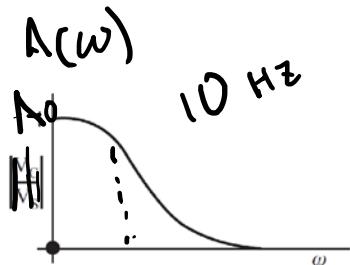1. A "finite"
2. Frequency dependent
 $A\omega \downarrow$ as $\omega \uparrow$



Opamp limitations

$$\left| \frac{V_o}{V_I} \right| = A_0 \cdot \frac{1}{1 + j \frac{\omega}{\omega_0}}$$

$$\frac{\omega_0}{2\pi} = 10 \text{ Hz}$$

"cut-off frequency"


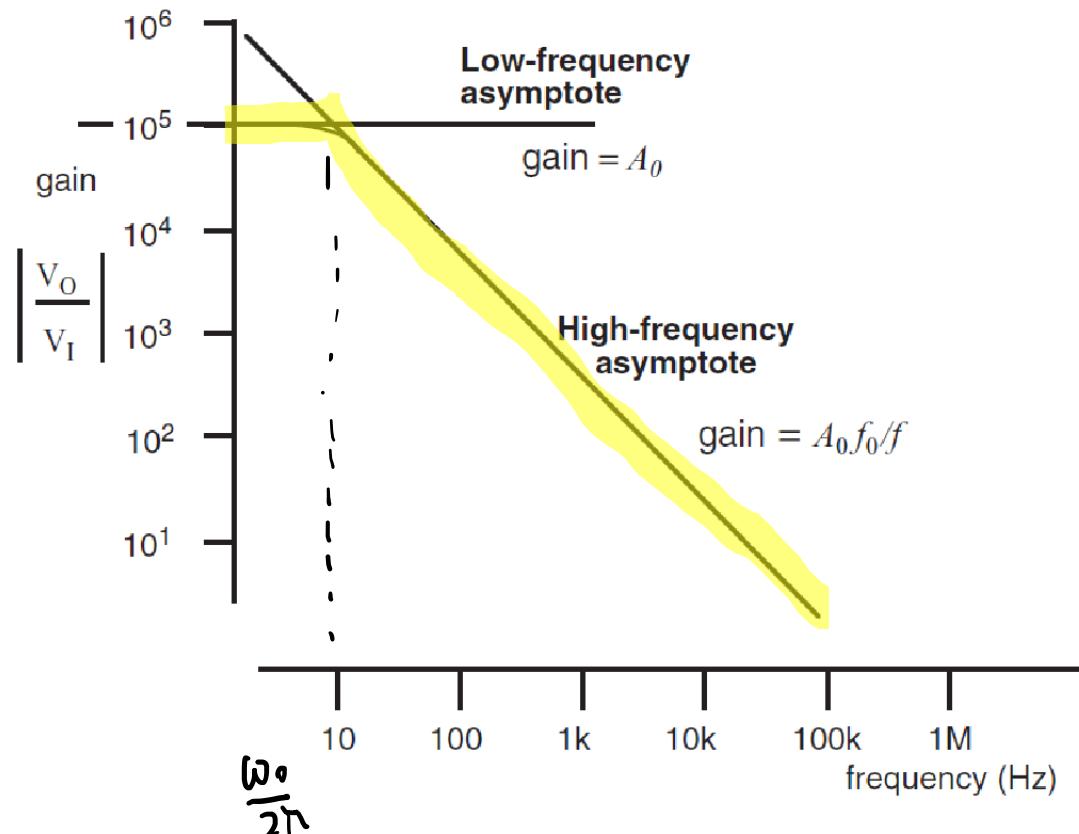
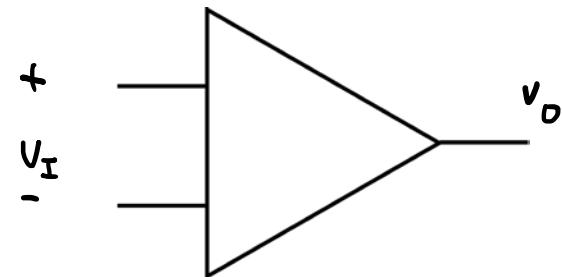


Figure 11.9 Typical low- and high-frequency asymptotes of the gain of an opamp

Inverter frequency response

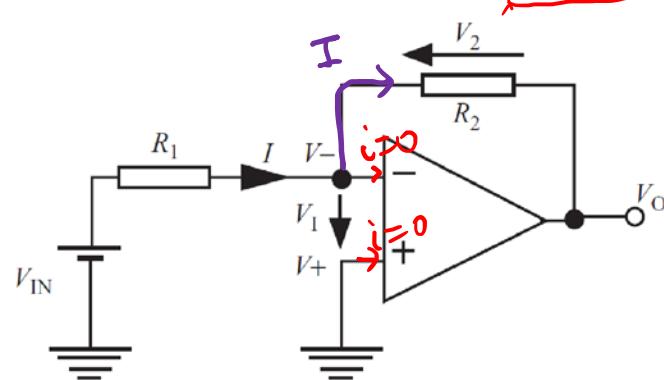


$V_o \sim V_{IN}$ Relation

$$\left\{ \begin{array}{l} I = \frac{V_{IN} - V_-}{R_1} = \frac{V_- - V_o}{R_2} \\ V_- = V_+ - V_I = -V_I \\ V_o = A_\omega V_I \end{array} \right.$$

Figure 11.8 The inverter circuit

$$\Rightarrow \frac{V_o}{V_{IN}} = - \frac{R_2}{R_1} \frac{1}{1 + \frac{1}{A_\omega} \left(\frac{R_2}{R_1} + 1 \right)}$$

Let $G = \frac{R_2}{R_1} \gg 1$

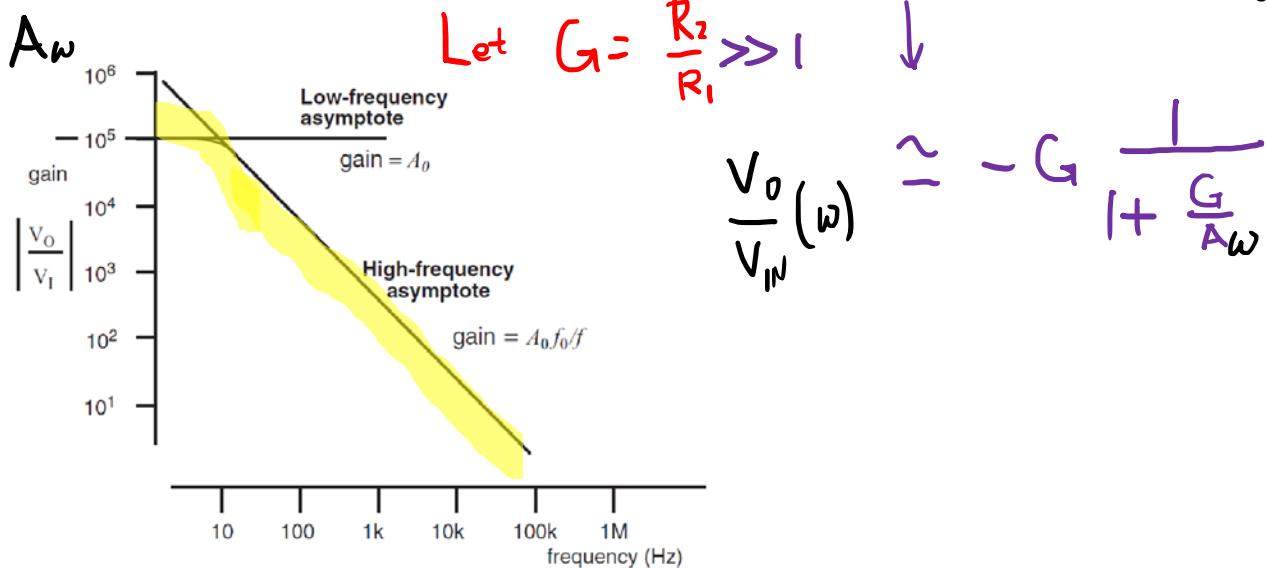

$$\frac{V_o}{V_{IN}}(\omega) \approx -G \frac{1}{1 + \frac{G}{A_\omega}}$$

Figure 11.9 Typical low- and high-frequency asymptotes of the gain of an opamp

Inverter frequency response

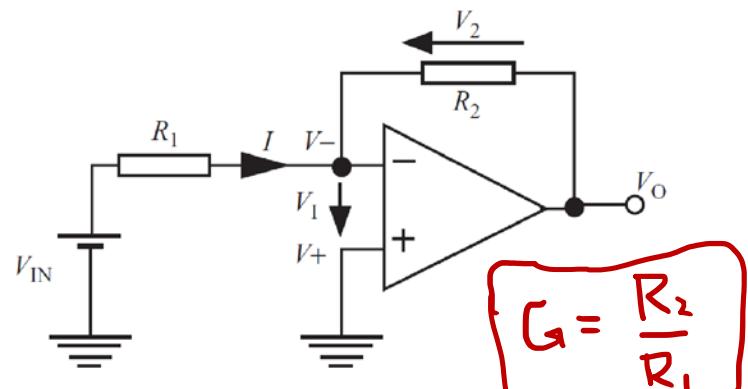


Figure 11.8 The inverter circuit

$$\frac{V_O}{V_{IN}}(\omega) = -G \frac{\frac{1}{1 + \frac{G}{Aw}}}{1 + \frac{G}{Aw}}$$

DC-gain

$$\frac{V_O}{V_{IN}} \approx -G \frac{1}{1 + \frac{1 + j\omega/\omega_o}{A_o/G}}$$

$$= -G \frac{1}{1 + \frac{1}{\omega_o/G} + j\frac{\omega}{\omega_o(A_o/G)}}$$

$$\approx -G \frac{1}{1 + j\frac{\omega}{\omega'_o}}$$

where $\omega'_o = \omega_o \frac{A_o}{G}$

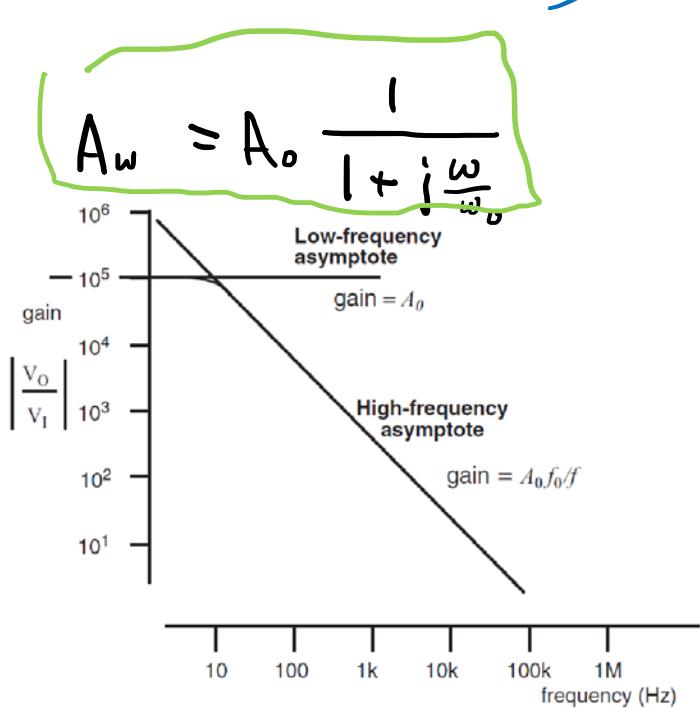


Figure 11.9 Typical low- and high-frequency asymptotes of the gain of an opamp

Inverter frequency response


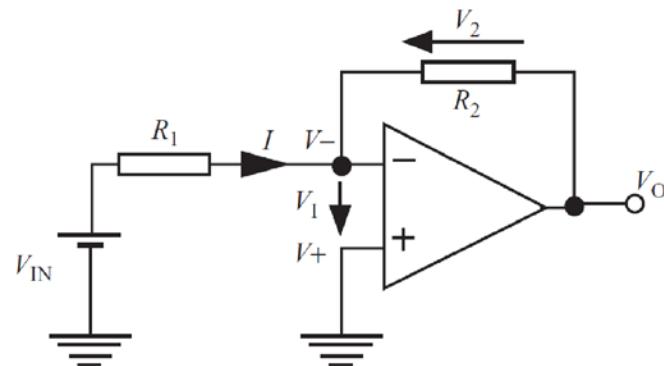


Figure 11.8 The inverter circuit

$$\frac{V_O}{V_{IN}} \approx -\frac{R_2}{R_1} \times \frac{1}{1 + j \frac{\omega}{\omega_o}}$$

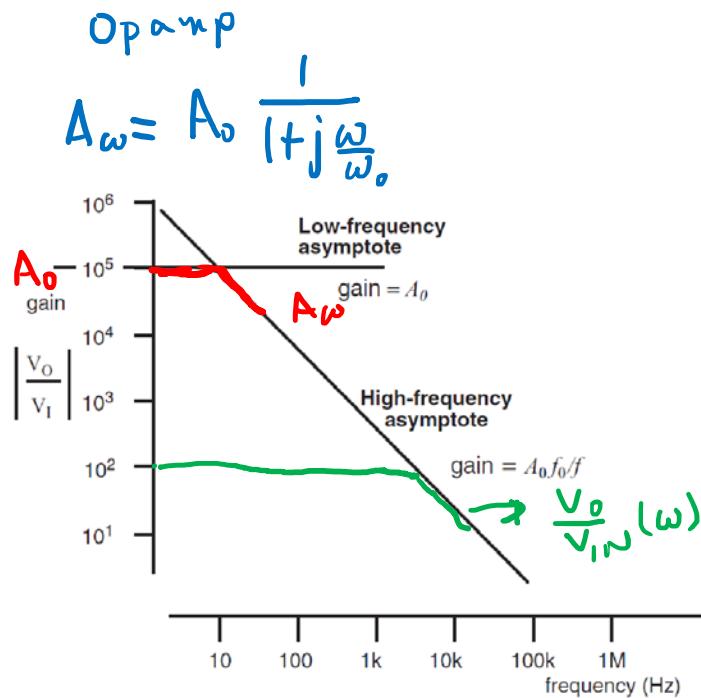G : dc gain $\omega_o' = \omega_o \cdot \frac{A_o}{(R_2/R_1)} = \omega_o \cdot \frac{A_o}{G}$



If $G = \frac{R_2}{R_1} = 100$
 $A_o = 10^5$

$$\Rightarrow \omega_o' = \omega_o \cdot 1000$$

Opamp \rightarrow Inverter
 Gain $10^5 \rightarrow 100 \downarrow$
 Cut-off freq $10^4 \text{ Hz} \rightarrow 10000 \uparrow$

Figure 11.9 Typical low- and high-frequency asymptotes of the gain of an opamp

Inverter frequency response



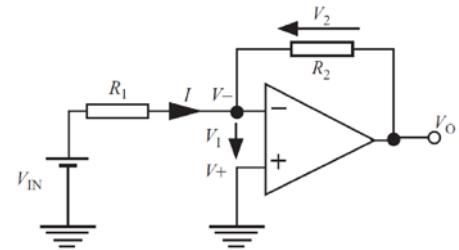


Figure 11.8 The inverter circuit

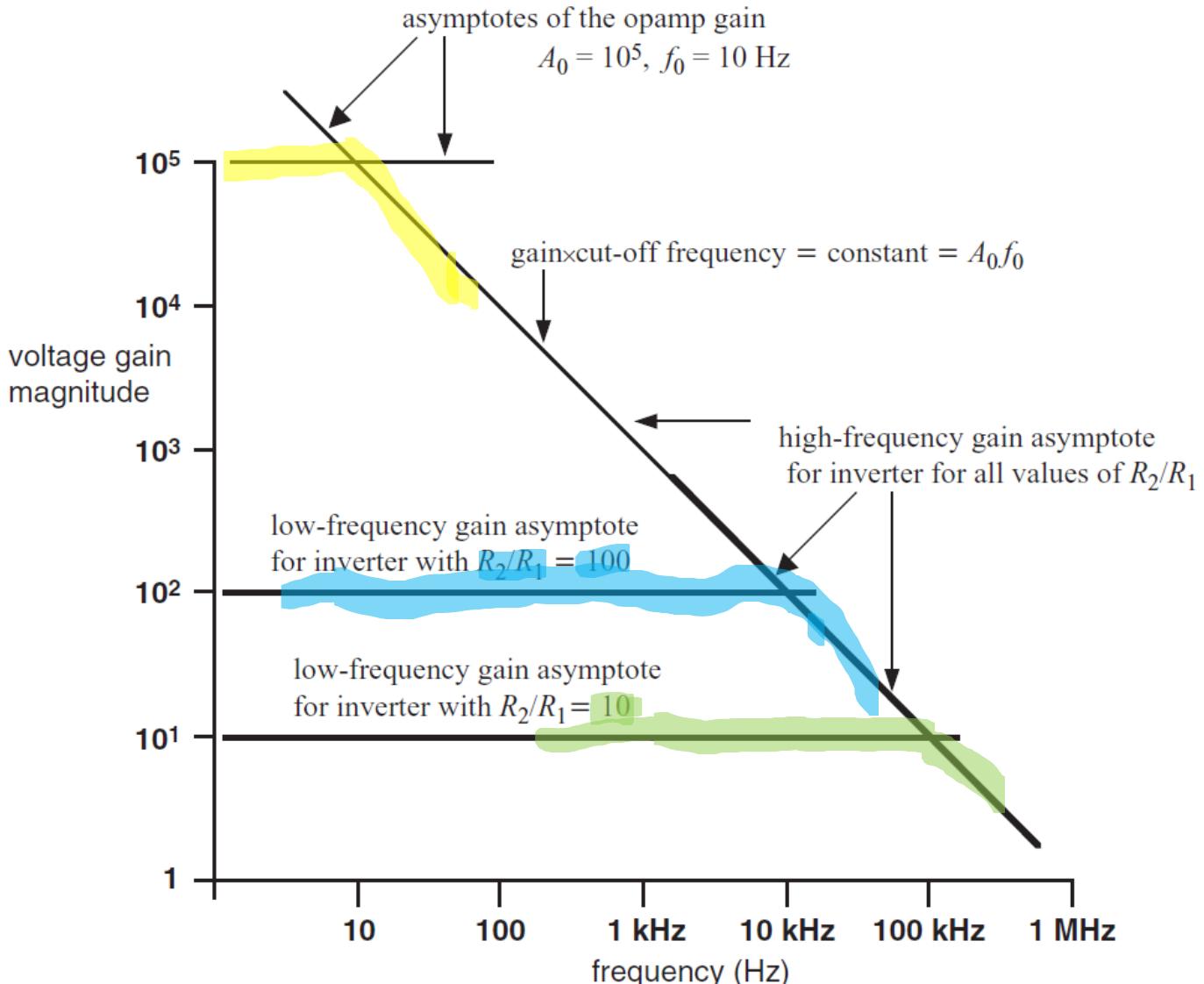

Summary

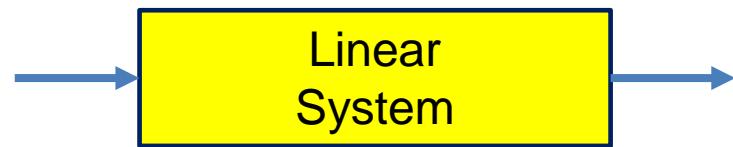

$$H(\omega)$$

Log-Log Scale

"Bode" plot

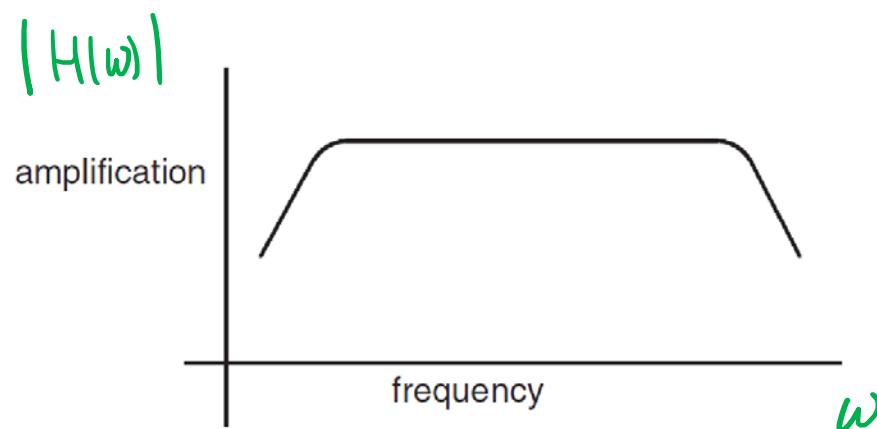


Figure 11.1 Typical form of the frequency dependence of an amplifier's gain