

電子電工學

Lecture 9



Midterm Exam II info


Date: Nov 25, 2020 (Wed)

Time: 3:10 ~ 6:00 pm (in class)

Location: 化工系館柏林講堂/93156

Coverage: Textbook ~ Chapter 8

Recap: Negative Feedback

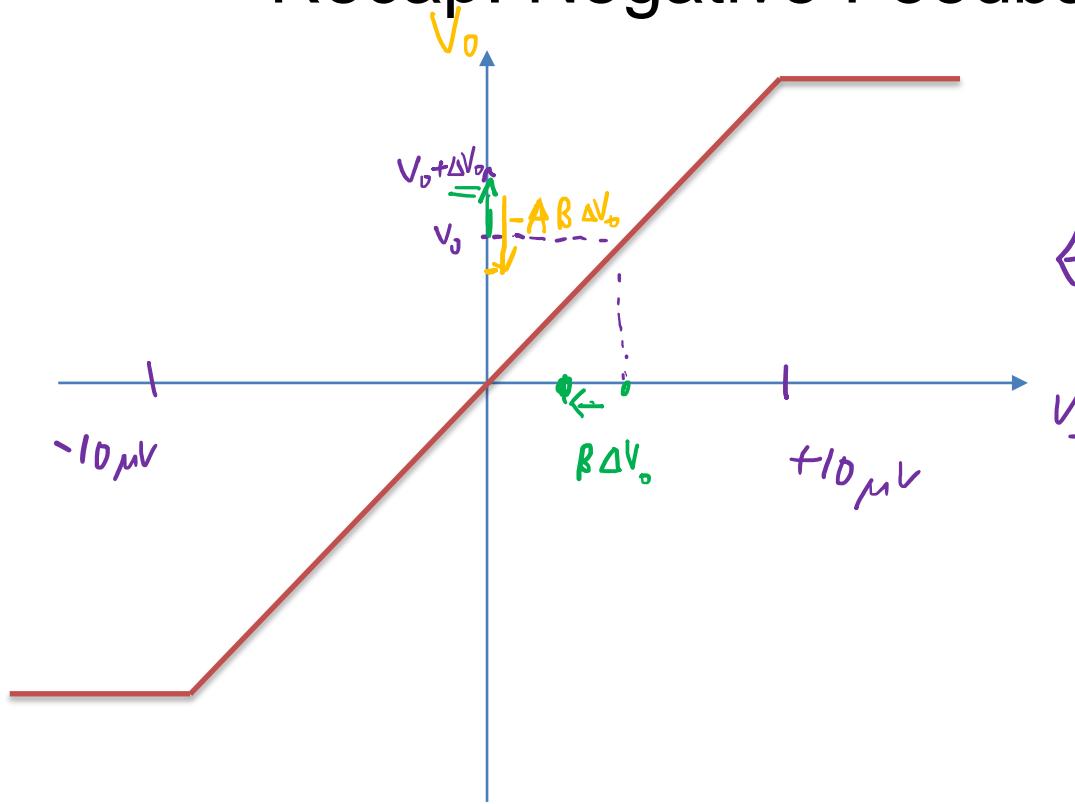

$$\begin{cases} V_{\Sigma} = V_{IN} - \beta V_O \\ V_O = A V_{\Sigma} \end{cases}$$

$$\Rightarrow \frac{V_O}{V_{IN}} = \frac{A}{1 + A\beta} \xrightarrow{A \rightarrow \infty} \frac{1}{\beta}$$

$Z_{DM IN}$

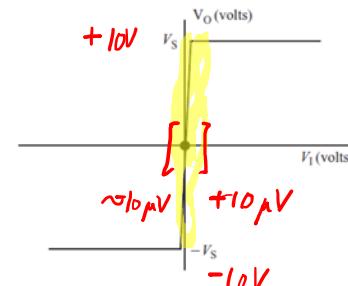


Figure 6.2 The form of the relation between the input V_I and output V_O voltages of an opamp

$$V_I = V_+ - V_-$$

$G_{out} \sim 10^5$

$$V_O = A V_I$$

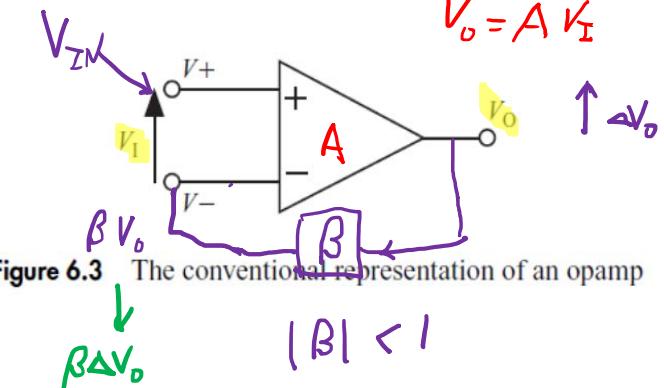




Figure 6.3 The conventional representation of an opamp

\Rightarrow STABLE CIRCUIT

Convert an Ammeter into a Voltmeter.

Example 7.3

To measure upto 5 V
 $R = ?$

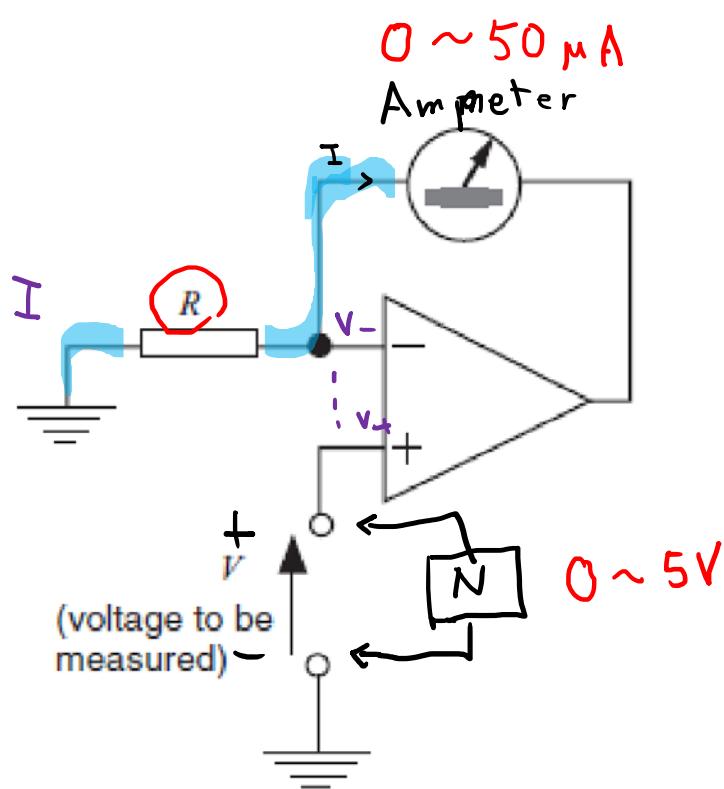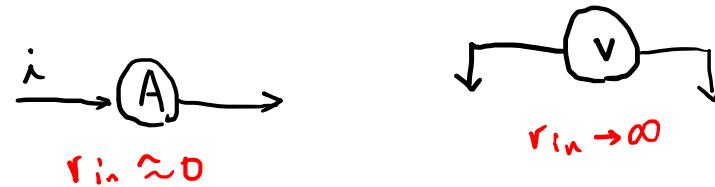

Negative Feedback

→ Virtual short Ckt

$$\rightarrow V_- = V_+ = V$$

$$\rightarrow I = \frac{0 - V_-}{R} = -\frac{V}{R}$$

$50 \mu A$

$$\rightarrow R = \frac{5V}{50 \mu A} = 100 k\Omega$$

Figure 7.16 A high-input-resistance voltmeter

Chapter 8

Mixed and Dynamic Opamp Circuits

Capacitor


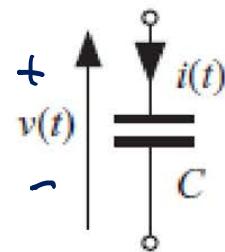


Figure 8.1 The symbol representing a capacitor. The constant C is its capacitance in farads

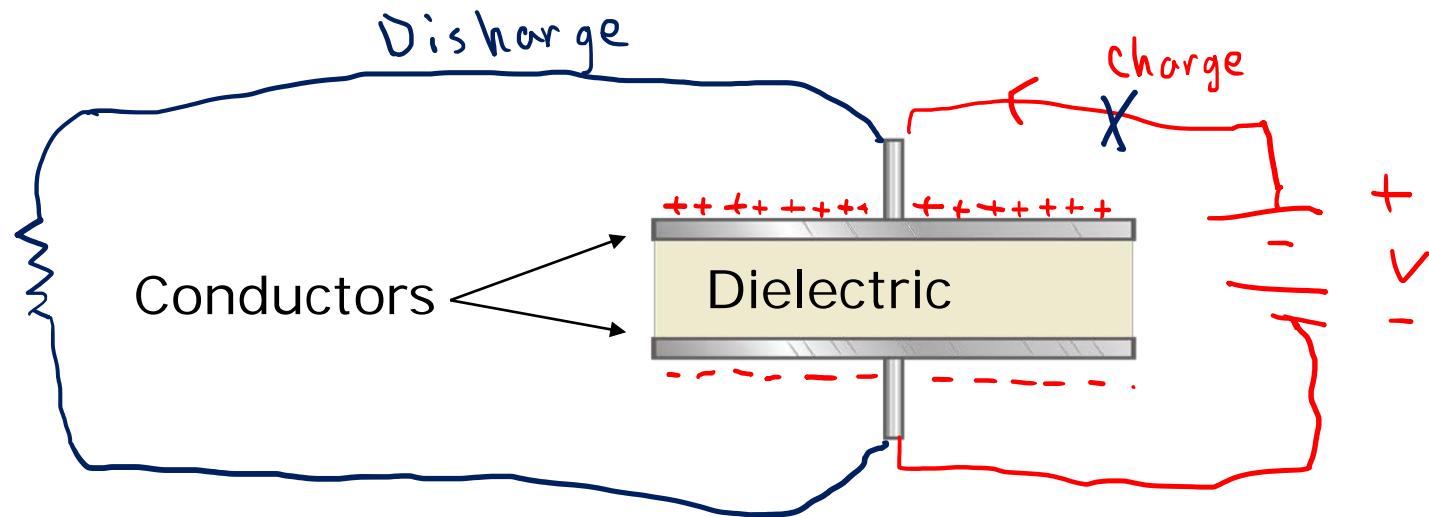

FIGURE 3.2 Some examples of practical capacitors.

Capacitor

Capacitance

(Farad)


$$C = \frac{q(t)}{v(t)}$$

Charge (Coulomb)

$v(t) = i(t) \cdot t$

$$q(t) = C \cdot v(t) \xrightarrow{\frac{d}{dt}} i(t) = C \cdot \frac{d}{dt} v(t)$$
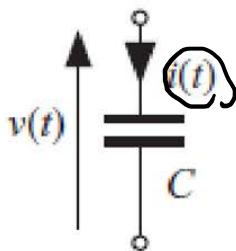
$$v(t) = \frac{1}{C} \int_{-\infty}^t i(\tau) d\tau$$



$$\boxed{q(t) = C \cdot v(t)}$$

$$i(t) = C \cdot \frac{d}{dt} v(t)$$

$$v(t) = \frac{q(t)}{C}$$

$$= \frac{1}{C} \int_{-\infty}^t i(\tau) d\tau$$

Figure 8.1 The symbol representing a capacitor. The constant C is its capacitance in farads

Capacitor

$$v(t) = \frac{1}{C} \int_{-\infty}^t i(\tau) d\tau$$


$$= \frac{1}{C} \left[\int_{-\infty}^0 i(\tau) d\tau + \int_0^t i(\tau) d\tau \right]$$

$$= v(0) + \frac{1}{C} \int_0^t i(\tau) d\tau$$


↑
Initial Voltage of Capacitor

$$v(t) = v(0) + \frac{1}{C} \int_0^t i(\tau) d\tau$$
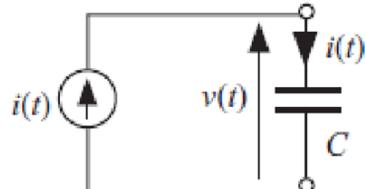
$$v(t) = v(0) + \frac{1}{C} \int_0^t I dt = \frac{v(0)}{C} + \frac{I}{C} t$$



$$v(0)$$

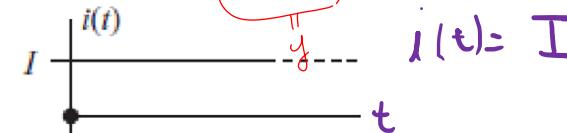

slope $\frac{I}{C}$

Figure 8.2 The application of a constant current to a capacitor, and the resulting voltage response

$$v(t) = \frac{1}{C} \int_{-\infty}^t i(\tau) d\tau$$

$$= \frac{1}{C} \left[\int_{-\infty}^0 i(\tau) d\tau + \int_0^t i(\tau) d\tau \right]$$

$$= v(0) + \frac{1}{C} \int_0^t i(\tau) d\tau$$

Capacitor

If $i(t) = I$ constant

$$v(t) = v(0) + \frac{1}{C} \int_0^t I \, dt$$
$$= v(0) + \frac{1}{C} \cdot I \cdot t$$

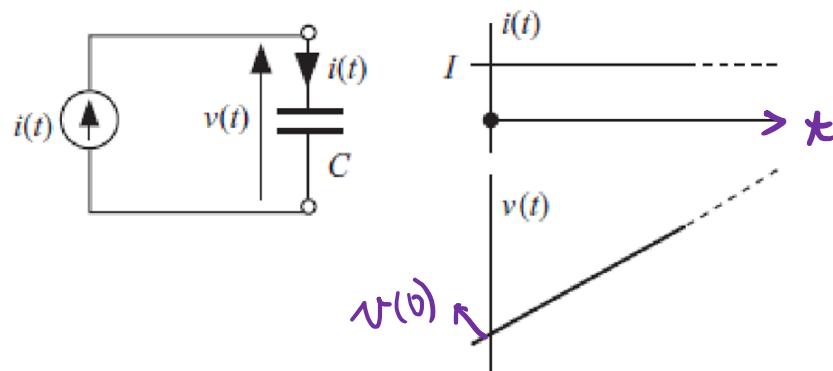


Figure 8.2 The application of a constant current to a capacitor, and the resulting voltage response

Capacitor



$$v(t) = v(0) + \frac{1}{C} \int_0^t i(\tau) d\tau$$

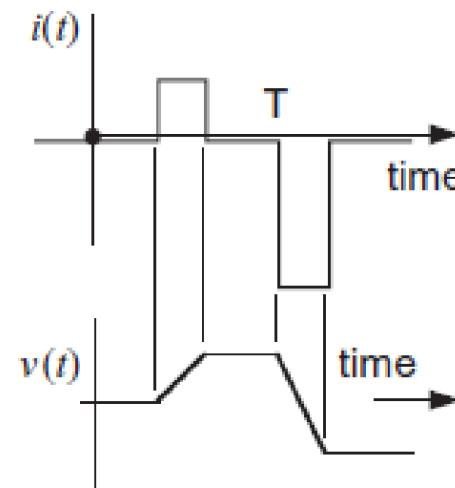
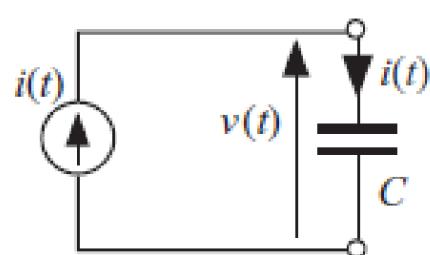


Figure 8.3 Response of a capacitor to a time-varying current source

Capacitor

$$i(t) = C \frac{dV(t)}{dt} \quad C = \frac{q(t)}{V(t)} \quad \therefore \frac{dq(t)}{dt} = i(t)$$

In practice, $V(t)$ does not change abruptly!

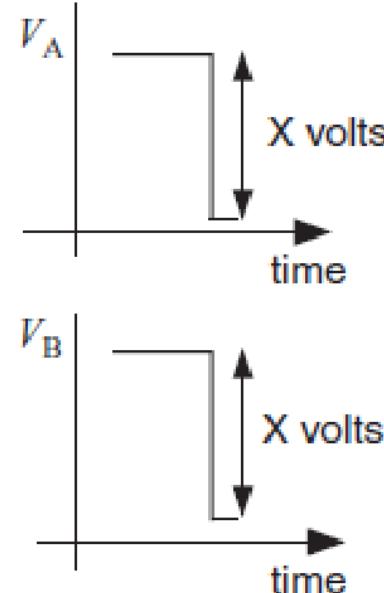
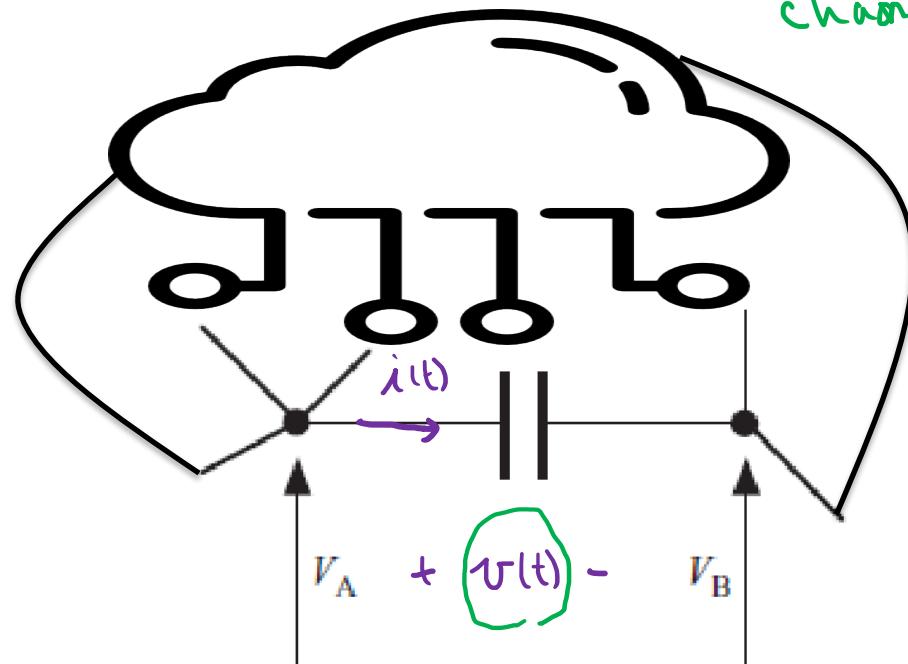


Figure 8.4 If the voltage at one terminal of a capacitor changes instantaneously, the voltage at the other terminal will exhibit the same change since, instantaneously, a capacitor voltage does not change

Capacitor

- Ⓐ A capacitor resists change in voltage
電容會抗拒電壓改變
- Ⓑ A inductor resists change in current
電感會抗拒電流改變

 A inductor resists change in current
電感會抗拒電流改變

A capacitor resists change in Voltage!
(inductor) (current)

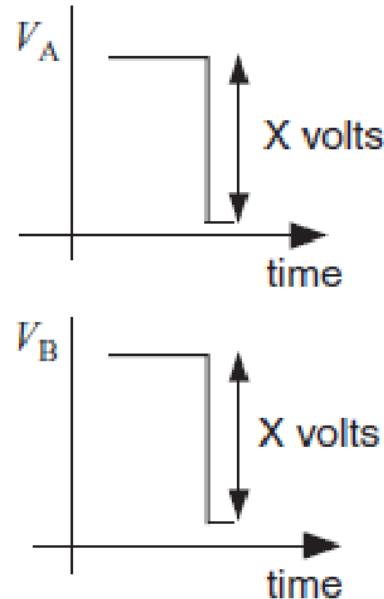
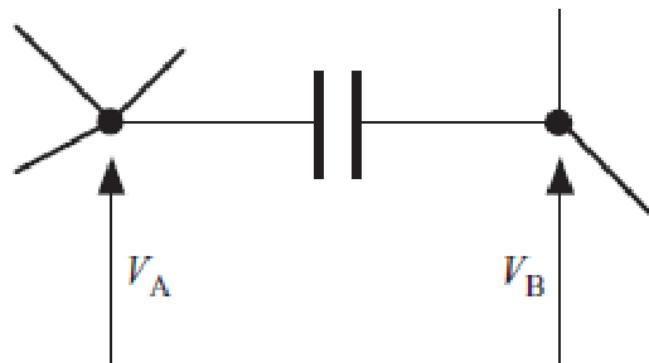


Figure 8.4 If the voltage at one terminal of a capacitor changes instantaneously, the voltage at the other terminal will exhibit the same change since, instantaneously, a capacitor voltage does not change


Integrator 積分器

Negative Feedback $\rightarrow V_I = 0 \therefore V_- = V_+ = 0$
 \Rightarrow Virtual short ckt $V_- = V_+ = 0$

$$i(t) = \frac{V_{IN}(t) - V_-}{R_1} = \frac{V_{IN}(t)}{R_1}$$

$$v_c(t) = v_c(0) + \frac{1}{C} \int_0^t i(\tau) d\tau$$
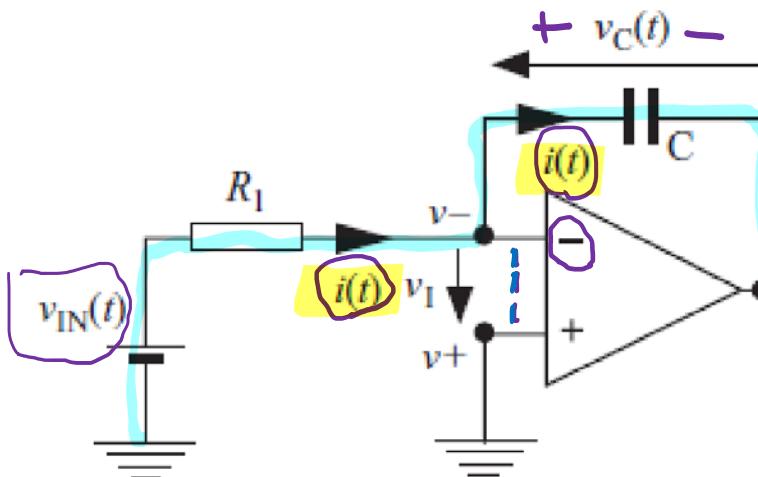
$$= v_c(0) + \frac{1}{R_1 C} \int_0^t V_{IN}(\tau) d\tau$$



$$i(t) = \frac{V_{IN}(t) - 0}{R_1} = \frac{V_{IN}(t)}{R_1}$$

$$v_c(t) = v_c(0) + \frac{1}{C} \int_0^t i(\tau) d\tau$$

$$= v_c(0) + \frac{1}{R_1 C} \int_0^t V_{IN}(\tau) d\tau$$

$$V_- - V_o(t) = -V_o(t)$$

$$V_o(t) = -V_c(0) - \frac{1}{R_1 C} \int_0^t V_{IN}(\tau) d\tau$$

Figure 8.5 An integrating circuit

$$V_o(t) = -V_c(0) \boxed{-\frac{1}{R_1 C} \int_0^t V_{IN}(\tau) d\tau}$$

Integrator

$$\therefore V_o(t) = k \int_0^t V_{IN}(\tau) d\tau$$

$$V_o(t) = V_- - V_c(t)$$

$$= -V_c(0) - \underbrace{\frac{1}{R_1 C}}_{k} \int_0^t V_{IN}(\tau) d\tau$$

If $V_c(0) = 0$

$$\Rightarrow V_o(t) \propto \int_0^t V_{IN}(\tau) d\tau$$

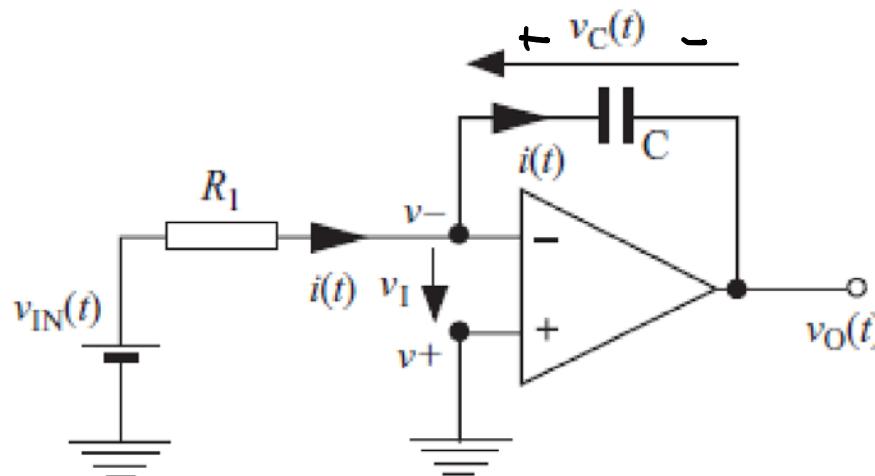


Figure 8.5 An integrating circuit

Example 8.1

$$V_o(t) = V_o(0) - \frac{1}{R_1 C} \int_0^t v_{IN}(\tau) d\tau$$

$$= V_o(0) - 100 \int_0^t v_{IN}(\tau) d\tau$$

$$V_o(t) = V_o(0) - \frac{1}{R_1 C} \int_0^t v_{IN}(\tau) d\tau$$

$$V_o(t) = -6 - 1000t$$

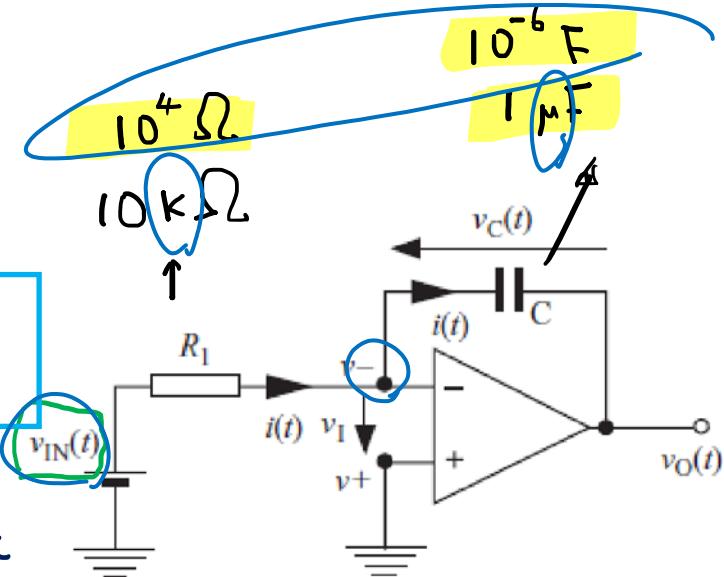


Figure 8.5 An integrating circuit

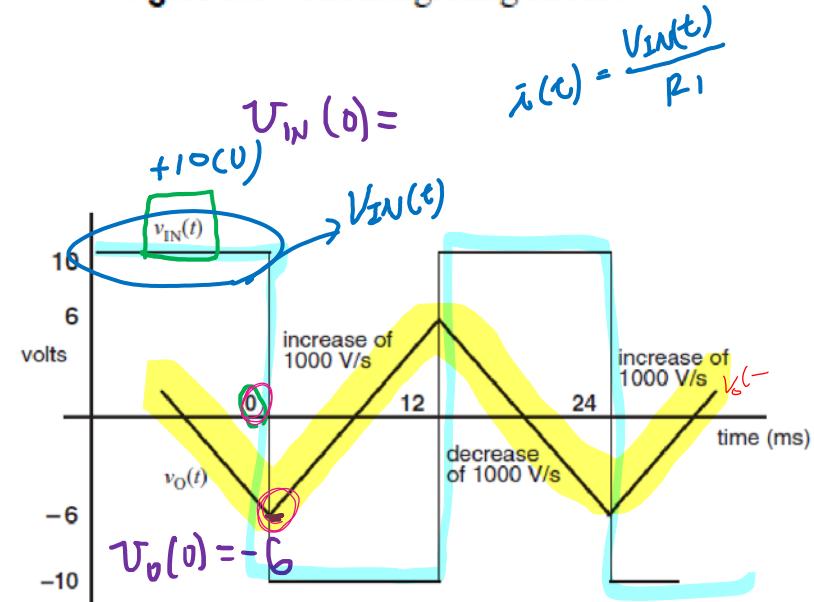



Figure 8.6 The input and output voltages of the integrator of Figure 8.5 (numerical values refer to Example 8.1)

Example 8.1

For $0 < t < 12 \text{ ms}$

$$v_{IN}(t) = -10 \text{ V}$$
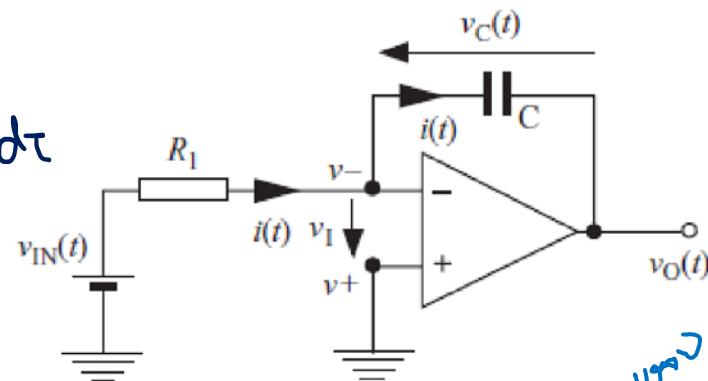
$$\begin{aligned} v_o(t) &= v_o(0) - 100 \int_0^t (-10) dt \\ &= -6 + 1000t \end{aligned}$$



v_+ = v_-

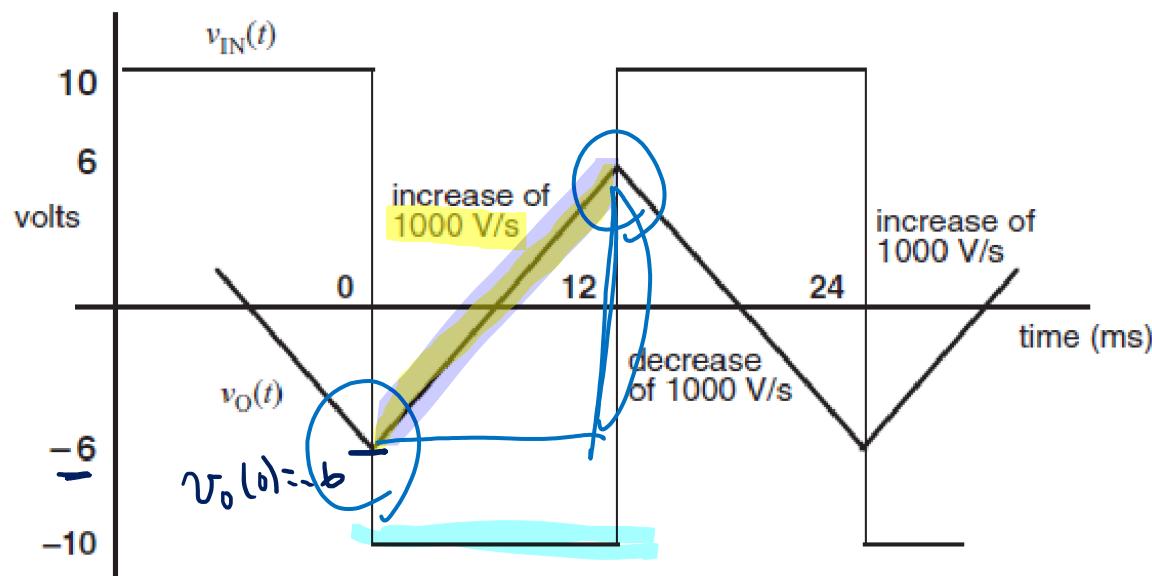


Figure 8.6 The input and output voltages of the integrator of Figure 8.5 (numerical values refer to Example 8.1)

Example 8.1

For $12 < t < 24$ ms

$$v_{IN}(t) = +10 \text{ V}$$

$$v_o(t) = v_o(12) - 100 \int_{12 \text{ ms}}^t (+10) dt$$

$$= 6 - 1000(t - 12)$$

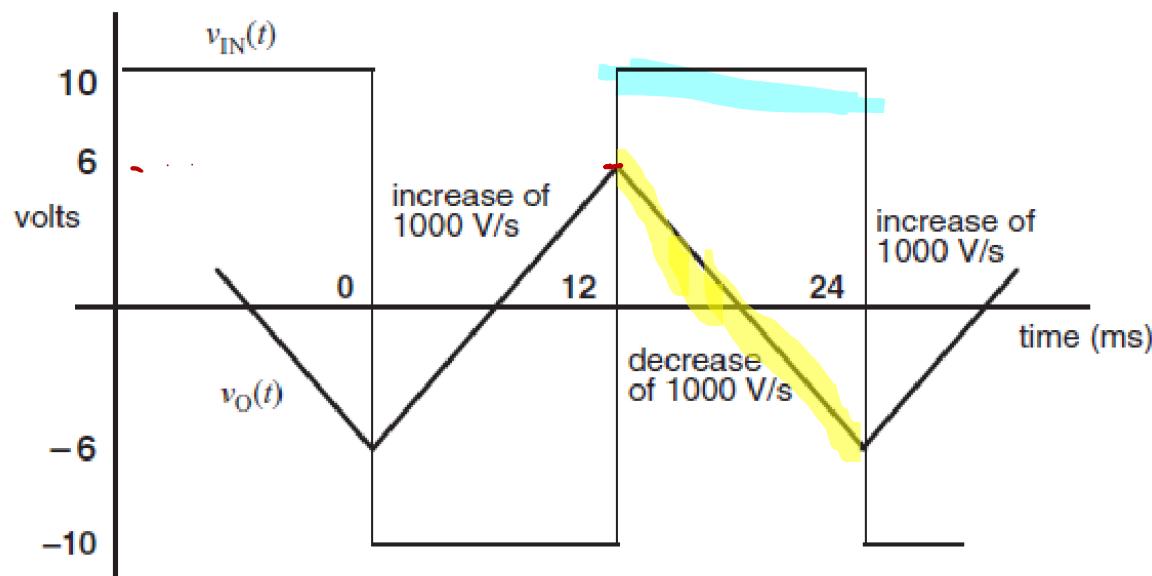
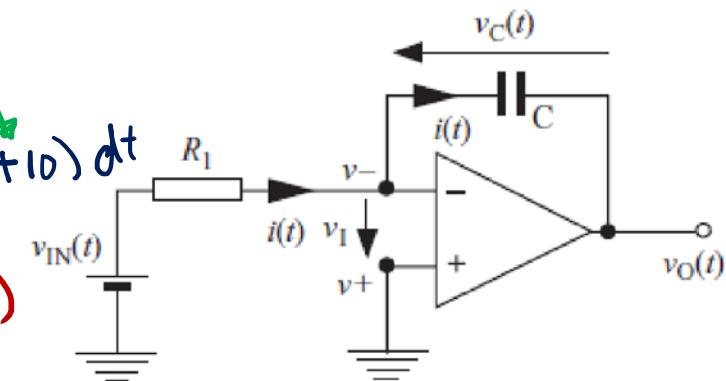


Figure 8.6 The input and output voltages of the integrator of Figure 8.5 (numerical values refer to Example 8.1)

Example 8.2

Dynam. Opamp Ckt

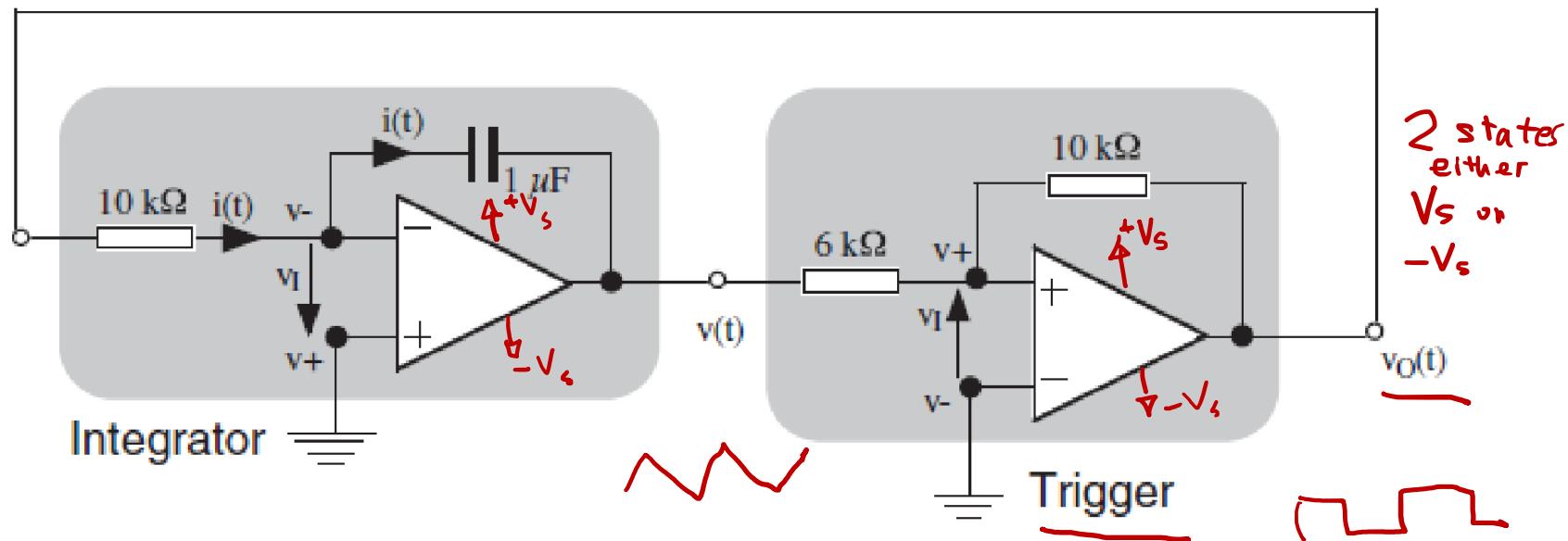


Figure 8.7 The circuit analysed in Example 8.2

Trigger circuit

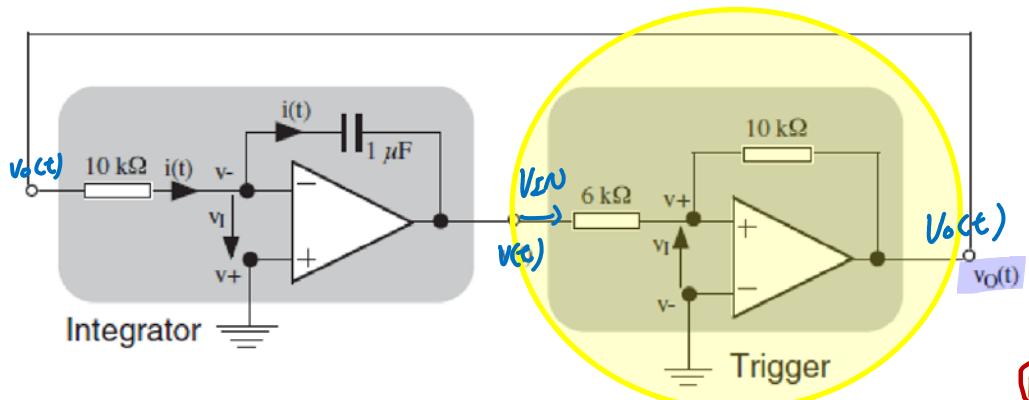


Figure 8.7 The circuit analysed in Example 8.2


When $V_o(t) = +V_s \Rightarrow V_{th} = -\frac{R_1}{R_2} V_s$

$$\left\{ \begin{array}{l} V_{IN} > V_{th} \Rightarrow V_o = +V_s \\ V_{IN} < V_{th} \Rightarrow V_o = -V_s \end{array} \right.$$

$$\left\{ \begin{array}{l} +V_s \quad V_{th} = -\frac{R_1}{R_2} V_s \quad \left\{ \begin{array}{l} V_{IN} > V_{th} + V_s \\ V_{IN} < V_{th} - V_s \end{array} \right. \\ -V_s \quad V_{th} = \frac{R_1}{R_2} V_s \quad \left\{ \begin{array}{l} V_{IN} < V_{th} + V_s \\ V_{IN} > V_{th} - V_s \end{array} \right. \end{array} \right.$$

$$+V_s \quad V_{th} = -\frac{R_1}{R_2} V_s \quad \left\{ \begin{array}{l} V_{IN} > V_{th} + V_s \\ V_{IN} < V_{th} - V_s \end{array} \right.$$
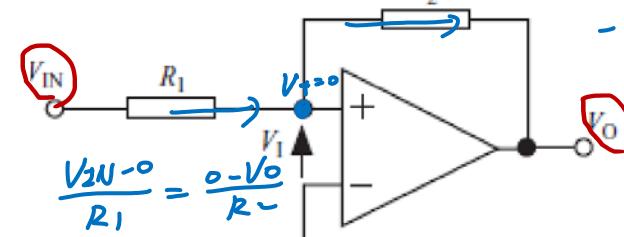
$$-V_s \quad V_{th} = \frac{R_1}{R_2} V_s \quad \left\{ \begin{array}{l} V_{IN} < V_{th} + V_s \\ V_{IN} > V_{th} - V_s \end{array} \right.$$



When $V_o(t) = -V_s \Rightarrow V_{th} = +\frac{R_1}{R_2} V_s$

$$\left\{ \begin{array}{l} V_{IN} < V_{th} \Rightarrow V_o = -V_s \\ V_{IN} > V_{th} \Rightarrow V_o = +V_s \end{array} \right.$$

*State
reverse*

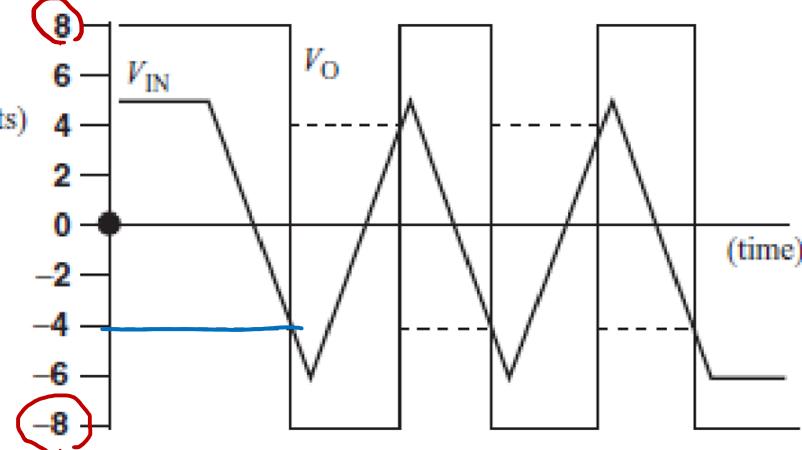


Figure 6.15 The waveform of the output voltage of the trigger circuit of Figure 6.13(a)

Integrator


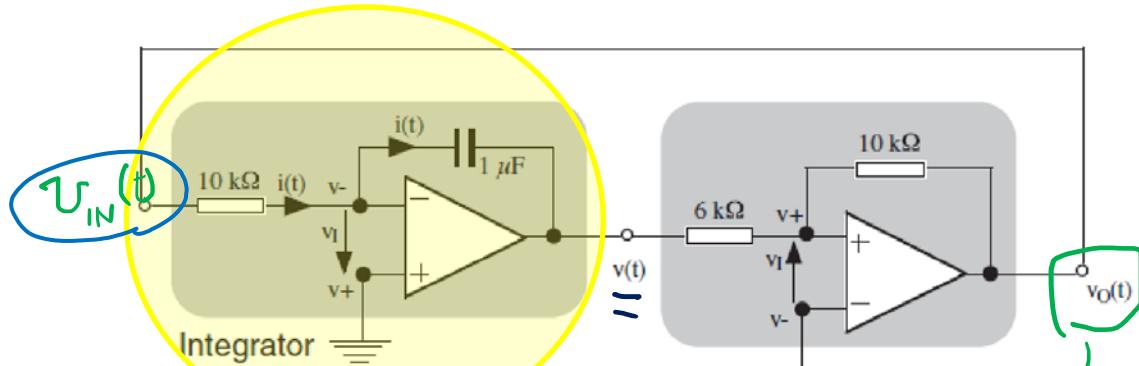
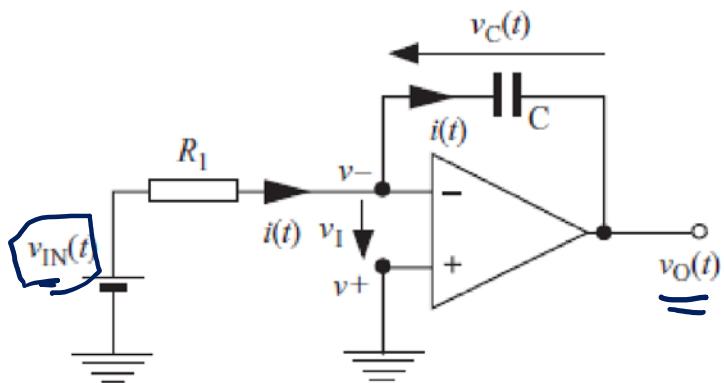


Figure 8.7 The circuit analysed in Example 8.2
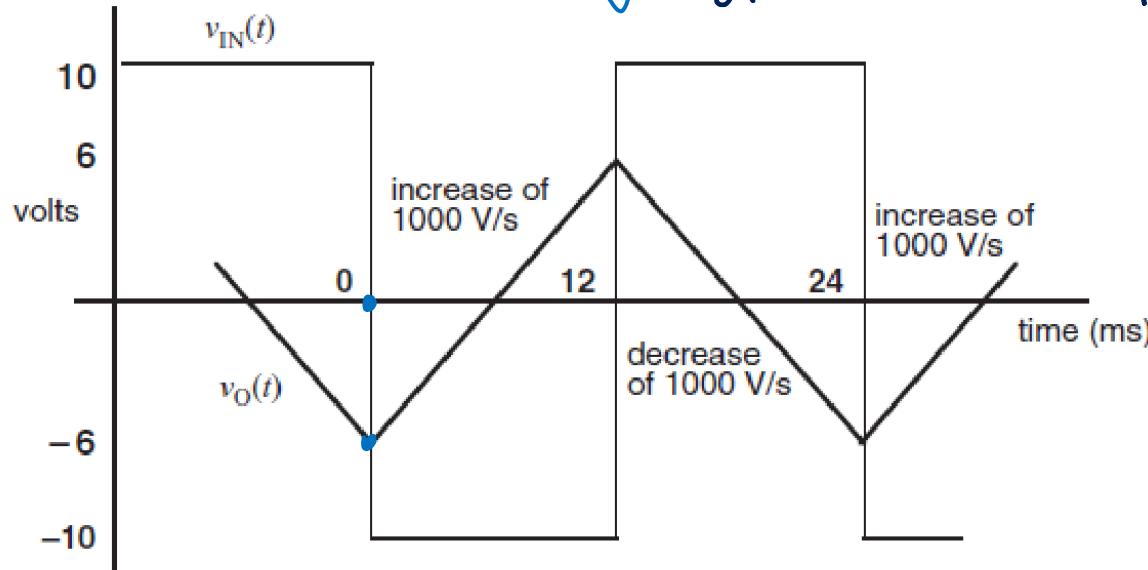
$$v_o(t) = v_o(0) - \frac{1}{R_1 C} \int_0^t v_{IN}(\tau) d\tau$$



2 states

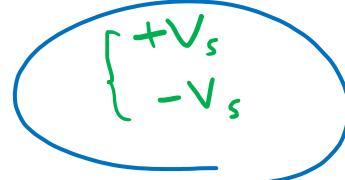


Figure 8.6 The input and output voltages of the integrator of Figure 8.5 (numerical values refer to Example 8.1)


Example 8.2 (1) $+ V_s$

For state $v_o(t) = +10V$

Integrator

$$v(t) = v(0) - \frac{1}{R_C} \int_0^t v_o(\tau) d\tau$$

$$= v(0) - 1000 t$$

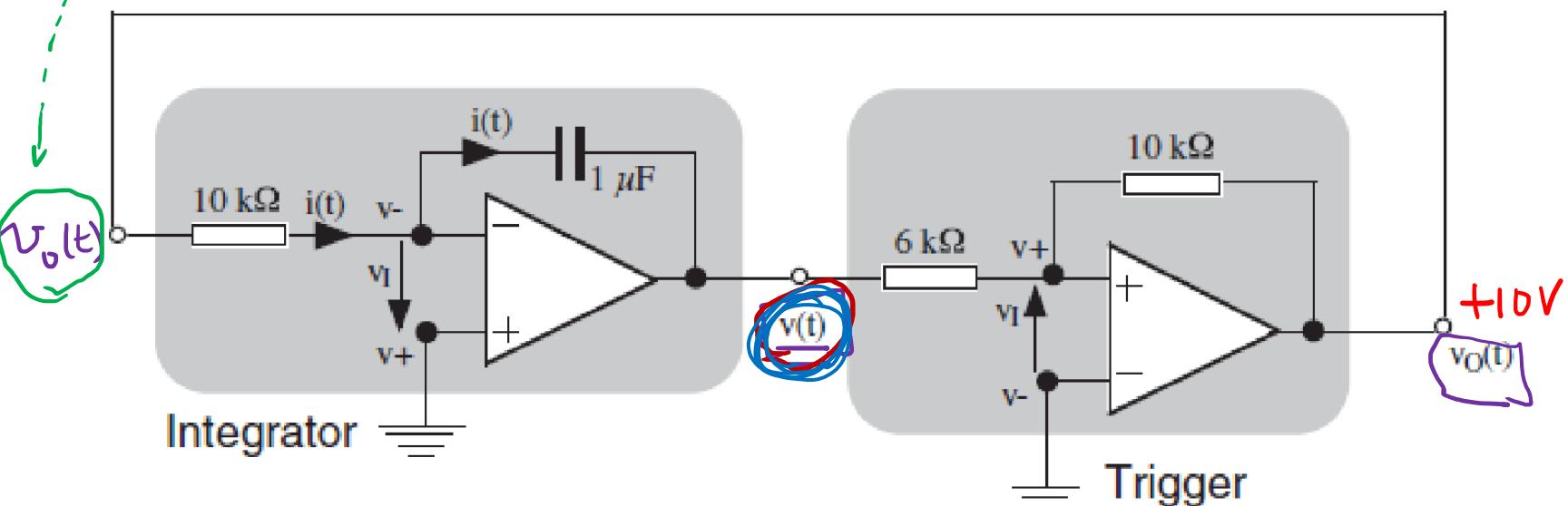

Trigger

$$V_{th} = -\frac{6}{10} \times 10 = -6V$$

If $v(t) > V_{th} \Rightarrow v_o(t) = +10V$

If $v(t) < V_{th} \Rightarrow v_o(t) = -10V$

V_{IN}

state reverse

Figure 8.7 The circuit analysed in Example 8.2

Example 8.2 (2)

For state $v_o(t) = -10V$
Integrator

$$v(t) = v(0) + 1000t$$

$$v(t) = v(0) - \frac{1}{R_1 C} \int_0^t v_{in}(t') dt' \\ v(t) = -10V$$

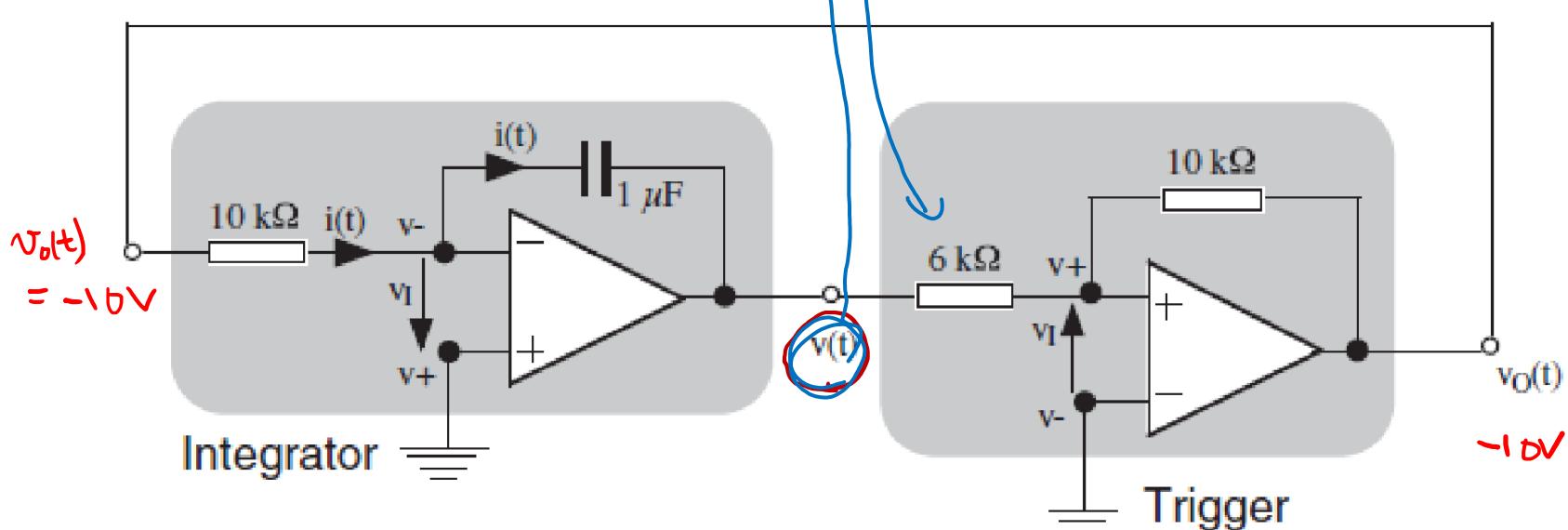


Figure 8.7 The circuit analysed in Example 8.2

Example 8.2 (3)

$$T = \text{period} = 24 \text{ ms}$$

$$\begin{aligned} f &= \text{frequency} = \frac{1}{\text{period}} \\ &= \frac{1 \text{ s}}{24 \text{ ms}} = 41.6 \text{ (Hz)} \end{aligned}$$

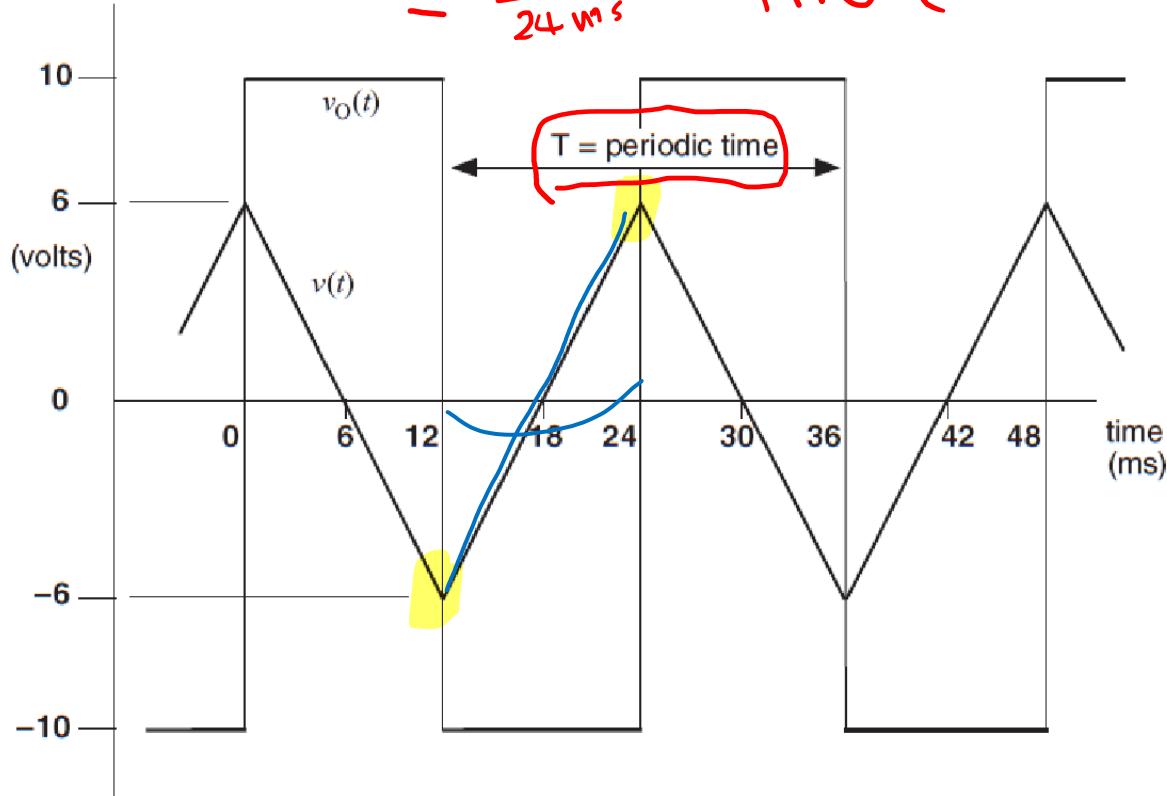


Figure 8.8 The voltages v_0 and v in the circuit of Figure 8.7

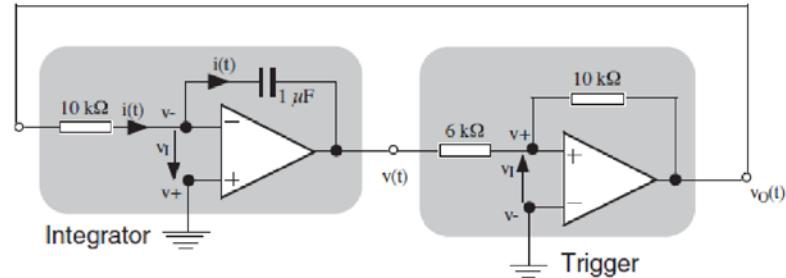


Figure 8.7 The circuit analysed in Example 8.2


Asymmetrical oscillator

$$\text{If } V_o = +10V \rightarrow i(t) = 1.5 \text{ mA}$$

$$\text{If } V_o = -10V \rightarrow i(t) = -0.5 \text{ mA}$$

$$v(t) = v(0) + \frac{1}{C} \int_0^t i(\tau) d\tau$$
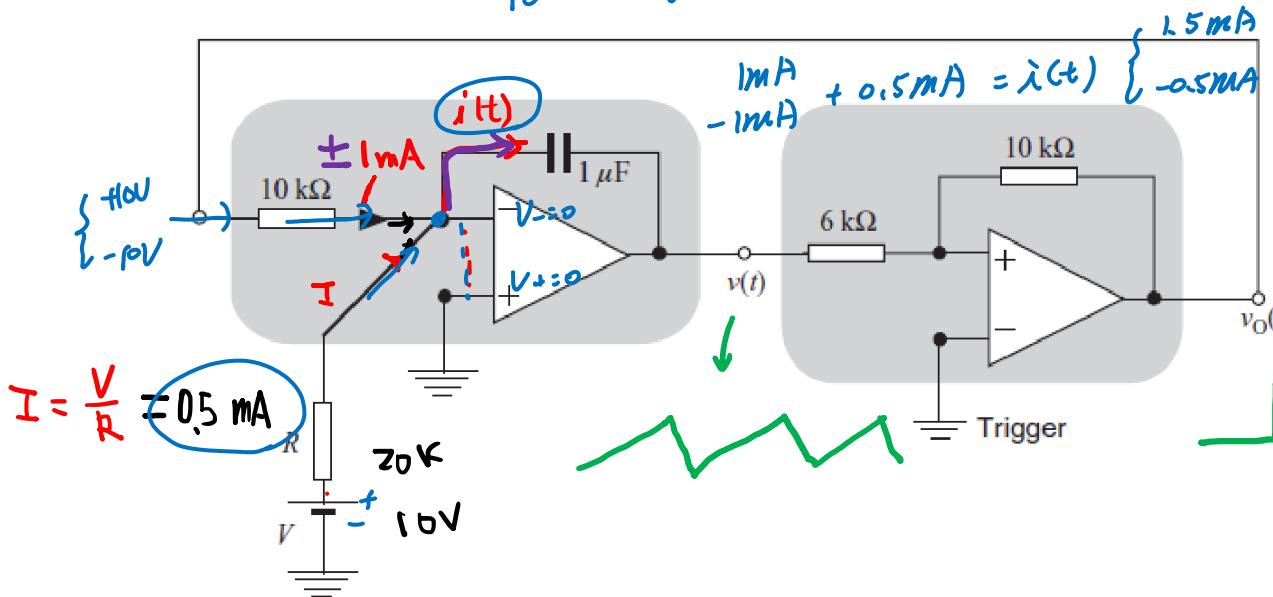
$$\frac{V_{IN} - 0}{10} = \begin{cases} 1mA \\ -1mA \end{cases}$$



$$V_{IN}(t) = V_{ch} + V_s$$

2 States

$$V_{out} = +10V$$

$$V_{IN} < V_{th}$$

$$V_{IN} > V_{th} + U_s$$

Figure 8.9 Modification to the circuit of Figure 8.7, resulting in asymmetrical waveforms

LAB 3. Asymmetrical Oscillator

Build an asymmetrical oscillator on the online simulator. For the opamps, set 'Max Output' to 10 and 'Min Output' to -10. Display $v(t)$ and $v_o(t)$. Export as text file and submit.

Suppose your student ID is
 $E(NN) 0 (BBB) (CC)$

Set the Voltage Source
 $V = 1.NN$

Set the resistor

$$R = 2.CC \text{ k}\Omega$$


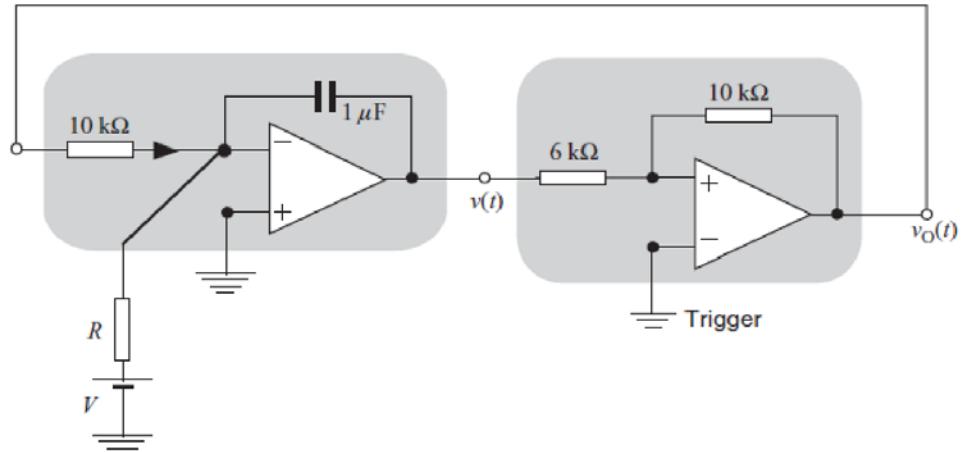


Figure 8.9 Modification to the circuit of Figure 8.7, resulting in asymmetrical waveforms

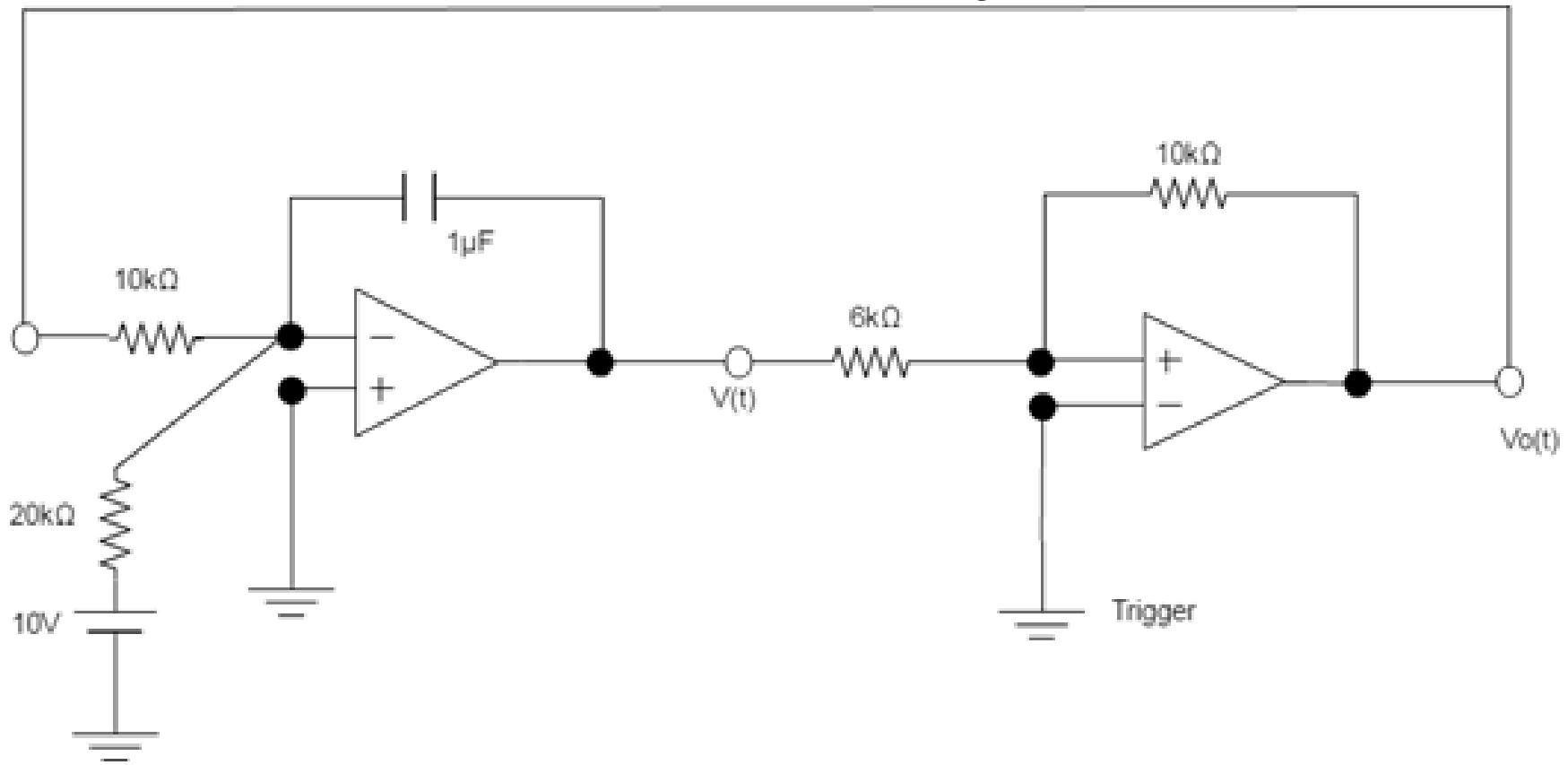Example: ID E34048154
NN=34, Voltage=1.34
CC=54, R=2.54 K

Quiz

Assume that the limits to V_O are +10 and -10 V, $V_O(0)=10$ V, $V(0)=6$ V. For the following circuit, draw the voltage waveforms of $V(t)$ and $V_O(t)$, respectively, for $0 < t < 80$ ms. What is the period of the waveform $V_O(t)$?



Quiz Review

For

$$V_o(t) = +10 \text{ V}$$

$$V_c(t) = V_c(0) + \frac{1}{C} \int_0^t i(\tau) d\tau$$

$\uparrow 10^{-6} \text{ F}$

$\uparrow 1.5 \text{ mA}$

$$= V_c(0) + 1500 t$$

$$V(t) = 0 - V_c(t) = -V_c(0) - 1500t$$

$$V(t) : 6 \text{ V} \rightarrow -6 \text{ V}$$



$$\Delta = \frac{(-6) - (+6)}{-1500} = 8 \mu\text{s}$$

$$V_c(t) = V_c(0) + \frac{1}{C} \int_0^t i(\tau) d\tau$$

\downarrow

$$\begin{cases} V_{IN} = +10 \text{ V} \Rightarrow +1 \text{ mA} \\ V_{IN} = -10 \text{ V} \Rightarrow -1 \text{ mA} \end{cases}$$
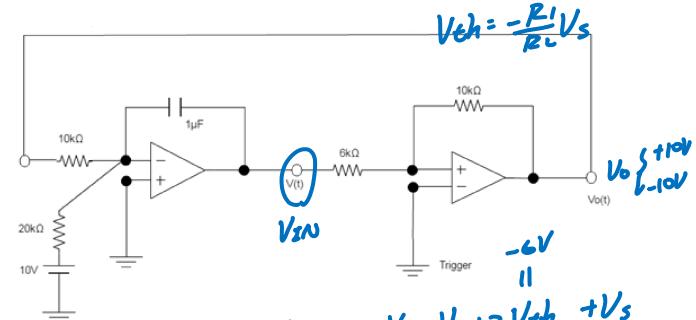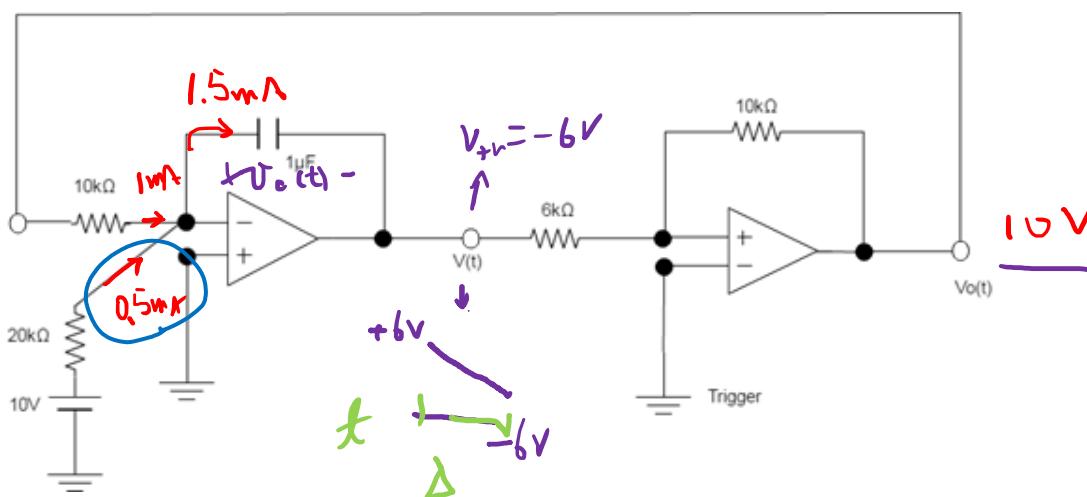
$$\Rightarrow i(t) \begin{cases} 1.5 \text{ mA} \\ -0.5 \text{ mA} \end{cases}$$



$$V_{th} = -\frac{R_1}{R_2} V_s$$

$$\begin{aligned} V_o &= +10 \text{ V} & V_{IN} &> V_{th} + V_s \\ V_{ZIN} &< V_{th} - V_s & V_{ZIN} &< V_{th} - V_s \\ &\Downarrow & &\Downarrow \\ & & -6 \text{ V} & -6 \text{ V} \end{aligned}$$

$$\begin{aligned} V_o &= -10 \text{ V} & V_{IN} &< V_{th} - V_s \\ V_{ZIN} &> V_{th} + V_s & V_{ZIN} &> V_{th} + V_s \\ &\Downarrow & &\Downarrow \\ & & 6 \text{ V} & 6 \text{ V} \end{aligned}$$

Quiz Review



For state $V_o(t) = -10V$

$$i(t) = -0.5 \text{ mA}$$

$$\text{slope} = +500 \text{ V/s}$$

$$\Delta = \frac{6 - (-6)}{500} = 24 \text{ ms}$$

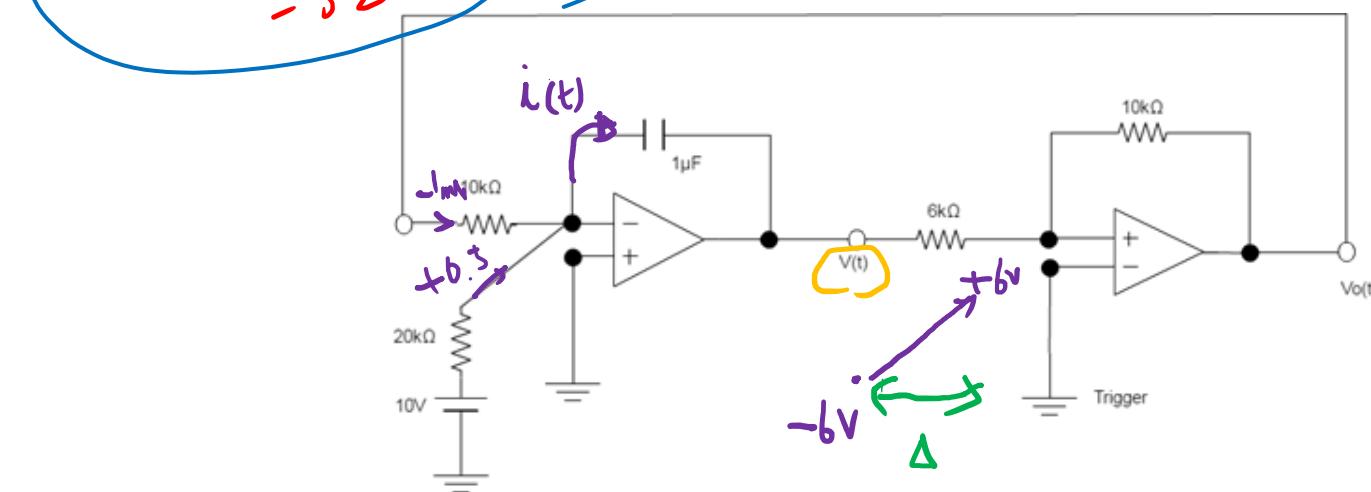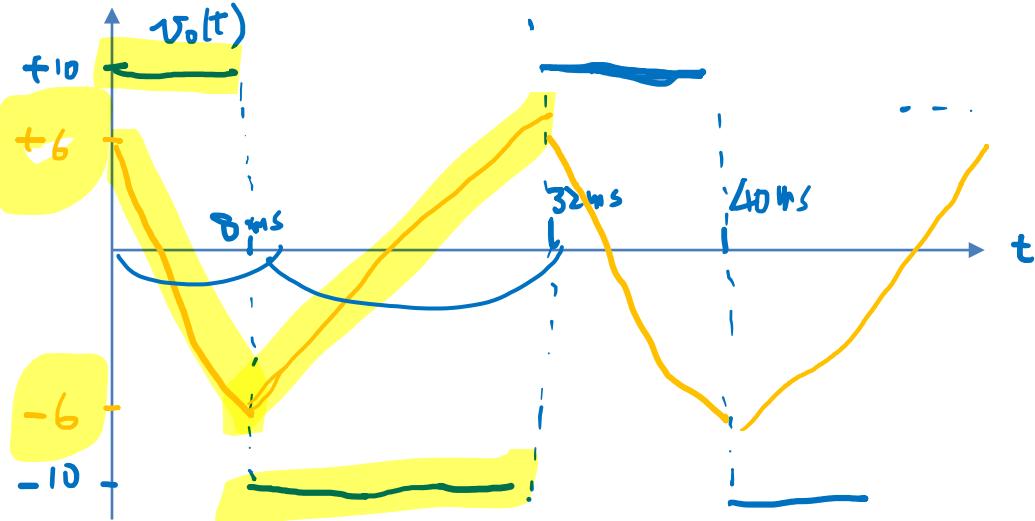Period = $8 \text{ ms} + 24 \text{ ms}$
 $= 32 \text{ ms}$



* Dependent Source

- . Nodal
- . Superposition
- . Thevenin

* Load-Line Analysis

* Opamp

Positive Feedback

Negative Feedback

* Capacitor \rightarrow Oscillation